

**LAHORE UNIVERSITY OF MANAGEMENT SCIENCES**  
**Department of Electrical Engineering**

**EE240 Circuits I**  
**Quiz 02 - Section 2**

---

**Name:** \_\_\_\_\_

**Campus ID:** \_\_\_\_\_

**Total Marks:** 10

**Time Duration:** 15 minutes

---

**Question 1** (4 marks)

The current entering the positive terminal of the inductor is  $i(t) = 3(1 - e^{-t})$  A for  $t \geq 0$  and  $i(t) = 0$  A for  $t < 0$ .

- (a) [2 marks] Determine the voltage across the inductor. Give an expression.
- (b) [1 mark] Determine the power absorbed by the inductor.
- (c) [1 mark] Determine the energy absorbed by the inductor in 2 seconds.

**Solutions:**

(a)  $v_L(t) = L \frac{di}{dt} = L 3e^{-t}$  Volts.

(b)  $p(t) = v_L(t) i(t) = L 3e^{-t} (1 - e^{-t})$  Watts.

(c)  $w(t) = \frac{1}{2} L i(t)^2 = L \frac{9}{2} (1 - e^{-t})^2 = 3.3644L$  Joules.

**Question 2** (6 marks)

The voltage across the  $0.5H$  inductor is given by  $v_L(t) = 4 \sin(\omega_o t)$ .

- (a) [2 marks] Evaluate the expression for the current  $i_L(t)$  through the inductor.
- (b) [2 marks] Plot the current, voltage and power versus time for  $0 \leq t \leq 4\pi/\omega_o$ . You must appropriately label the plots.
- (c) [1 mark] How does the amplitude of the current change with the increase in the frequency  $\omega_o$ ?
- (d) [1 mark] How much energy (average power) over one period is stored in an inductor?

**Solutions:**

(a)  $i_L = \frac{1}{L} \int v_L(t) dt = -\frac{8}{\omega_o} \cos(\omega_o t)$ .

(b) See next page

(c) The current decreases as evident in the expression evaluated on part(a).

(d)  $p(t) = -\frac{16}{\omega_o} \cos(\omega_o t) \sin(\omega_o t) = -\frac{8}{\omega_o} \sin(2\omega_o t)$ . Average over two periods is zero.

