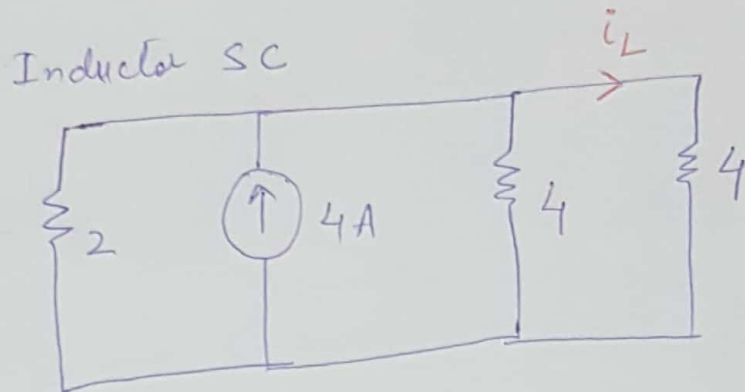


QUIZ - 05

Section 01

Solution


At $t = 0^-$



$$i_L(0^-) = 1A, v_o(0^-) = 4V$$

At $t = 0^+$

$$V_o(0^+) = 4V$$

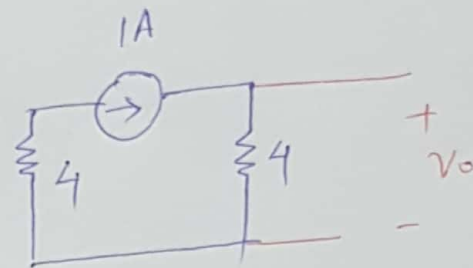

At $t = \infty$

$$V_o(\infty) = 0$$



Time constant:

$$\tau = \frac{L}{R_{eq}}$$

$$R_{eq} = 4 + 4 = 8 \Omega$$

$$\Rightarrow \tau = \frac{1}{2} \text{ sec}$$

$$V_o(t) = K_1 + K_2 e^{-t/\tau} \quad | \quad K_1 = 0, K_2 = 4$$

$$= 4 e^{-2t}$$

