

LAHORE UNIVERSITY OF MANAGEMENT SCIENCES
Department of Electrical Engineering

EE240 Circuits I
Quiz 09 - Section 2

Name: _____

Campus ID: _____

Total Marks: 10

Time Duration: 20 minutes

Question 1 (10 marks)

In the following circuit, the switch is moved from position 1 to position 2 at $t = 0$. Determine $v_o(t)$ for $t \geq 0$.

