

EE240 – Circuits I  
Mid Examination (Fall 2018)

**SOLUTIONS**

November 6, 2018

06:00 pm–08:30 pm

---

Student ID .....

Name .....

Signature .....


---

**INSTRUCTIONS:**

- Do not flip this page over until told to do so.
- **The exam needs to be solved on this book and not on blue book.**
- If you need the blue book for rough work, please ask the exam staff.
- The exam is closed book and notes. You are allowed to bring calculator and one A4 sheet with you with *hand-written* notes on both sides.
- Read all the questions before you start working on the exam.
- You cannot keep your mobile phone(s) with you (even on silent mode or switched off).

## Part 1: Sources and I-V Characteristics of R, L, C

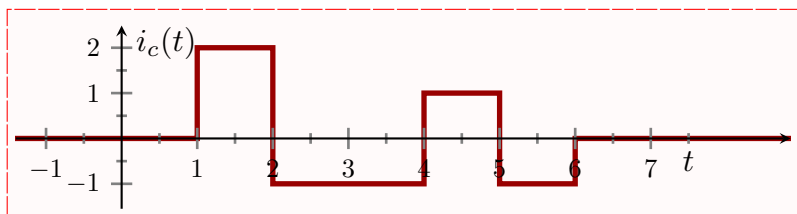**Problem 1.** (10 pts) The current  $i_c(t)$  through the capacitor of capacitance  $\frac{1}{2}F$  is shown in Figure 1 below.



(a) (1 pts) Express  $i_c(t)$  as piecewise function of time.


$$i_c(t) = \begin{cases} 0 & t < 1 \\ 2 & 1 \leq t < 2 \\ -1 & 2 \leq t < 4 \\ 1 & 4 \leq t < 5 \\ -1 & 5 \leq t < 6 \\ 0 & 6 \leq \end{cases}$$

(b) (8 pts) Assuming that the voltage is zero for times  $t \leq -1$  seconds, determine the voltage across the capacitor and **plot** for  $0 \leq t \leq 7$  seconds.

Let  $v_c(t)$  be the voltage across capacitor.

$$v_c(t) = \frac{1}{C} \int_{-\infty}^t i_c(t) dt$$
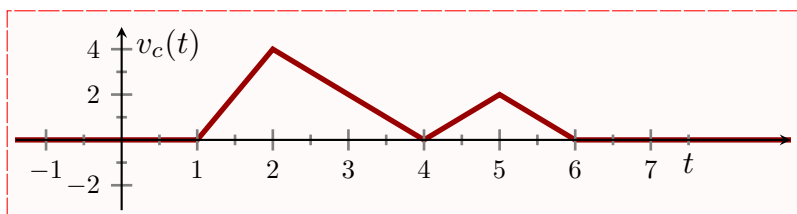
$$v_c(t) = 2 \begin{cases} 0 & t < 1 \\ 2t - 2 & 1 \leq t < 2 \\ -t + 4 & 2 \leq t < 4 \\ t - 4 & 4 \leq t < 5 \\ -t + 6 & 5 \leq t < 6 \\ 0 & 6 \leq \end{cases}$$




(c) (1 pts) Determine the energy stored in the capacitor at  $t = 3.5$  seconds.


$$w_c(t) = \frac{1}{2}C(v_c(t))^2 \Rightarrow w_c(3.5) = \frac{1}{4}(v_c(3.5))^2 = 0.25J.$$

**Problem 2. (6 pts)** Consider a circuit where the DC voltage source of  $5V$  is connected to a series combination of  $4\ \Omega$  resistor and  $1F$  capacitor through the switch. Assume that the switch is initially open and is closed at  $t = 0$  and the capacitor is uncharged before the switch is closed, that is, the capacitor voltage  $v_c(t) = 0$  for all  $t < 0$ .



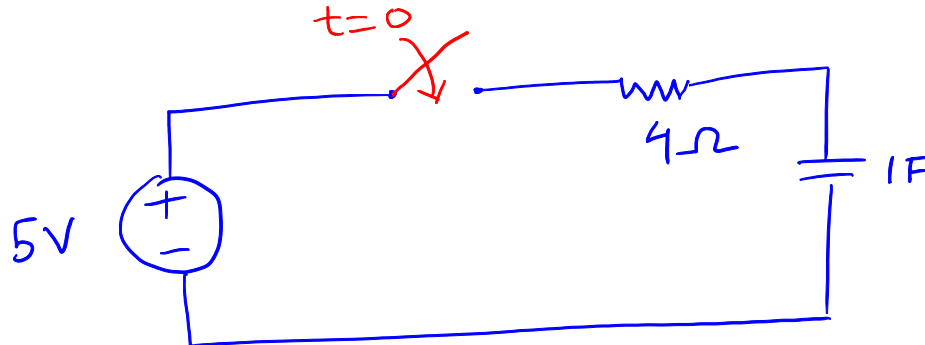
- (a) (1 pts) Draw the circuit and indicate the current  $i(t)$  through the circuit and the voltages  $v_R(t)$  and  $v_C(t)$  across the resistor and the capacitor respectively.



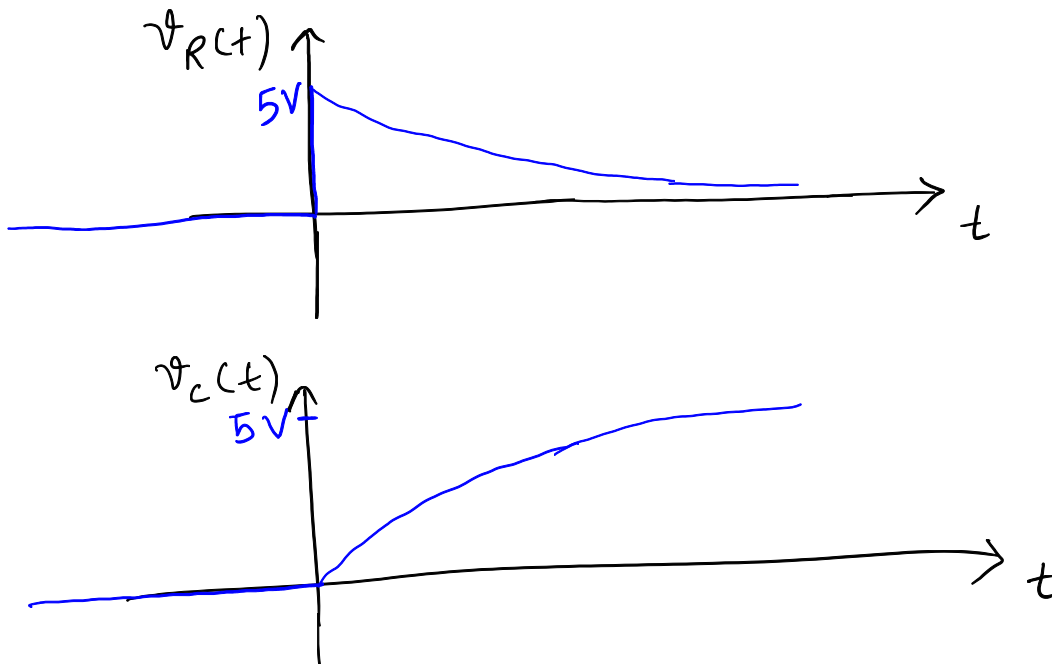- (b) (5 pts) Plot the waveforms (not to the scale) of the voltages  $v_R(t)$  and  $v_C(t)$ .







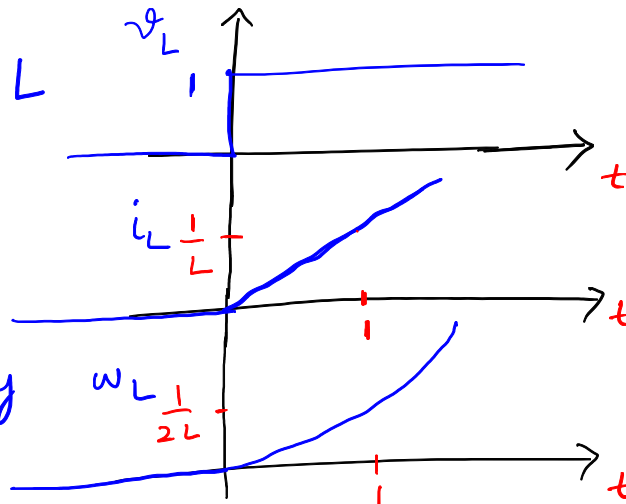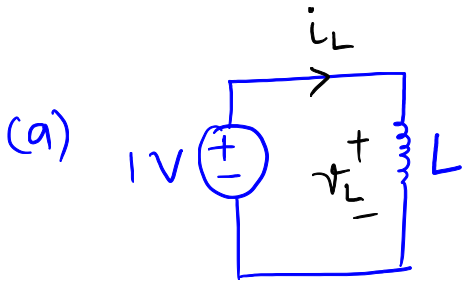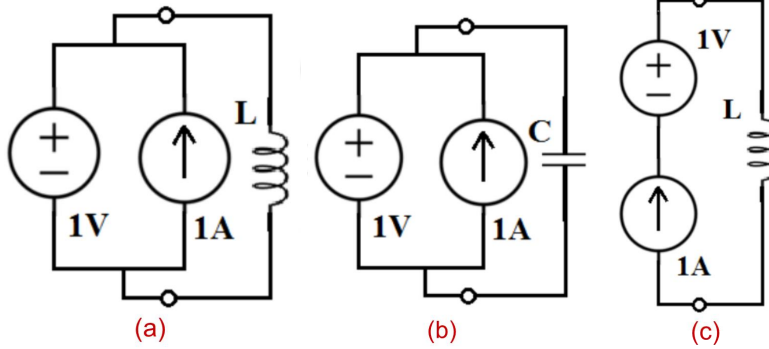**Problem 3. (9 pts)** Consider the following four circuits. Assuming that the sources are switched on at  $t = 0$  and the elements do not carry any current or voltage before the sources are turned-on, draw the voltage, current and energy waveform for  $0 \leq t \leq 1$  seconds for each circuit (element). Total of 9 waveforms.



$$i_L = \frac{1}{L} \int_{-\infty}^t v dt = \begin{cases} \frac{t}{L} & t \geq 0 \\ 0 & t < 0 \end{cases}$$
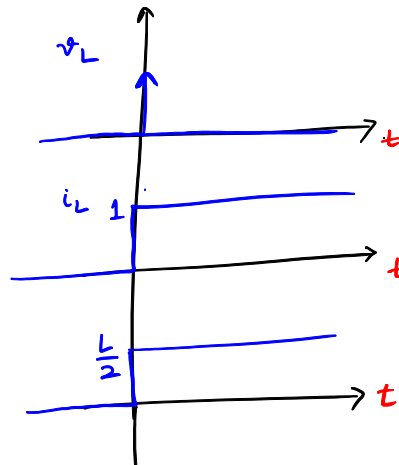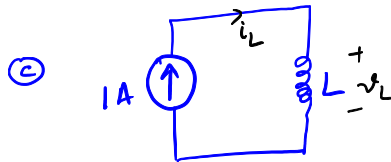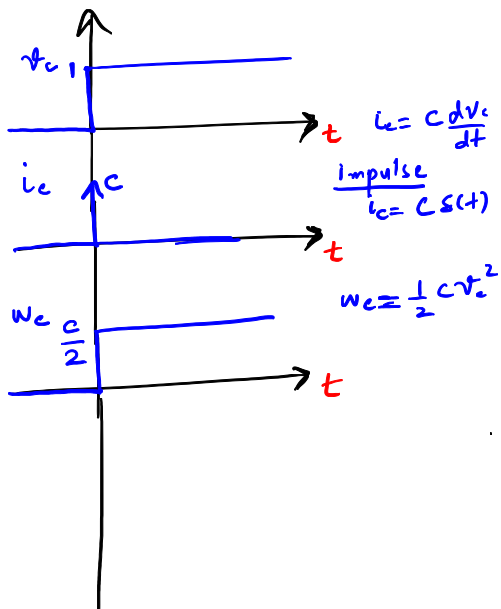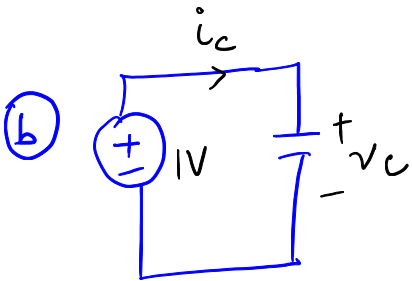
$$w_L = \frac{1}{2} L i^2 = \begin{cases} \frac{1}{2} \frac{t^2}{L} & t \geq 0 \\ 0 & t < 0 \end{cases}$$




$$v_L = L \frac{di_L}{dt} = L \delta(t)$$

$$w_L = \frac{1}{2} L i_L^2$$

## Part 2: Network Topology, Network Equations and Equivalent Circuits

### Problem 4. (20 pts)


Consider the circuit given below.

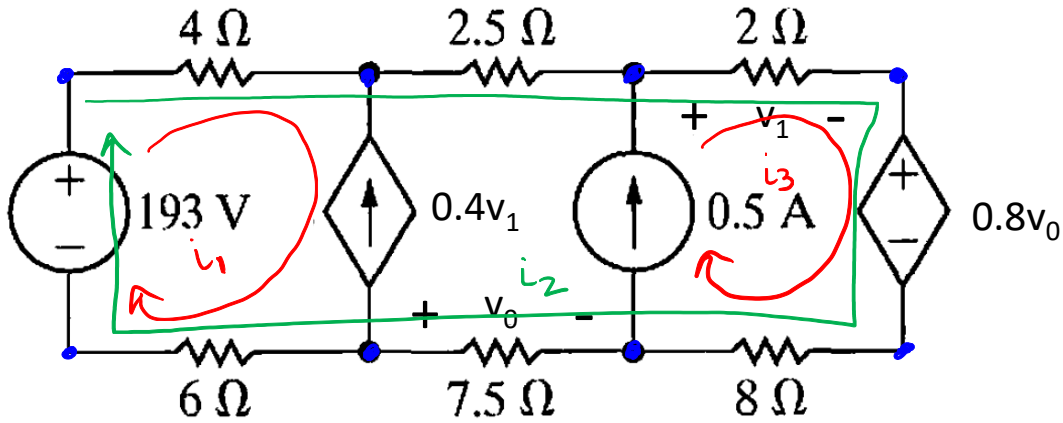


Nodes : Blue dots

- (a) (5 pts) Draw the graph and one tree of the circuit. Determine the number of nodes and number of branches in a circuit.

Graph

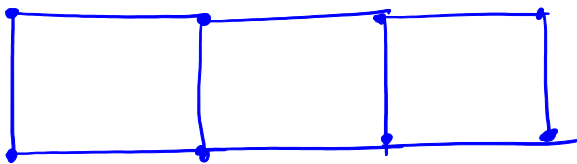

Tree (one possibility)

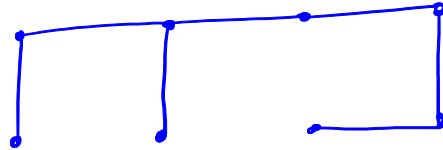

no. of nodes =  $n = 8$   
 no. of branches =  $b = 10$

- (b) (2 pts) Determine the number of network equations required for carrying out i) nodal analysis and ii) loop analysis.

Nodal Analysis : No. of equations =  $n - 1 = 7$   
Loop Analysis : No. of equations =  $b - (n - 1) = 3$

(c) (9 pts) Carry out the loop analysis, that is, identify and determine the loop currents.

Controlled Sources

$$v_0 = -7.5 i_2$$

$$v_1 = (i_2 + i_3)(2)$$

$$v_1 = 2i_2 + 1$$

Currents indicated on circuit

$$i_1 = -0.4 v_1 = -0.8 i_2 - 0.4$$

$$i_3 = 0.5 \text{ A}$$

Green loop :

$$10 i_1 + 30 i_2 + 10 i_3 + 0.8 v_0 = 193$$

$$10(-0.8 i_2 - 0.4) + 30 i_2 + 5 + (0.8)(-7.5 i_2) = 193$$

$$16 i_2 = 192 \Rightarrow i_2 = 12 \text{ A}$$

$$i_1 = -0.8 i_2 - 0.4$$

$$i_1 = -10 \text{ A}$$

(d) (4 pts) Determine the power delivered by the independent current source. 2

We find the voltage across current source as  $V_{AB}$


$$V_{AB} = V_{AC} + V_{CD} + V_{DA}$$

$$= 2(i_2 + i_3) + (0.8)(-7.5 i_2) + 8(i_2 + i_3)$$


$$= 25 - 72 + 100 = 53 \text{ V}$$

$$\text{Power} = V_{AB} (0.5) = \boxed{26.5 \text{ Watts}}$$

↑  
 $i_3$

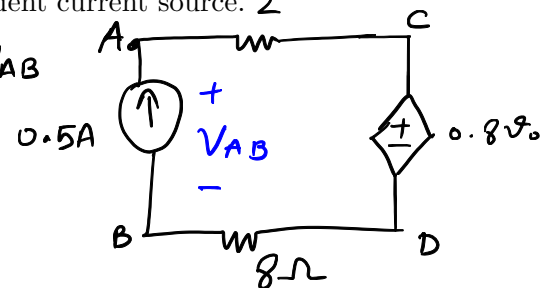

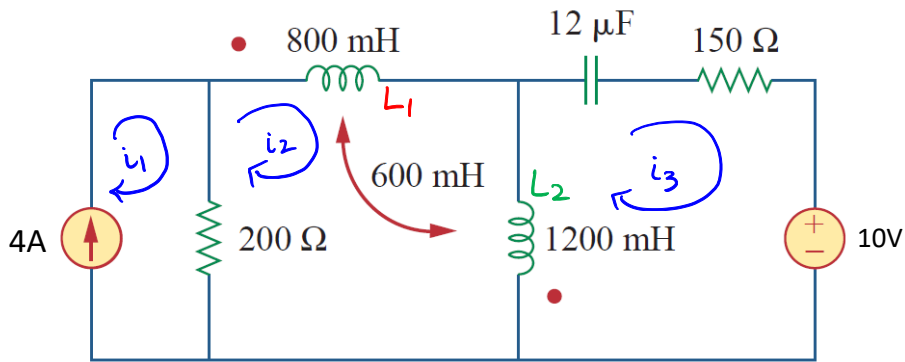**Problem 5.** (10 pts) Consider the circuit given below.



(a) (5 pts) Formulate the network equations using loop analysis.

Loop 1:

$$i_1 = 4A$$

Loop 2:


$$0.8 \frac{di_2}{dt} + 1.2 \frac{d(i_2 - i_3)}{dt} + 200(i_2 - i_1)$$

$$+ 0.6 \frac{d(i_3 - i_2)}{dt} \quad - 0.6 \frac{di_2}{dt}$$


Effect on  $L_1$  due to current  $(i_3 - i_2)$  entering dot of  $L_2$ .  
 Effect on  $L_2$  due to  $i_2$  current entering dot of  $L_1$ .

$$\text{Loop 3: } \frac{1}{12\mu} \int i_3 dt + 150i_3 + 1.2 \frac{d(i_3 - i_2)}{dt} + 0.6 \frac{di_2}{dt} = -10$$

(b) (4 pts) Find an equivalent circuit where each coupled inductor is replaced with an uncoupled inductor and a controlled source. Draw the equivalent circuit.

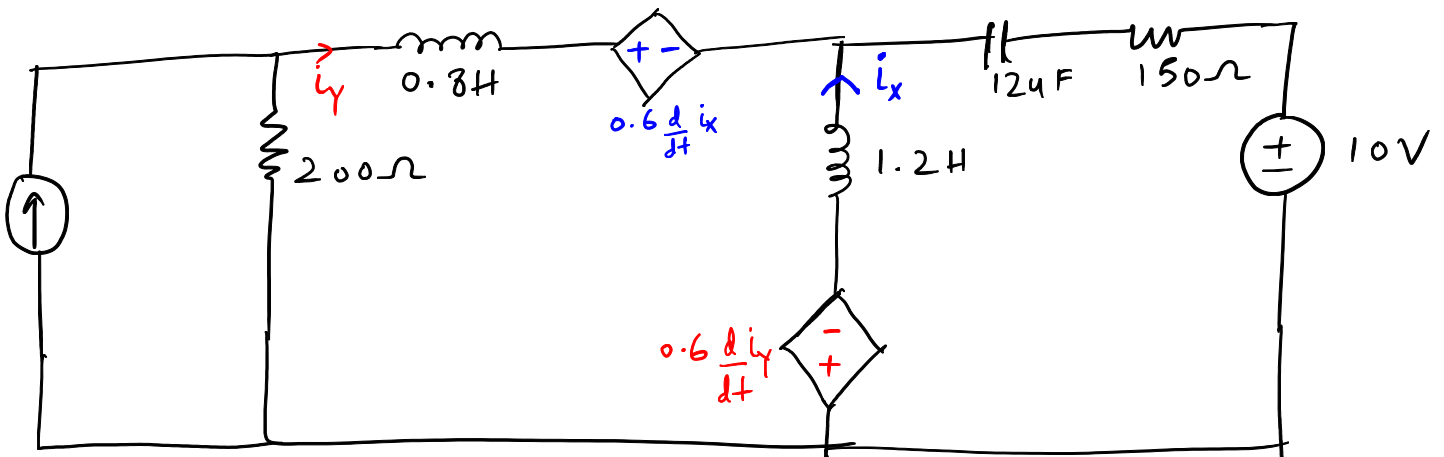

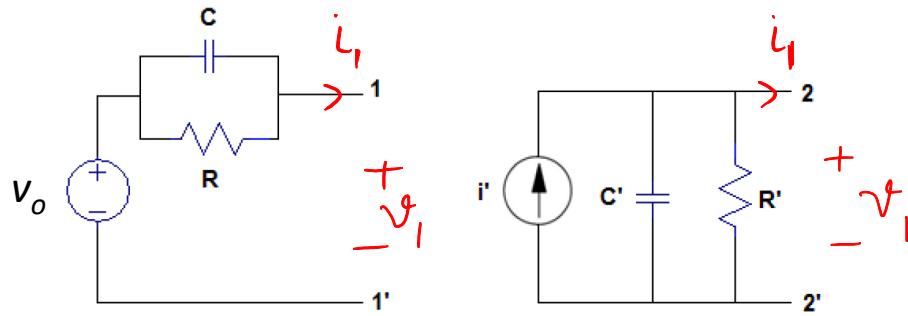**Problem 6. (6 pts)** Find the values of  $i'$ ,  $R'$  and  $C'$  in terms of  $R$ ,  $C$  and  $v_o$  such that the networks shown below are equivalent at terminals 11 and 22.



$$i_1 = \frac{v_o - v_1}{R} + C \frac{d}{dt} (v_o - v_1)$$

$$i_1 = \left( \frac{1}{R} + C \frac{d}{dt} \right) v_o - \frac{v_1}{R} - C \frac{d}{dt} v_1 \quad \text{--- (1)}$$

$$i_1 = i' - \frac{v_1}{R'} - C' \frac{dv_1}{dt} \quad \text{--- (2)}$$

By comparing (1) and (2)

$$i' = \frac{v_o}{R} + C \frac{dv_o}{dt}$$


$$R' = R$$

$$C' = C$$



## Part 3: Additional Analysis Techniques

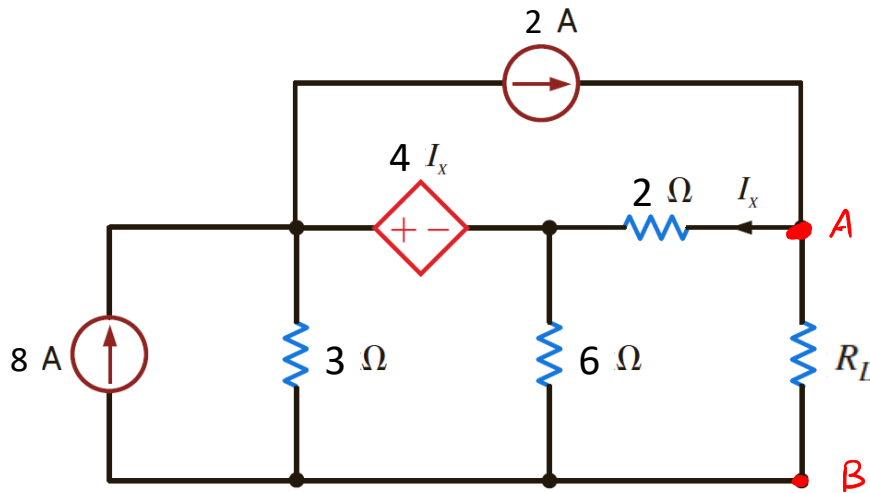**Problem 7.** (12 pts) For the circuit given below, determine the value of  $R_L$  for maximum power transfer to  $R_L$  using Thevenin's Theorem.




Find Thevenin Equivalent across AB:-

$V_{th}$ :  $i_1 = 8A$ ,  $i_2 = 2A = i_x$

Loop 3:  $9i_3 - 3i_1 + 4i_x = 0$

$\Rightarrow 9i_3 - 24 + 8 = 0 \Rightarrow i_3 = \frac{16A}{9}$

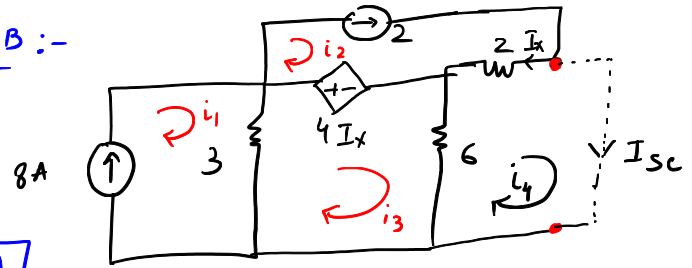$V_{th} = V_{AB} = 2i_2 + 6i_3 = 4 + \frac{32}{3} = \frac{44}{3} V$




$I_{sc}$ :  $i_1 = 8A$ ,  $i_2 = 2A$ ,  $i_x = i_2 - i_4$ ,  $i_4 = I_{sc}$

Loop 3:  $9i_3 - 3i_1 + 4i_x - 6i_4 = 0 \Rightarrow 9i_3 - 24 + 8 - 10i_4 = 0 \Rightarrow 9i_3 - 10i_4 = 16$

Loop 4:  $2(i_4 - i_2) + 6(i_4 - i_3) = 0 \Rightarrow 8i_4 - 6i_3 = 4 \Rightarrow 4i_4 - 3i_3 = 2 \Rightarrow i_4 = 11A = I_{sc}$

$R_{th} = \frac{V_{th}}{I_{sc}} = \frac{4}{3} \Omega$

Equivalent Circuit

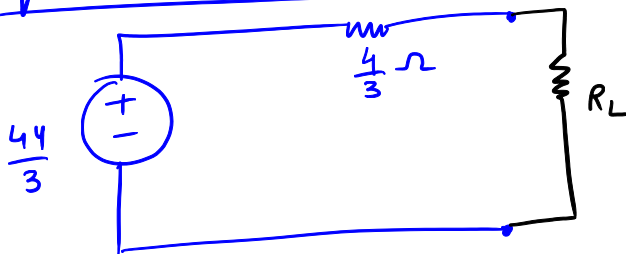


For max. power transfer:

$R_L = R_{th} = \frac{4}{3} \Omega$

Alternatively; we can use test-source approach method.

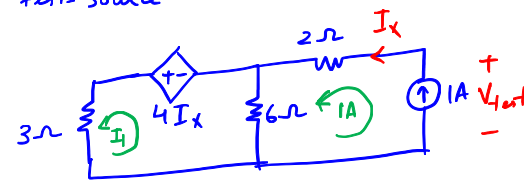- \* Switch off sources
- \* Apply 1A current source




$i_x = 1A$   
 Loop 1:  $9i_1 - 4i_x - 6(1) = 0$   
 $\Rightarrow i_1 = \frac{10A}{9}$


$V_{test} = (2)(1) + 6(1 - \frac{10}{9}) = 2 - \frac{2}{3} = \frac{4}{3} V$

$\Rightarrow R_{th} = \frac{V_{test}}{1} = \frac{4}{3} \Omega$

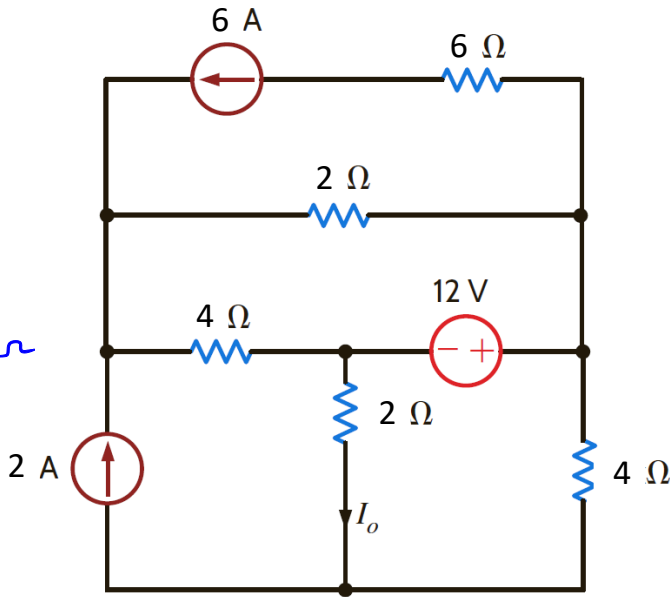**Problem 8.** (9 pts) Determine  $I_o$  using the superposition theorem (principle) for the circuit given below.




only 12V ON

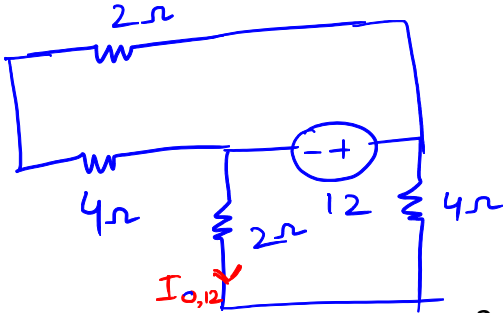


$$I_{o,12} = \frac{-12}{6} = \underline{\underline{-2A}}$$


ONLY 6A ON :

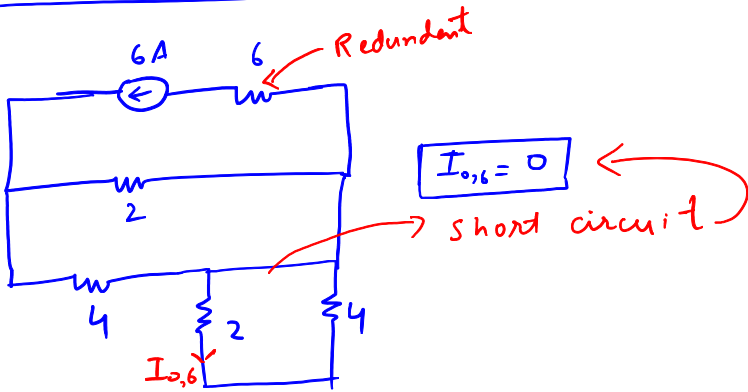

ONLY 2A ON

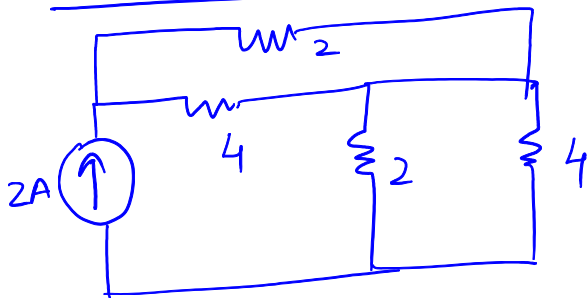

$\equiv$

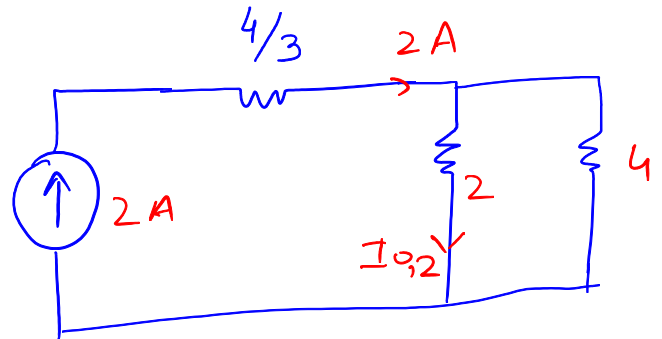


$$\Rightarrow I_o = \frac{4}{6} \times 2 = \underline{\underline{\frac{4}{3}A}}$$

$$I_o = I_{o,12} + I_{o,6} + I_{o,2}$$

$$= -2 + \frac{4}{3} = \underline{\underline{-\frac{2}{3}A}}$$

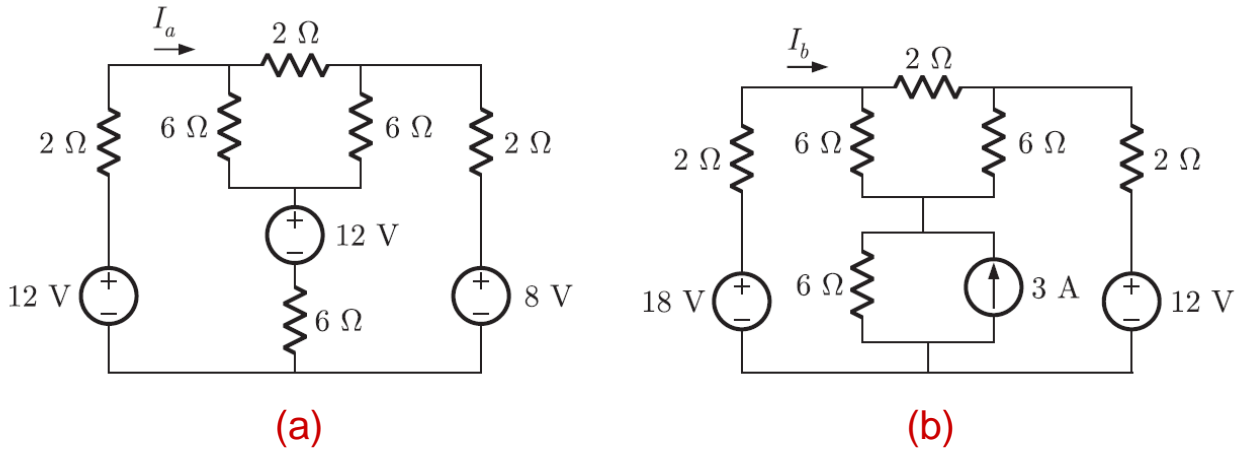**Problem 9.** (4 pts) Given the following two circuits, determine the relation between  $I_a$  and  $I_b$ . You must provide justification to support your answer. (Hint: Use the concept of linearity.)




This was just a piece of cake!



Since the sources in (b) have values (1.5) times the sources in (a); linearity implies  $I_b = 1.5 I_a$  (Scaling + Superposition)

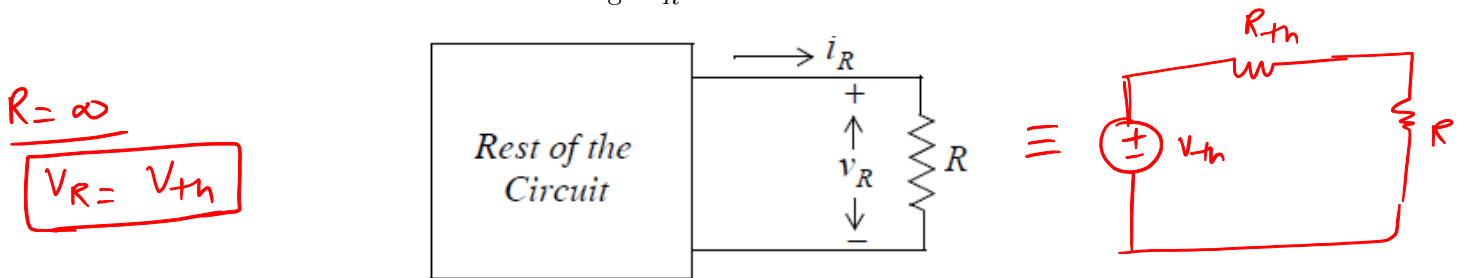**Problem 10.** (5 pts) Consider the network shown below, where the rest of the circuit is pure resistive in nature. The voltage  $V_R = 6V$  for  $R = 4\Omega$  and the current  $i_R = 2.4A$  for  $R = 0\Omega$ . Determine the voltage  $V_R$  in volts when  $R = \infty$ .



$R = \infty$   
 $V_R = V_{th}$

$R = 4$   $V_R = \frac{4}{R_{th} + 4} V_{th} = 6 \Rightarrow 6R_{th} + 24 = 4V_{th}$

$R = 0$   $i_R = \frac{V_{th}}{R_{th}} = 2.4 \Rightarrow V_{th} = 2.4 R_{th} \Rightarrow R_{th} = \frac{V_{th}}{2.4}$

$\Rightarrow 2.5 V_{th} + 24 = 4V_{th} \Rightarrow V_{th} = 16V$