

Department of Electrical Engineering
School of Science and Engineering

EE240 Circuits I - Fall 2020

ASSIGNMENT 5 – SOLUTIONS

Q 1. Analyse the circuit at $t = 0^-$,

$$V_c(0^-) = 10V$$

Since capacitor does not allow instantaneous change in voltage,

$$V_c(0^+) = 10V$$

Form a differential equation,

$$6i(t) + \frac{1}{C} \int i(t) dt = 40e^{-t}u(t)$$

Taking its derivative,

$$\frac{di(t)}{dt} + \frac{1}{0.331 \cdot 6} i(t) = -\frac{40}{6} e^{-t} u(t)$$

The forms of the particular and the complementary solution will be:

Complementary solution $i_c(t)$ (form a characteristic equation):

$$s + 0.5 = 0$$

$$s = -0.5$$

Hence,

$$i_c(t) = K_1 e^{-0.5t}$$

Particular solution $i_p(t)$ (will have the form of the excitation):

$$i_p(t) = K_2 e^{-t}$$

Lets start by finding the particular solution, substitute $i_p(t)$ in the differential equation,

$$\begin{aligned} \frac{di_p(t)}{dt} + 0.5i_p(t) &= \frac{40}{6} e^{-t} \\ -K_2 e^{-t} + 0.5K_2 e^{-t} &= \frac{-40}{6} e^{-t} u(t) \\ -0.5K_2 e^{-t} &= \frac{-40}{6} e^{-t} u(t) \\ K_2 &= 13.33 \end{aligned}$$

So,

$$i(t) = K_1 e^{-0.5t} + 13.33e^{-t}$$

Using the initial equation we get that,

$$V_c(t) = 40e^{-t} - 6i(t)$$

Substitute the expression for $i(t)$,

$$V_c(t) = 40e^{-t} - 6(K_1 e^{-0.5t} + 13.33e^{-t})$$

Solve at $t = 0^+$,

$$K_1 = -8.33$$

Finally,

$$i(t) = -8.33e^{-0.5t} + 13.33e^{-t}$$

Q 2. (a) Nodal analysis,

$$C \frac{dV_c}{dt} + \frac{V_c}{R} + \frac{1}{L} \int V_c dt = 0$$

For $\frac{dV_c(0^+)}{dt}$ evaluate equation at $t = 0^+$,


$$\begin{aligned} \frac{dV_c(0^+)}{dt} &= -\frac{V_c}{RC} - \frac{I_L}{C} \\ &= \frac{-12.4}{24 \cdot 0.5} - \frac{250m}{0.5} = -1.6V_s^{-1} \end{aligned}$$

(b) Derivate the equation to get,

$$\begin{aligned} C \frac{d^2V_c}{dt^2} + \frac{1}{R} \frac{dV_c}{dt} + \frac{V_c}{L} &= 0 \\ \frac{d^2V_c}{dt^2} + \frac{1}{RC} \frac{dV_c}{dt} + \frac{V_c}{LC} &= 0 \\ \frac{d^2V_c}{dt^2} + \frac{1}{12} \frac{dV_c}{dt} + \frac{1}{5} V_c &= 0 \end{aligned}$$

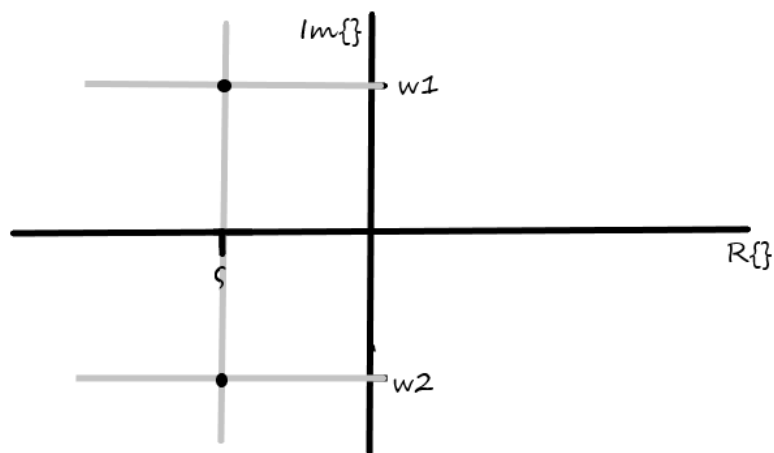(c) Form a characteristic equation,

$$\begin{aligned} s^2 + \frac{1}{12}s + \frac{1}{5} &= 0 \\ s_1 &= -0.04 + 0.44j \\ s_2 &= -0.04 - 0.44j \end{aligned}$$



(d)

(e)

$$V_c(t) = (K_1 \cos(\omega t) + K_2 \sin(\omega t))e^{\sigma t}$$

Where,

$$\sigma = -0.04$$

$$\omega = 0.44$$

(σ signifies the decay and ω is the frequency of oscillation)

$$V_c(t) = e^{-0.04t}(K_1 \cos(0.44t) + K_2 \sin(0.44t))$$

$$\frac{dV_c(t)}{dt} = -0.04e^{-0.04t}(K_1 \cos(0.44t) + K_2 \sin(0.44t))$$


$$+ e^{-0.04t}(-0.44K_1 \sin(0.44t) + 0.44K_2 \cos(0.44t))$$

Substitute $V_c(0^+)$ and $\frac{dV_c(0^+)}{dt}$ when evaluating these equations at $t = 0^+$,

$$K_1 = 12.9$$

$$K_2 = -2.5$$

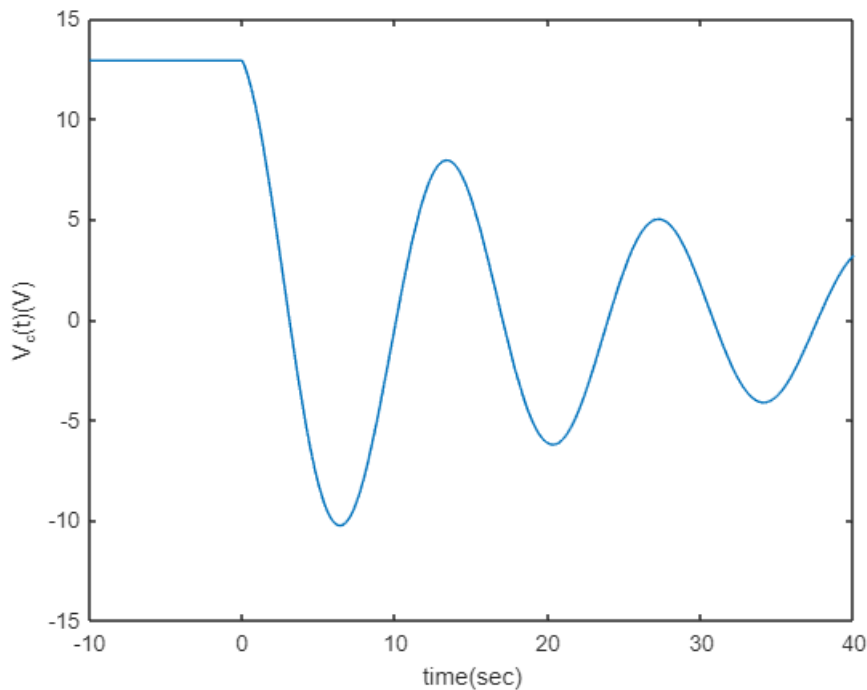
$$V_c(t) = \begin{cases} e^{-0.04t}(12.9 \cos(0.44t) - 2.5 \sin(0.44t))V & t \geq 0 \\ 12.9V & t < 0 \end{cases}$$



MATLAB code:

```
syms t
y = piecewise(t < 0, 12.9, t >= 0, exp(-0.04.*t).*(12.9.*cos(0.44.*t)) - 2.5.*sin(0.44.*t))
fplot(y)
axis([-10 40 -15 +15])
xlabel('time(sec)')
ylabel('V_c(t)(V)')
```

Q 3. (a) At $t = 0^-$,

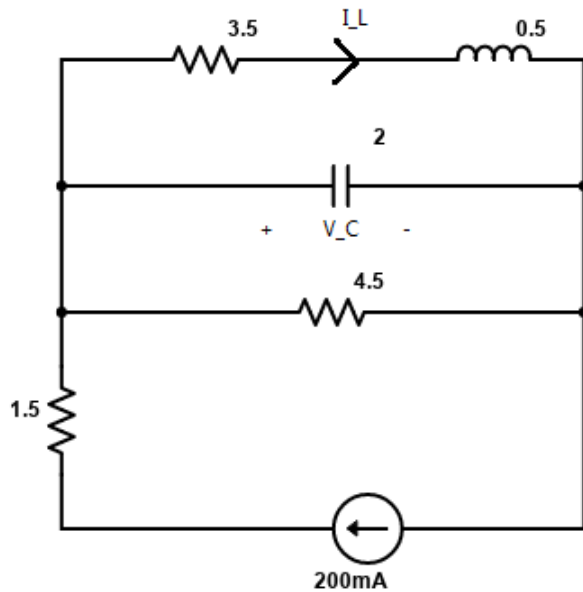

For V_c , notice that the capacitor is in parallel with 3.5Ω and 4.5Ω resistors. The 1.5Ω resistor is redundant as it is in series with the current source.

$$V_c = IR$$

$$(200 \cdot 10^{-3}) \cdot \frac{3.5 \cdot 4.5}{8} = 0.39V$$

For I_L , use current divider or simply ohm's law,


$$V_c = I_L R$$

$$I_L = \frac{V_c}{R} = \frac{0.39}{3.5} = 0.11A$$

So,

$$V_c(0^-) = 0.39V, \quad I_L(0^-) = 0.11A$$

(b) At $t = 0^+$,

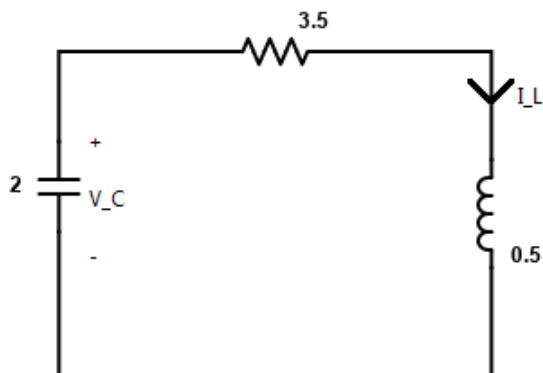

Loop equation:

$$-\frac{1}{C} \int I_L dt + I_L R + L \frac{dI_L}{dt} = 0 \quad (1)$$

For $\frac{dI_L(0^+)}{dt}$,

Evaluate (1) at 0^+ , (note that $V_c(0^-) = V_c(0^+)$ and $I_L(0^-) = I_L(0^+)$),

$$-0.39 + (0.11 \cdot 3.5) + 0.5 \frac{dI_L(0^+)}{dt} = 0$$

$$\frac{dI_L(0^+)}{dt} = 0.01As^{-1}$$

(c) Take derivative of (1),

$$\frac{I_L}{C} + R \frac{dI_L}{dt} + L \frac{d^2 I_L}{dt^2} = 0$$

$$\frac{d^2 I_L}{dt^2} + 7 \frac{dI_L}{dt} + I_L = 0 \quad (2)$$

$$s^2 + 7s + 1 = 0$$

$$s_1 = -0.15$$

$$s_2 = -6.85$$

Notice that the roots are real and distinct (Over-damped),

$$I_L(t) = K_1 e^{-0.15t} + K_2 e^{-6.85t}$$


Use $I_L(0^+)$ and $\frac{dI_L(0^+)}{dt}$ to find K_1 and K_2 ,

$$K_1 = 0.11 \quad K_2 = -0.004$$

So

$$I_L(t) = \begin{cases} 0.11e^{-0.15t} - 0.004e^{-6.85t} \text{ A} & 0 \leq t < 4 \\ 0.06 \text{ A} & t = 4 \end{cases}$$

(d) For $t > 4$

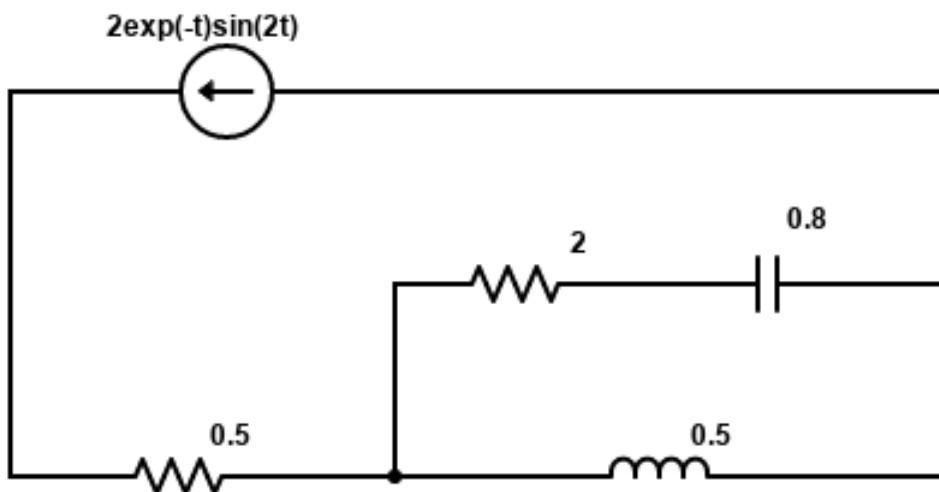

0.5Ω is redundant as it is in series to the current source.

Loop equation:

$$0.5 \frac{dI_L}{dt^2} + 2(I_L - 2e^{-t} \sin(2t)) + \frac{1}{0.8} \int (I_L - 2e^{-t} \sin(2t)) = 0 \quad (3)$$

$$\frac{d^2 I_L}{dt^2} + 4 \frac{dI_L}{dt} + 2.5 I_L = 3e^{-t} \sin(2t) - 16e^{-t} \cos(2t) \quad (4)$$

For $\frac{dI_L(4^+)}{dt}$, Evaluate (3) at $t=4$,

$$\begin{aligned} \frac{dI_L(4^+)}{dt} &= 2(-2I_L(4) + 4e^{-4} \sin(8) + 0) \\ &= -0.22 \text{ A s}^{-1} \end{aligned}$$

(e) Refer to Equation (4)

(f)

$$y_p(t) = [A \cos(2t) + B \sin(2t)]e^{-t}$$

$$\frac{dy_p(t)}{dt} = e^{-t}[-2A \sin(2t) + 2B \cos(2t)] - e^{-t}[A \cos(2t) + B \sin(2t)]$$

$$\frac{d^2y_p(t)}{dt^2} = 4Ae^{-t} \sin(2t) - 3Ae^{-t} \cos(2t) - 4Be^{-t} \cos(2t) - 3Be^{-t} \sin(2t)$$

Substitute in (4),

$$\begin{aligned} \sin(2t)e^{-t}[4A - 3B - 8A - 4B + 2.5B] + \cos(2t)e^{-t}[-3A - 4B + 8B - 4A + 2.5A] \\ = 3e^{-t} \sin(2t) - 16e^{-t} \cos(2t) \end{aligned}$$

So,

$$A = 1.66$$

$$B = -2.14$$

$$I_p(t) = [1.66 \cos(2t) - 2.14 \sin(2t)]e^{-t}$$

(g)

$$s^2 + 4s + 2.5 = 0$$

$$s_1 = -0.78$$

$$s_2 = -3.22$$

Roots are real and distinct(over-damped).

$$I_c(t) = K_1 e^{-0.78t} + K_2 e^{-3.22t}$$

Combine the complementary and particular solution to find K_1 and K_2 ,

$$I_L(t) = I_c(t) + I_p(t)$$

$$I_L(t) = K_1 e^{-0.78t} + K_2 e^{-3.22t} + [1.66 \cos(2t) - 2.14 \sin(2t)] - e^{-t}[1.66 \cos(2t) - 2.14 \sin(2t)]$$

Use $I_L(4^+)$ and $\frac{dI_L(4^+)}{dt}$ to find K_1 and K_2 ,

$$K_1 = -0.03$$


$$K_2 = 14455$$

$$I_c(t) = -0.03e^{-0.78t} + 14455e^{-3.22t} A$$

(h)

$$I_c(t) = \begin{cases} 0.11A & t < 0 \\ 0.11e^{-0.15t} - 0.004e^{-6.85t} A & 0 \leq t \leq 4 \\ -0.03e^{-0.78t} + 14455e^{-3.22t} + [1.66 \cos(2t) - 2.14 \sin(2t)]e^{-t} A & t > 4 \end{cases}$$

Plot:

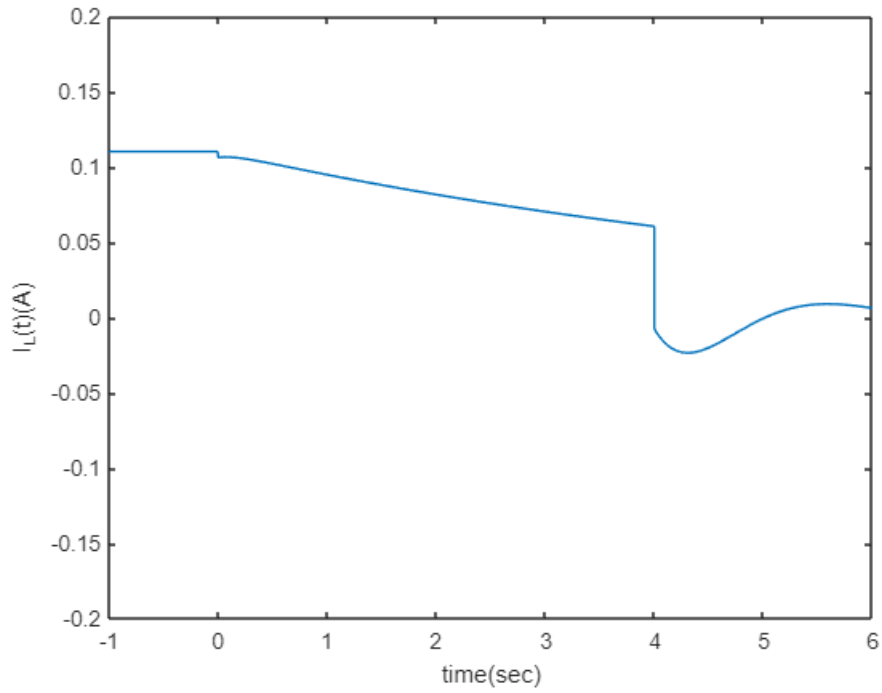

Matlab code:

```

syms t
y = piecewise(t < 0, 0.11, t <= 4, 0.11 * exp(-0.15 * t) - 0.004 * exp(-6.85 * t), t > 4,
-0.03 * exp(-0.78 * t) + 14455 * exp(-3.22 * t) + (1.66 * cos(2 * t) - 2.14 * sin(2 * t)) * exp(-t))
fplot(y)
axis([-1 6 -0.2 +0.2])
xlabel('time(sec)')
ylabel('I_L(t)(A)')

```


Q 4. Information given:

$$v(0) = 10V$$

$$i(0) = 0$$

$$L = 0.1H$$

$$C = 0.01F$$

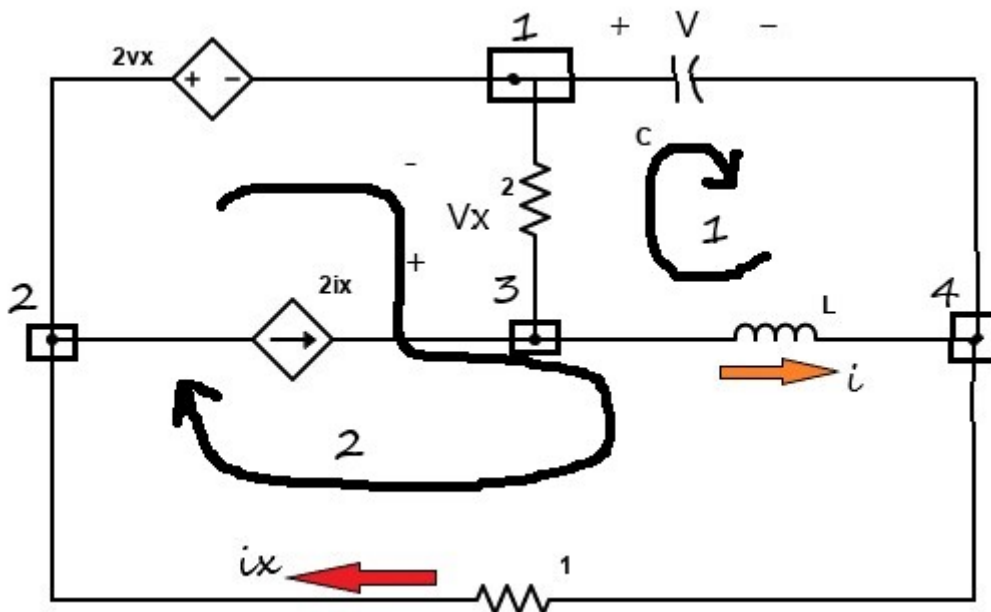

Using KCL, write currents at node 2:

$$i_x + i_y = 2i_x$$

$$i_y = i_x$$

Write nodal equation at node 1:

$$i_c - \frac{v_x}{2} + i_y = 0$$

$$C \frac{dv}{dt} - \frac{v_x}{2} + i_x = 0$$

$$0.01 \frac{dv}{dt} - \frac{v_x}{2} + i_x = 0 \rightarrow (1)$$

Write nodal equation at node 3:

$$i - 2i_x + \frac{v_x}{2} = 0$$

$$2i - 4i_x + v_x = 0$$

$$v_x = 4i_x - 2i \rightarrow (2)$$

Substitute (2) in (1),

$$0.01 \frac{dv}{dt} + i - i_x = 0 \rightarrow (3)$$

Write KVL around loop 1:

$$v - v_L + v_x = 0$$

$$v - L \frac{di}{dt} + 4i_x - 2i = 0$$

$$\frac{di}{dt} - 10v - 40i_x + 20i = 0 \rightarrow (4)$$

Write KVL around loop 2:

$$2v_x - v_x + v_L + 1i_x = 0$$

$$v_x + L \frac{di}{dt} + i_x = 0$$

$$4i_x - 2i + 0.1 \frac{di}{dt} + i_x = 0$$

$$5i_x - 2i + 0.1 \frac{di}{dt} = 0$$

Solving for i_x ,

$$i_x = 0.4i - 0.02 \frac{di}{dt} \rightarrow (5)$$

Put i_x from (5) in (3),

$$0.01 \frac{dv}{dt} + i - (0.4i - 0.02 \frac{di}{dt}) = 0$$

$$\frac{dv}{dt} + 60i + 2 \frac{di}{dt} = 0 \rightarrow (6)$$

Put i_x from (5) in (4),

$$\frac{di}{dt} - 10v - 40(0.4i - 0.02 \frac{di}{dt}) + 20i = 0$$

$$0.18 \frac{di}{dt} + 0.4i = v \rightarrow (7)$$

Put v from equation (7) in (6),

$$\begin{aligned} \frac{d}{dt}[0.18 \frac{di}{dt} + 0.4i] + 60i + 2 \frac{di}{dt} &= 0 \\ 0.18 \frac{d^2i}{dt^2} + 0.4 \frac{di}{dt} + 60i + 2 \frac{di}{dt} &= 0 \\ \frac{d^2i}{dt^2} + 13.33 \frac{di}{dt} + 333.33i &= 0 \rightarrow (8) \end{aligned}$$

This is the differential equation for current.

Characteristic equation:

$$s^2 + 13.33s + 333.33 = 0$$

The roots of this equation are:

$$s_{1,2} = -6.67 \pm j17$$

From this, $\alpha = 6.67$ $\omega_d = 17$. so,

$$i_c = e^{-6.67t}[A \cos(17t) + B \sin(17t)]$$

Since the equation is homogeneous and has no forcing function, the particular solution, $i_p=0$

The total response is:

$$\begin{aligned} i(t) &= i_c + i_p \\ i(t) &= e^{-6.67t}[A \cos(17t) + B \sin(17t)] \end{aligned}$$

When $t=0$,

$$\begin{aligned} i(0) &= e^0[A \cos(0) + B \sin(0)] \\ A &= 0 \end{aligned}$$

Now total response is:

$$i(t) = e^{-6.67t} B \sin(17t)$$

Differentiate both sides:

$$\frac{di(t)}{dt} = -6.67e^{-6.67t} B \sin(17t) + 17Be^{-6.67t} B \cos(17t) \rightarrow (9)$$

From Equation (7), find $\frac{di(0)}{dt}$:

$$\begin{aligned} 0.18 \frac{di(0)}{dt} + 0.4i(0) &= v(0) \\ 0.18 \frac{di(0)}{dt} + 0.4(0) &= 10 \\ \frac{di(0)}{dt} &= 55.56 \end{aligned}$$

Put this in (9),

$$\begin{aligned} \frac{di(0)}{dt} &= -6.67e^{-6.67(0)} B \sin(17(0)) + 17Be^{-6.67(0)} B \cos(17(0)) \\ \frac{di(0)}{dt} &= 17B \\ B &= 3.27 \end{aligned}$$

Finally, the equation for the inductor's current is:

$$i(t) = 3.27e^{-6.67t} \sin(17t)$$

Now, find out v(t). From equation (7):

$$v(t) = 0.18 \frac{di}{dt} + 0.4i$$

Find di/dt from $i(t)$:

$$\begin{aligned}\frac{di(t)}{dt}i &= 3.27(-6.67)e^{-6.67t}\sin(17t) + 3.2717e^{-6.67t}\cos(17t) \\ &= -21.82e^{-6.67t}\sin(17t) + 55.59e^{-6.67t}\cos(17t)\end{aligned}$$

Now solve for $v(t)$:

$$\begin{aligned}v(t) &= 0.18[-21.82e^{-6.67t}\sin(17t) + 55.59e^{-6.67t}\cos(17t)] + 0.4[3.27e^{-6.67t}\sin(17t)] \\ v(t) &= e^{-6.67t}(10\cos(17t) - 2.62\sin(17t))V\end{aligned}$$