

**LAHORE UNIVERSITY OF MANAGEMENT SCIENCES**  
**Department of Electrical Engineering**


**EE240 Circuits I**  
**Quiz 01**

**Total Marks:** 10

**Time Duration:** 20 minutes


**Question 1** (10 marks)

- (a) [4 marks] The current  $i_c(t)$  through the capacitor of capacitance  $\frac{1}{4}F$  is shown in Figure 1 below. Determine the voltage across the capacitor. You must show working to support your answer. Also plot the voltage for  $1 \leq t \leq 5$ .

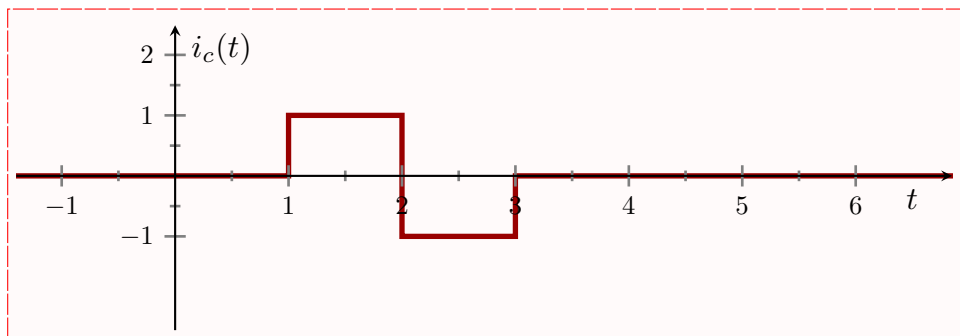

**Figure 1:** Current through the Capacitor.

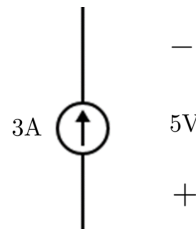- (b) [1 mark] Plot  $i - v$  characteristics of the ideal DC current source.  
 (c) [2 marks] The voltage across 3A ideal current source connected in a circuit is indicated in the figure below. Determine the power being supplied by the current source.



- (d) [3 marks] Consider the circuit given below. The switch is initially opened and is closed at  $t = 0$ . Plot  $v(t)$ ,  $i_R(t)$  and  $i_C(t)$  for all times.

