

EE240 – Circuits I  
**Final Examination (Fall 2020)**

December 21, 2020


12:30 pm–03:30 pm

---

**INSTRUCTIONS:**


- We require you to solve the exam in a single time-slot of two hours and thirty minutes without any external or electronic assistance.
- We encourage you to solve the exam on A4 paper, use new sheet for each question and write sheet number on every sheet.
- The exam is closed book and notes. You are allowed to have two A4 sheet with you with hand-written notes on both sides. Calculators can be used.
- For the sake of completeness, we require you to write the following statement on your first page of submission: *I commit myself to uphold the highest standards of (academic) integrity.*
- Reading time: 10 minutes
- Writing time: 2 hours and 30 minutes
- Submission time: 20 minutes
- The exam consists of 6 problems worth a total of 90 points.

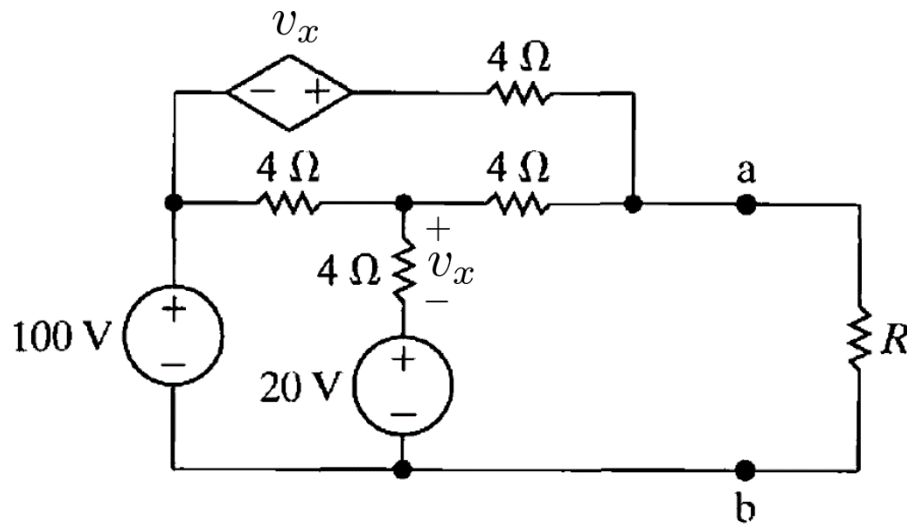**Problem 1.** (15 pts) The variable resistor  $R$  in the circuit given below is adjusted until it absorbs the maximum power from the circuit.




- (a) (6 pts) Calculate the value of  $R$  for maximum power.
- (b) (6 pts) Determine the maximum power absorbed by  $R$ .
- (c) (3 pts) Determine the Norton equivalent of the circuit at terminals a-b.

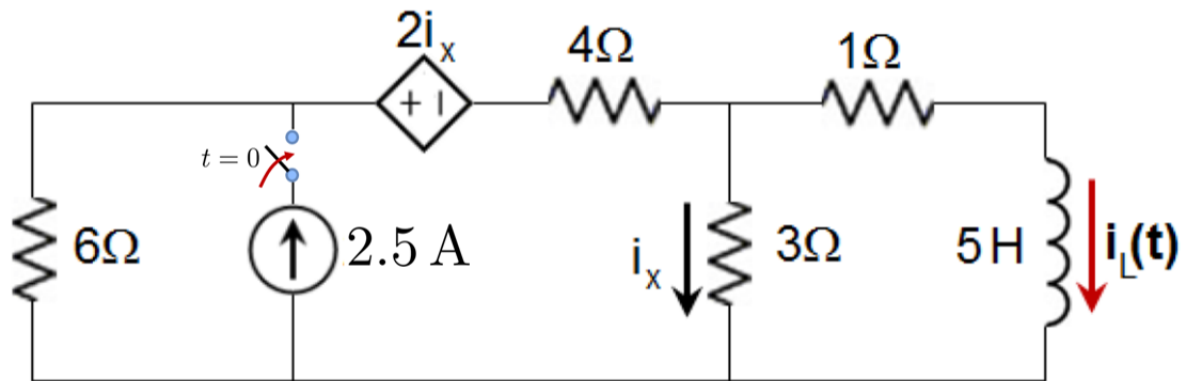**Problem 2. (15 pts)** The circuit given below is in steady state with switch in open state. The switch is closed at  $t = 0$ .



- (2 pts)** Determine the current  $i_L(t)$  at  $t = 0^-$ .
- (1 pts)** Determine the current  $i_L(t)$  at  $t = 0^+$ .
- (5 pts)** Determine the current  $i_L(t)$  at  $t = \infty$
- (7 pts)** Using the results of the previous parts, or otherwise, determine the current  $i_L(t)$  for all times and plot it.

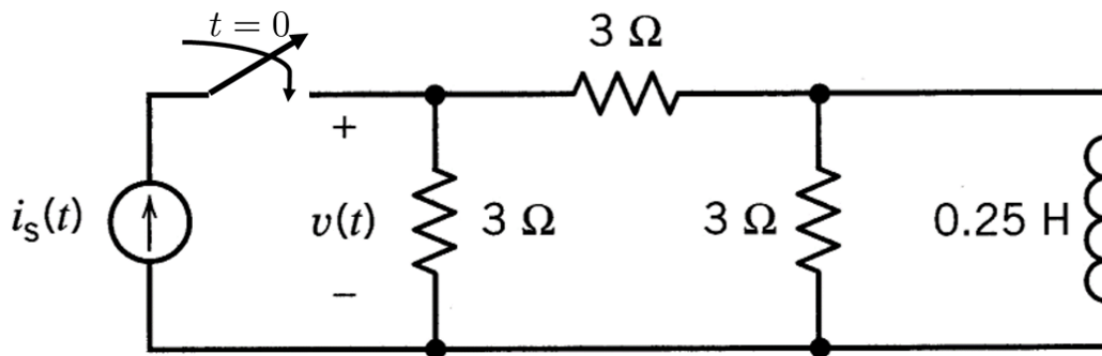
**Problem 3.** (15 pts) Consider the circuit given below. The circuit is in steady state and the the switch is closed at  $t = 0$ .



- (4 pts) For a circuit for  $t > 0$ , form an equivalent series RL circuit containing one source, one resistor and one inductor. Ignore  $v(t)$  indicated in the circuit. (Hint: You may use source transformation or Thevenin equivalent approach.)
- (8 pts) For  $i_s(t) = e^{-t} \cos t$ , determine the current through the inductor for  $t \geq 0$ . Ignore  $v(t)$  indicated in the circuit.
- (3 pts) Using the result of previous part or otherwise, determine the voltage  $v(t)$  indicated in the circuit for  $t \geq 0$ .


**Problem 4. (10 pts)** In the circuit below, we have  $R_2 = R_3 = 20\Omega$ . We assume that the steady state is reached with switch  $K$  open. At time  $t = 0$ , the switch is closed. Determine values of resistance  $R_1$ , inductance  $L$ , capacitance  $C$  and voltage  $V$  of the voltage source using the following information.

- $i_1(0^+) = 2 \text{ A}$
- $i_2(0^+) = 1 \text{ A}$
- $\frac{di_1}{dt}(0^+) = 40 \text{ A/s}$
- $\frac{di_2}{dt}(0^+) = -\frac{1}{2} \text{ A/s}$

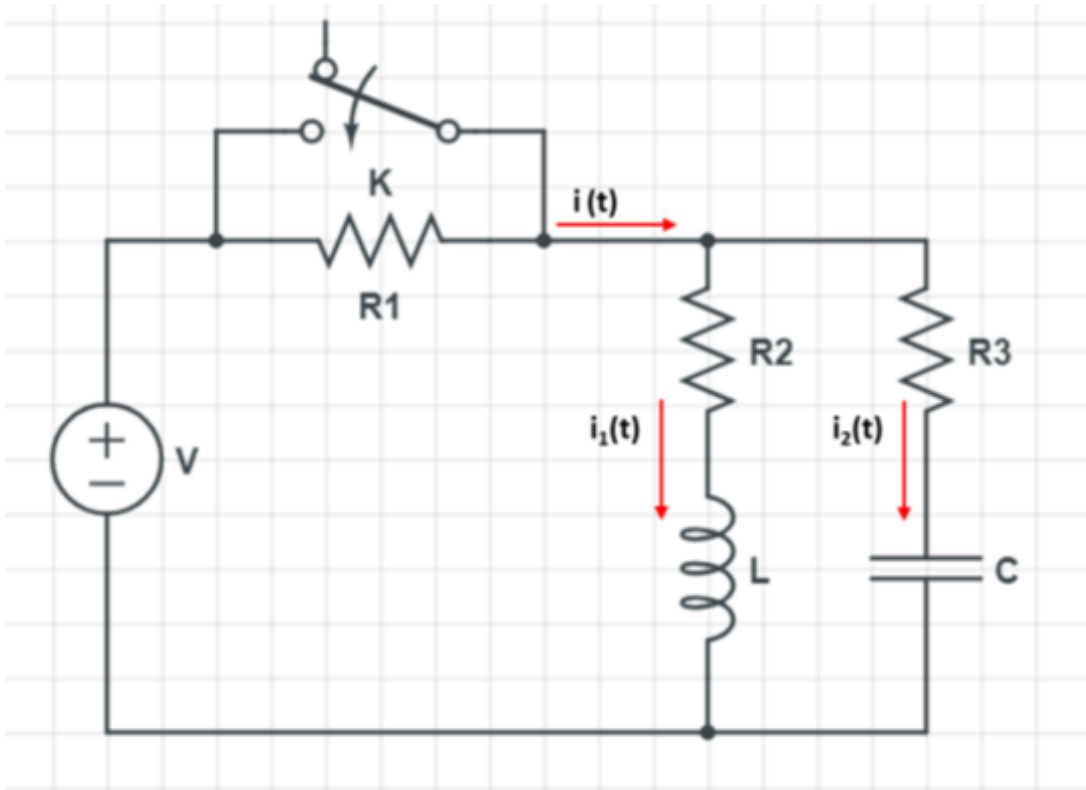

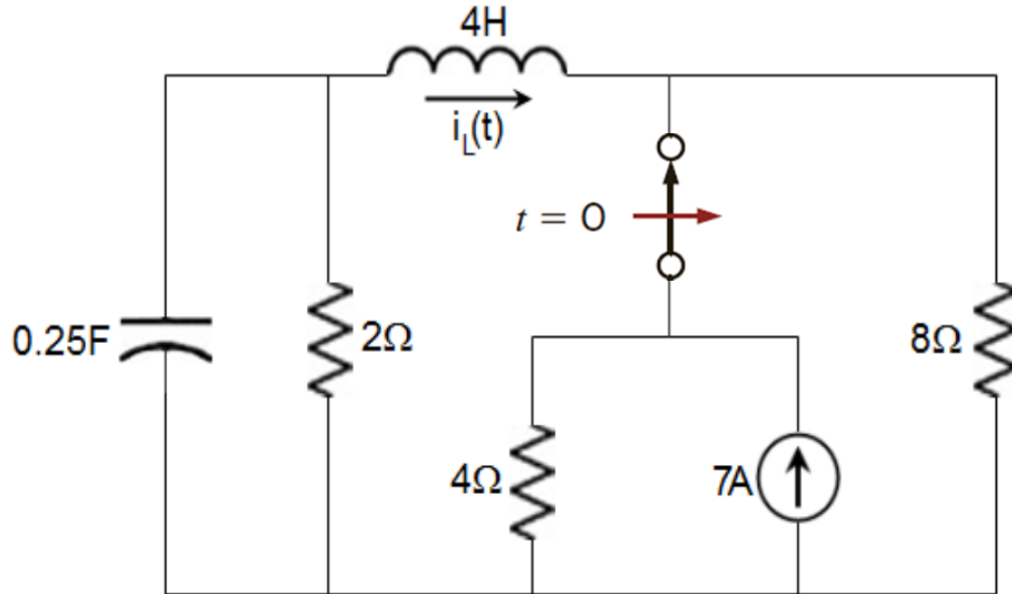**Problem 5. (20 pts)**


Consider the circuit shown below. The circuit is in steady state with switch in closed state. The switch is opened at  $t = 0$ .



- (6 pts) Determine  $i_L(t)$  and  $\frac{di_L}{dt}$  at  $t = 0^+$ .
- (5 pts) Formulate the second-order differential equation describing the current  $i_L(t)$  for  $t \geq 0$ .
- (2 pts) Determine the damping ratio  $\zeta$  and natural frequency  $\omega_n$  of the circuit after the switch is closed.
- (7 pts) Determine and plot (with labels)  $i_L(t)$  for all times.

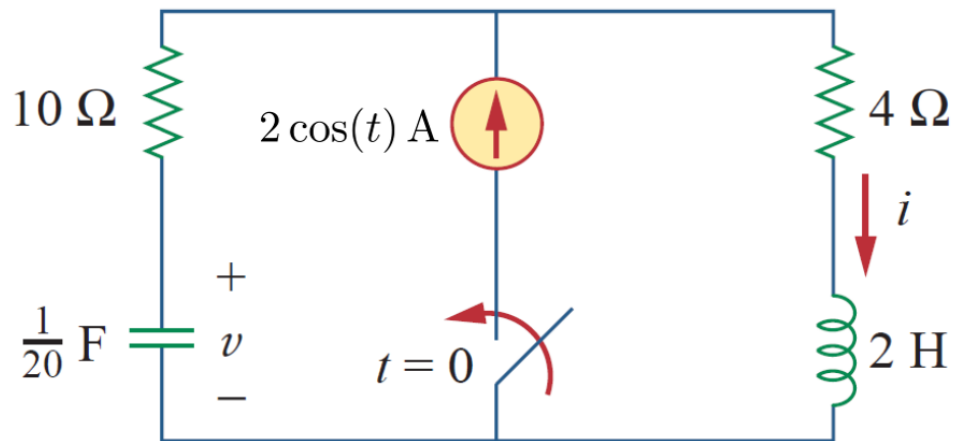**Problem 6. (15 pts)**

The switch in the following circuit is closed at  $t = 0$ .



- (5 pts) Formulate the second order differential equation describing the voltage  $v(t)$  after the switch is closed.
- (8 pts) Determine  $v(t)$  for all times.
- (2 pts) Using the result of previous part or otherwise, determine  $i(t)$  for all times.