

EE240 – Circuits I  
**Mid Examination (Fall 2020)**

November 07, 2020

02:00 pm–04:30 pm

---

**INSTRUCTIONS:**

- We require you to solve the exam in a single time-slot of two hours without any external or electronic assistance.
- We encourage you to solve the exam on A4 paper, use new sheet for each question and write sheet number on every sheet.
- Clearly outline all your steps in order to obtain any partial credit.
- The exam is closed book and notes. You are allowed to have one A4 sheet with you with hand-written notes on both sides. Calculators can be used.
- For the sake of completeness, we require you to write the following statement on your first page of submission: *I commit myself to uphold the highest standards of (academic) integrity.*
- If you are ready, please proceed to the next page.


**Mapping between exam parts and course learning outcomes (CLOs)**

- Part 1: R, L, C Basics, Sources and I-V Characteristics (CLO1)
- Part 2: Network Topology, Network Equations and Kirchhoff's Laws (CLO2)
- Part 3: Additional Analysis Techniques (CLO3)


## Part 1: R, L, C Basics, Sources and I-V Characteristics

### Problem 1. (10 pts)

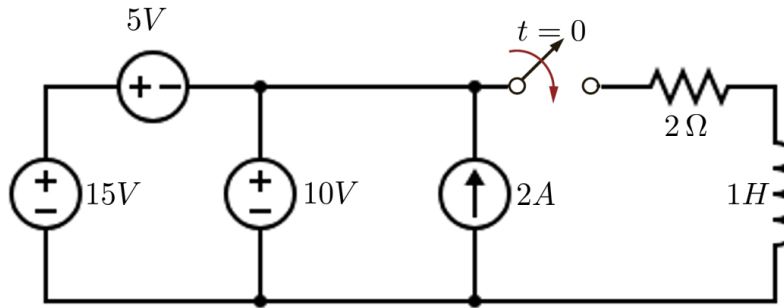
- (a) (5 pts) For a circuit given below, assume that the switch is initially open and is closed at  $t = 0$  and the inductor is not carrying any current before the switch is closed. Label the voltages across resistor and inductor as  $v_R(t)$  and  $v_L(t)$  respectively and plot the waveforms of the voltages.



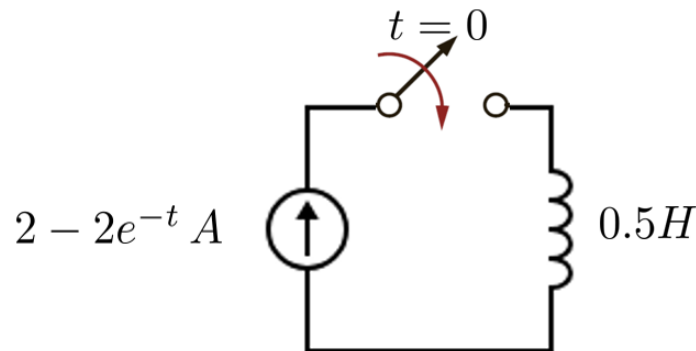
- (b) (5 pts) For a circuit given below, assume that the switch is initially open and is closed at  $t = 0$  and the inductor is not carrying any current before the switch is closed. Determine the voltage across the inductor and the total energy supplied to the inductor.




**Problem 2.** (5 pts) For the circuit given below, determine the equivalent resistance  $R_{eq}$  and the current  $i_o$  indicated in the circuit.  $R_{eq}$  is the equivalent resistance across terminals A and B.

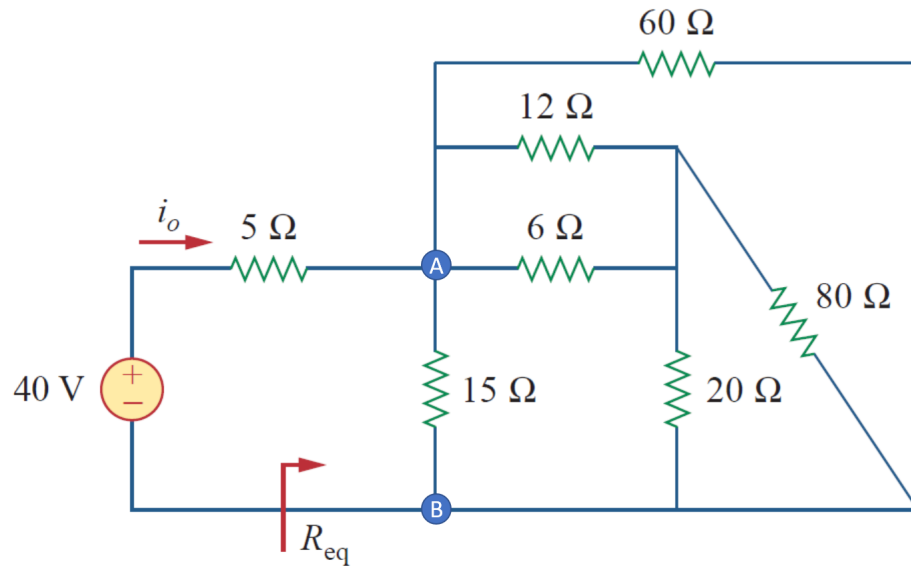


**Problem 3. (3 pts)** For the circuit given below, determine  $V_o$ ,  $I_o$  and  $I_1$  indicated in the circuit. Provide brief justification or working to support your answer.

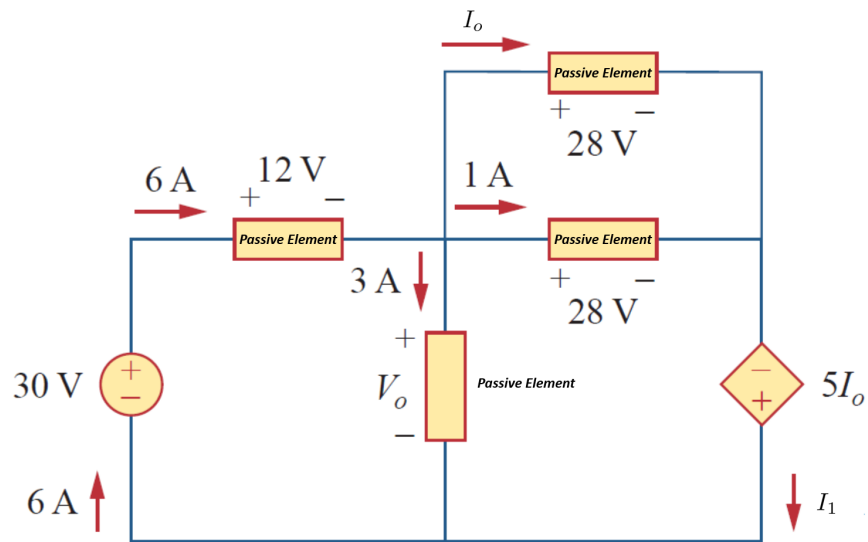

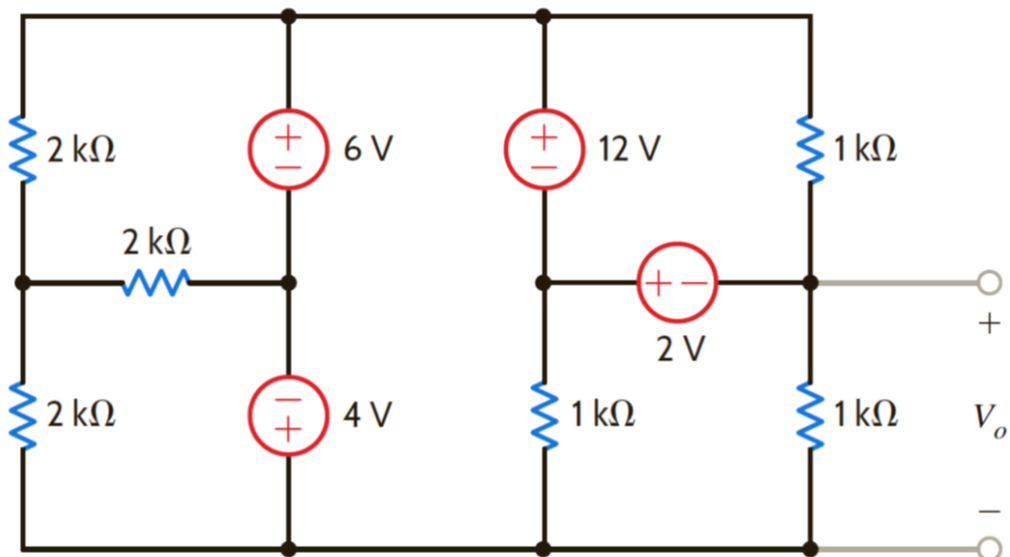**Problem 4. (2 pts)** For the circuit given below, determine  $V_o$ . Provide brief justification or working for your answer.



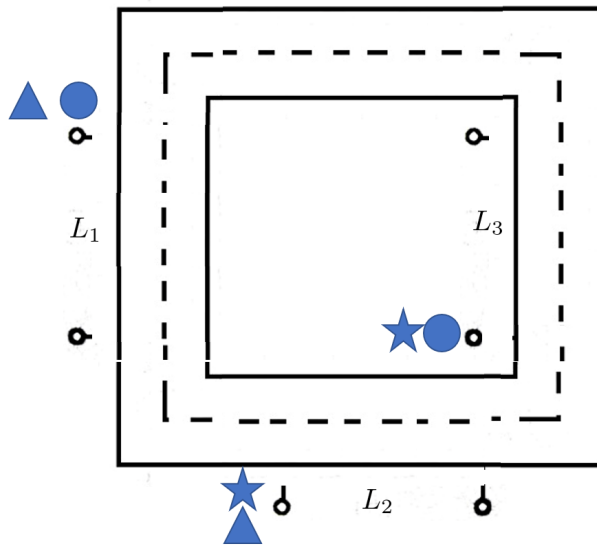**Problem 5. (5 pts)** The figure below shows the dots marked for three windings  $L_1$ ,  $L_2$  and  $L_3$  on a magnetic flux-conducting core. If the dots are marked using the dot convention, draw the windings on the core with directions consistent with the dots.



## Part 2: Network Topology, Network Equations and Kirchhoff's Laws

### Problem 6. (2 pts)


i) What do we mean by electrically equivalent circuits?

ii) Do you agree with the following statement (support your answer with the justification)?

*The two electrically equivalent circuits may not be topologically equivalent but two 'topologically equivalent' circuits are electrically equivalent.*

**Problem 7. (18 pts)**


Consider the circuit given below.

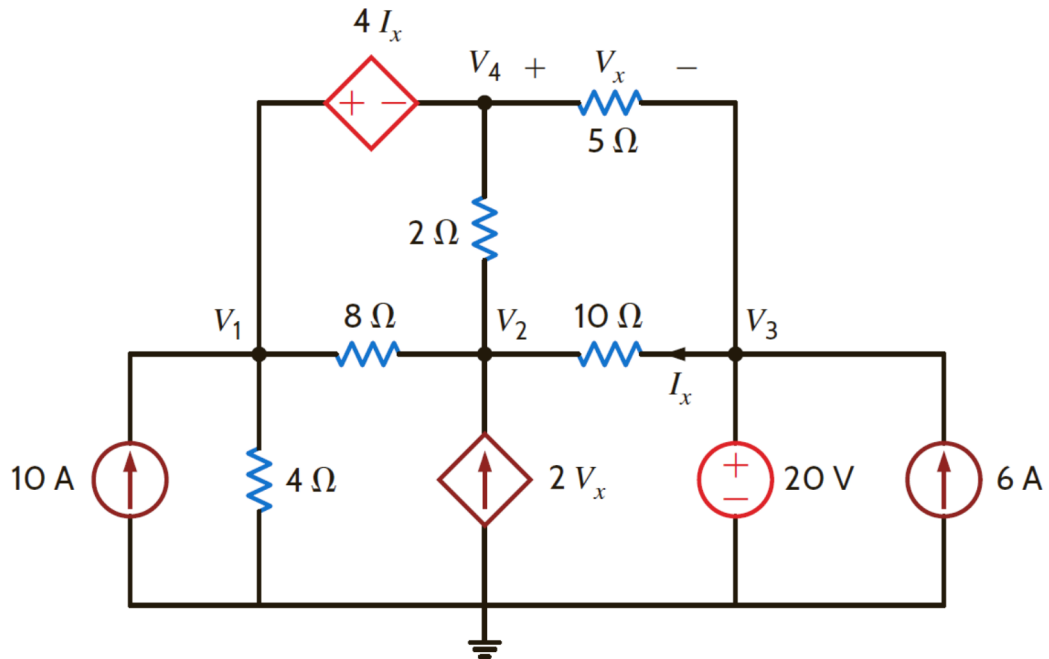

- (4 pts) Draw the graph and one tree of the circuit. Determine the number of nodes and number of branches in a circuit.
- (2 pts) Determine the number of network equations required for carrying out i) nodal analysis and ii) loop analysis.
- (9 pts) Use Kirchhoff current law to determine the nodal voltages indicated on the circuit.
- (3 pts) Determine the power supplied by the voltage source.

### Part 3: Additional Analysis Techniques

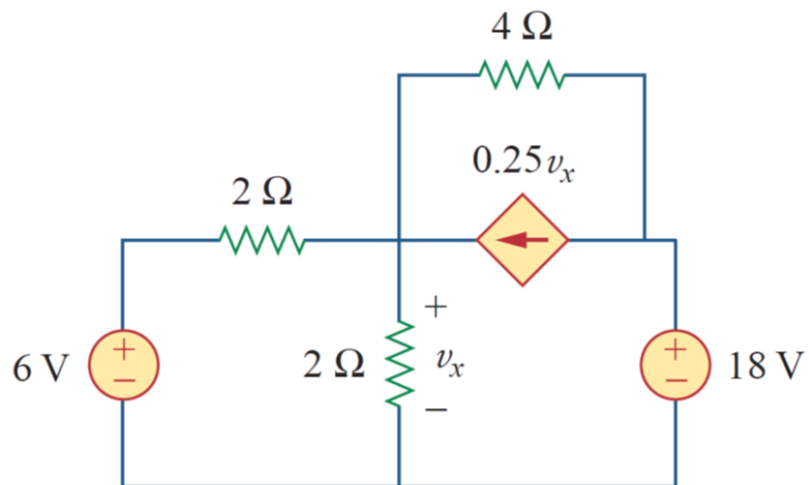**Problem 8.** (8 pts) Determine the voltage  $v_x$  in the following circuit using the source transformation technique.





**Problem 9.** (12 pts) For the circuit given below, determine the current  $i_o$  using superposition principle. You can use any of the techniques (nodal analysis, loop analysis and source transformation) to carry out analysis when you keep one independent source in the circuit.

