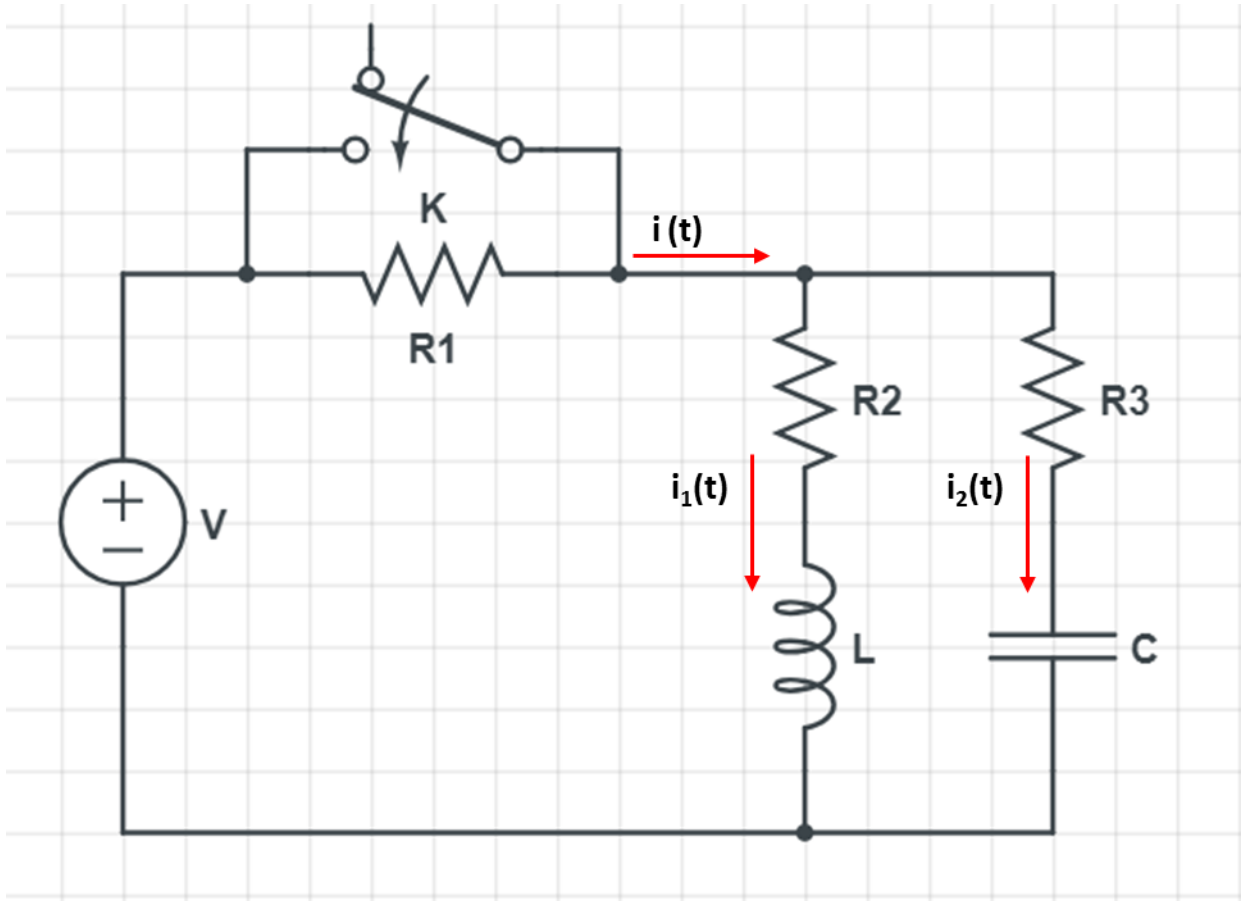


Evaluation of Initial Conditions

Problems – In class


Problem 1 (5-20): In the circuit below, we have $R_1 = 10\Omega$, $R_2 = R_3 = 20\Omega$, $L = 1H$ and $C = 1\mu F$. Assume that the steady state is reached with switch K open. At time $t = 0$, the switch is closed. Determine $i_1(0^+)$, $i_2(0^+)$, $di_1/dt(0^+)$ and $di_2/dt(0^+)$.



Evaluation of Initial Conditions

Problems – In class

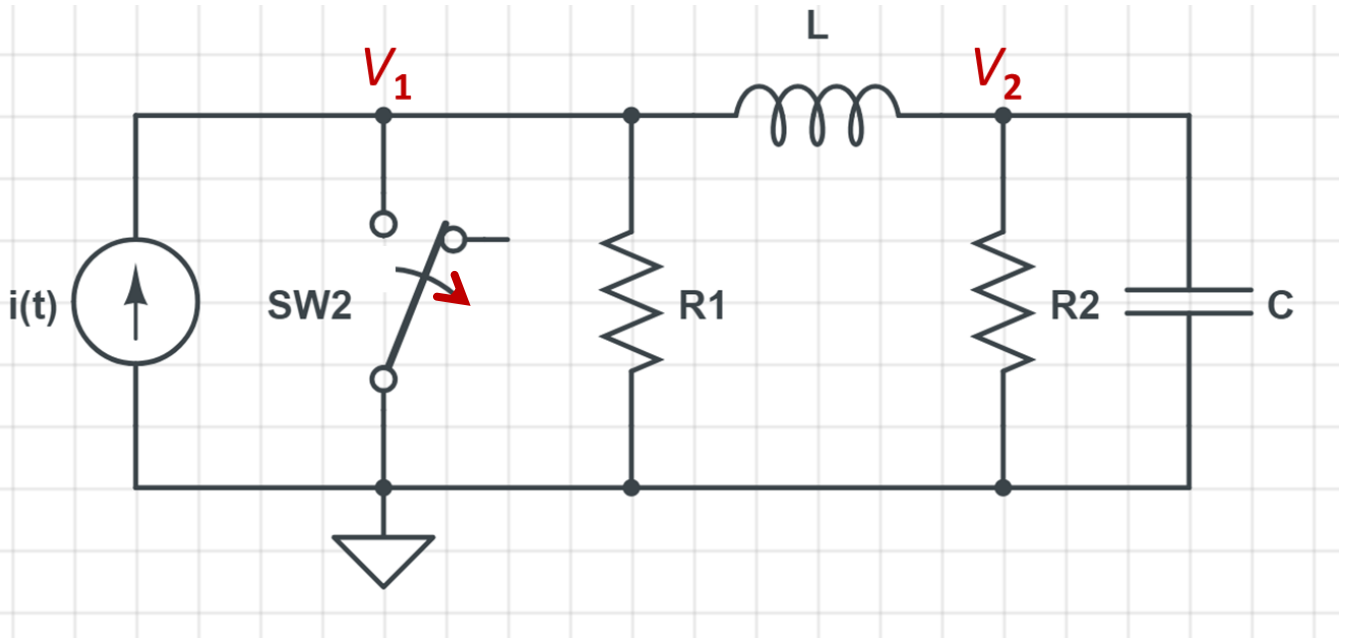
Problem 2 (5-21): In the circuit below, the steady state is reached with switch SW2 in closed state. At time $t = 0$, the switch is closed. Determine $V_1(0^+)$, $V_2(0^+)$, $dV_1/dt(0^+)$ and $dV_2/dt(0^+)$.



Evaluation of Initial Conditions

Problems – In class


Problem 3 (5-24): In the circuit below, the steady state is reached with switch K in opened state. At time $t = 0$, the switch is closed connected a voltage source $v(t) = V \sin(t/\sqrt{MC})$, where M denotes the mutual inductance between the coupled inductors. Determine $V_a(0^+)$, $dV_a/dt(0^+)$ and $d^2V_a/dt^2(0^+)$.

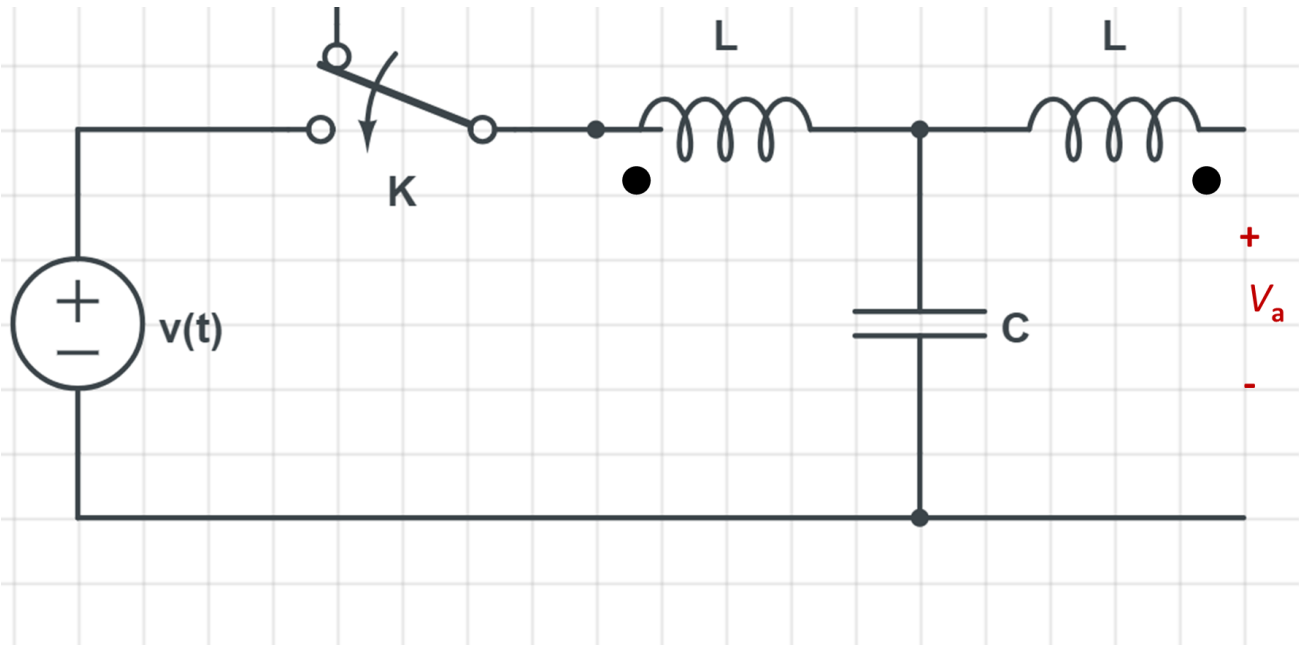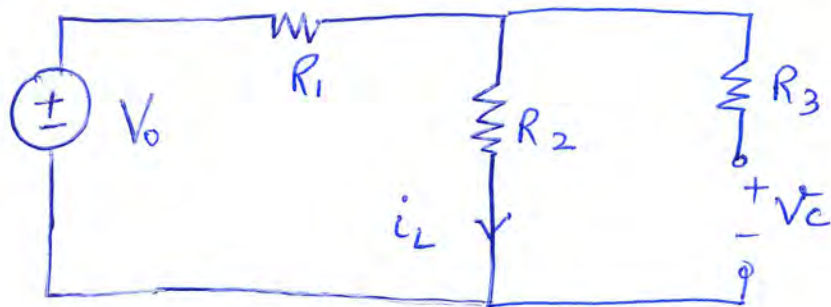


PROBLEM 015-20EVALUATION OF INITIAL CONDITIONSAt $t = 0^-$

$$i_L = \frac{V_0}{R_1 + R_2}$$

$$V_c = \frac{R_2}{R_1 + R_2} V_0$$

At $t = 0^+$
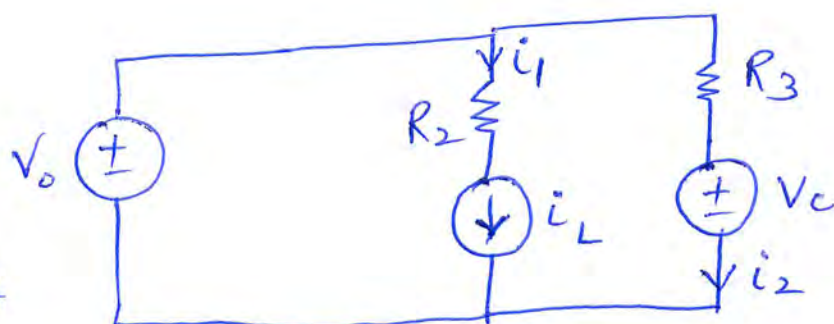
$$\Rightarrow i_1(0^+) = i_L \quad \text{A}$$



$$i_2(0^+) = \frac{V_0 - V_c}{R_3} = \frac{V_0 (R_1)}{R_3 (R_1 + R_2)} \quad \text{A}$$

Loop 1: (V_0 , R_2 and L)

$$\text{Equation: } V_0 = i_1 R_2 + L \frac{di_1}{dt}$$

$$\Rightarrow L \frac{di_1}{dt} = V_0 - i_1 R_2$$

$$\Rightarrow \frac{di_1}{dt} (0^+) = \frac{V_0}{L} - \frac{V_0 R_2}{L (R_1 + R_2)} = \frac{V_0}{L} \frac{R_1}{(R_1 + R_2)} \quad \text{A/sec}$$

Loop 2: V_0 , R_3 and C

$$\text{Equation: } V_0 = i_2 R_3 + \frac{1}{C} \int i_2 dt \Rightarrow 0 = R_3 \frac{di_2}{dt} + \frac{i_2}{C}$$

$$\Rightarrow \frac{di_2}{dt} = - \frac{i_2}{R_3 C}$$

$$\Rightarrow \frac{di_2}{dt} (0^+) = \frac{-V_0 R_1}{R_3^2 (R_1 + R_2)} \quad \text{A/sec.}$$


Problem 02

5-21

At $t=0^-$

$$i_L = 0$$


$$v_C = 0$$

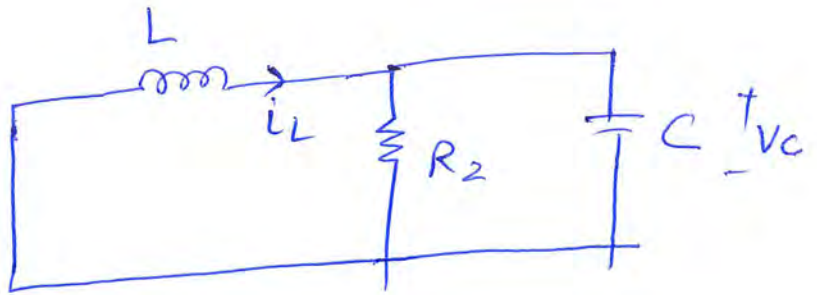

At $t=0^+$; Replace L with open circuit
 and C with short circuit

$$v_1 = R_1 i(t) = R_1 i(0^+) \text{ Volts}$$

$$v_2 = 0 \text{ Volts}$$

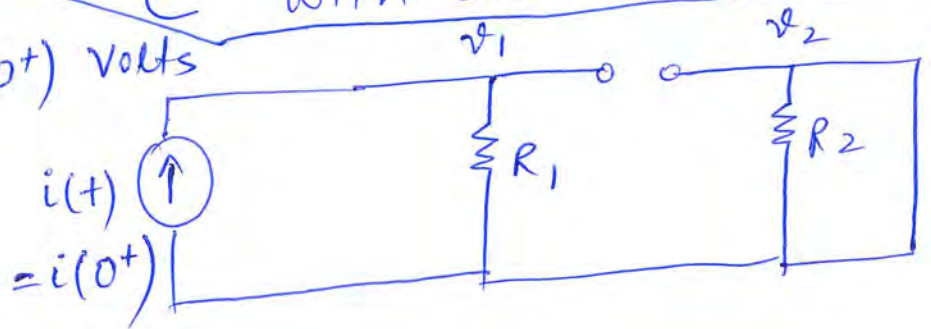

Node ① Equation

$$\frac{v_1}{R_1} + \frac{1}{L} \int (v_1 - v_2) dt = i(t)$$

$$\frac{1}{R_1} \frac{dv_1}{dt} + \frac{v_1 - v_2}{L} = \frac{di}{dt}$$

$$\Rightarrow \frac{dv_1}{dt} = R_1 \frac{di}{dt} + R_1 \frac{v_2 - v_1}{L}$$

$$\text{at } t=0^+ \quad \frac{dv_1}{dt} = R_1 \frac{di(0^+)}{dt} - R_1 \frac{i(0^+)}{L}$$

Node ② Equation

$$\frac{v_2}{R_2} + \frac{C dv_2}{dt} + \frac{1}{L} \int (v_2 - v_1) dt = 0$$

At $t=0^+$

$$i_L = 0 \text{ at } t=0^+$$

V/sec

$$\Rightarrow \boxed{\frac{dv_2}{dt} = 0} \text{ at } t=0^+$$


Problem 03

5-24

~~At~~ At $t=0^-$; * current through inductor is zero
 * voltage across capacitor is zero

After the switch is closed :-

$i(0^+) = 0$
Loop Equation

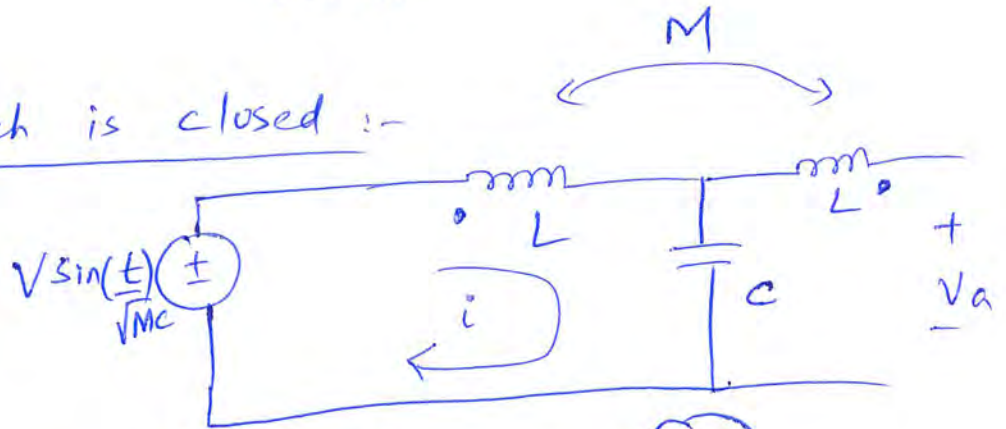

$$V \sin \frac{t}{\sqrt{MC}} + L \frac{di}{dt} + \underbrace{\frac{1}{C} \int i dt}_{0 \text{ at } t=0^+} = 0 \quad \text{--- (01)}$$

$$\Rightarrow \frac{di(0^+)}{dt} = - \frac{V}{L} \sin\left(\frac{t}{\sqrt{MC}}\right) \Big|_{t=0^+} = 0$$

$$\underline{V_a} :- \quad V_a = \frac{1}{C} \int i dt + M \frac{di}{dt} \quad \text{--- (02)}$$

$t=0^+$ $V_a = 0$

Taking derivative of (01) $\Rightarrow \frac{d^2 i}{dt^2} (0^+) = \frac{V}{\sqrt{MC}}$

Taking (02) $\Rightarrow \frac{dV_a}{dt} (0^+) = \frac{V}{L} \sqrt{\frac{M}{C}}$

Taking twice

$$\frac{d^2 V_a}{dt^2} = \frac{1}{C} \frac{di}{dt} + M \frac{d^3 i}{dt^3} \Rightarrow \frac{d^2 V_a}{dt^2} (0^+) = 0$$