

**LAHORE UNIVERSITY OF MANAGEMENT SCIENCES**  
**Department of Electrical Engineering**

**EE240 Circuits I**  
**Quiz 01 Solutions**

Name: \_\_\_\_\_


Campus ID: \_\_\_\_\_

Total Marks: 10

Time Duration: 15 minutes

**Question 1** (4 marks)

The charge on the capacitor of capacitance  $0.5F$  is plotted against time in Figure 1 below.

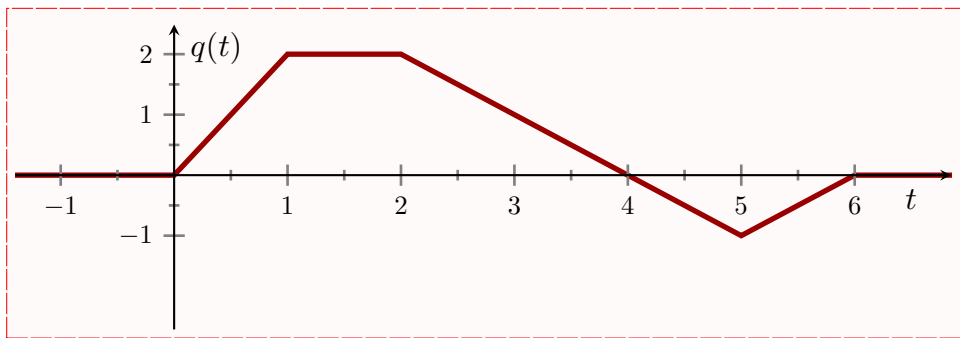

**Figure 1:** Charge on the Capacitor.


- (a) [3 marks] Determine (or plot) the current  $i_c(t)$  through the capacitor.

**Solution:** The current through the capacitor is given by

$$i_c(t) = \frac{dq(t)}{dt}$$

$$i_c(t) = \begin{cases} 0 & t \leq 0 \\ 2 & 0 < t \leq 1 \\ 0 & 1 < t \leq 2 \\ -1 & 2 < t \leq 5 \\ 1 & 5 < t \leq 6 \\ 0 & 6 < t \end{cases}$$

The plot is given below:

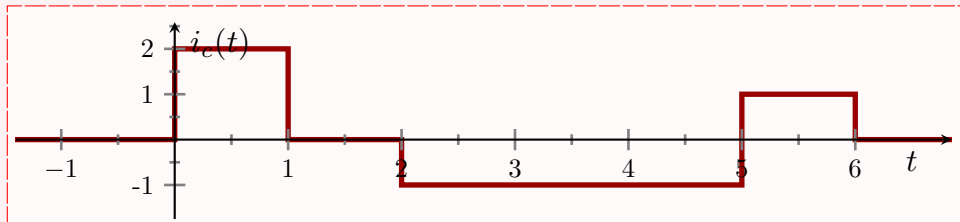

- (b) [1 mark] Determine the energy stored in the capacitor at  $t = 1.5s$ .


**Solution:** Energy in the capacitor is given by  $w = \frac{1}{2}CV^2 = \frac{q^2}{2C}$ . Since  $q(1.5) = 2$  Coulombs,  $w = 4J$ .

**Question 2** (2 marks)

The current source is connected to elements 1 and 2 in series in the circuit given below. Determine


the power being *supplied* by the current source and the power being *absorbed or dissipated* by the elements.

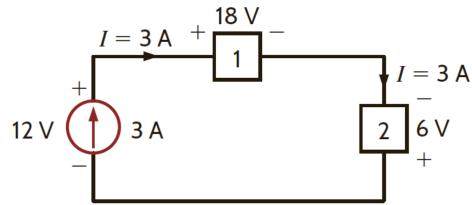**Solution:** Current source supplies 36 W. Element 1 absorbs 54 W and element 2 absorbs -18 W (using passive sign convention).



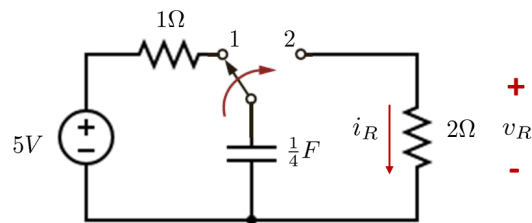**Question 3** (4 marks)

Consider the circuit given below. Assume that the switch is at position 1 for very long time and the capacitor is fully charged. The switch is moved from position 1 to position 2 at  $t = 0$ . Plot  $v_R(t)$  and  $i_R(t)$  for all times.



**Solution:** Capacitor is fully charged means that the voltage across capacitor is 5V.  $v_R(t)$  is zero for  $t \leq 0$ . As soon the switch is operated  $v_R(t) = 5V$  which decays exponentially to zero with time. Mathematically,  $v_R(t) = 5e^{-2t}u(t) V$  and  $i_R = 2.5e^{-2t}u(t) A$ .