

**LAHORE UNIVERSITY OF MANAGEMENT SCIENCES**  
**Department of Electrical Engineering**

**EE240 Circuits I**  
**Quiz 04 Solutions**

Name: \_\_\_\_\_


Campus ID: \_\_\_\_\_

Total Marks: 10

Time Duration: 20 minutes

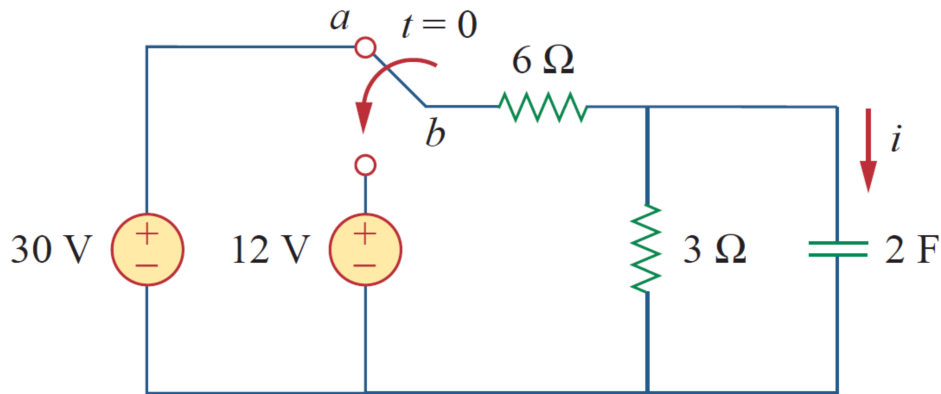**Question 1** (10 marks)

In a first-order circuit given below, the switch is operated from position a to position b at  $t = 0$ .



- (a) [1 mark] Determine the voltage across capacitor at  $t = 0^-$ .

**Solution:**

$$v_c(0^-) = 30 \frac{3}{9} = 10 \text{ V}$$

- (b) [2 marks] Determine  $i(t)$  at  $t = 0^+$ .

**Solution:** For  $t \geq 0$ ,  $v_c(t)$  and  $i(t)$  are related by  $v_c(t) = \frac{1}{2} \int i dt$ . Applying KCL yields

$$\frac{v_c}{3} + \frac{v_c - 12}{6} + i = 0 \quad \Rightarrow \quad \frac{v_c}{2} - 2 + i = 0.$$

We can evaluate this at  $t = 0$  to obtain  $i(0^+) = 2 - 5 = -3 \text{ A}$ .

- (c) [2 marks] Write down the differential equation, in terms of  $i(t)$ , describing the circuit after the switch is operated, that is, for  $t \geq 0$ .

**Solution:** Using the equation formulated in part(b), we obtain

$$\frac{1}{4} \int i dt + i = 2. \quad \Rightarrow \quad \frac{di}{dt} + \frac{i}{4} = 0$$

- (d) [1 mark] Determine  $i(t)$  at  $t = \infty$ .

**Solution:**

$$i(0^+) = 0 \text{ A}$$

- (e) [3 marks] Determine  $i(t)$  for all values of  $t$  and plot (and label) it.

**Solution:**  $i(t) = 0$  for  $t < 0$ . Using differential equation formulation, we determine

$$i(t) = Ke^{-t/4},$$

where  $K = -3$  using the initial conditions.

Alternatively, we can start with the following solution:

$$i(t) = K_1 + K_2e^{-t/\tau}.$$

We can find  $K_1 = 0$  and  $K_2 = -3$  using initial and final conditions and  $\tau = R_{\text{eq}}C = 4\text{ s}$ , where  $R_{\text{eq}} = 6||3 = 2\Omega$ .

- (f) [1 mark] On the plot that is obtained in part (e), superimpose plot of  $i(t)$  for if 2 F capacitor is replaced with 1 F capacitor.

**Solution:** For  $C = 1\text{ F}$ , time constant is halved and therefore the current decays to zero relatively faster.