

Department of Electrical Engineering

School of Science and Engineering

EE240 Circuits I - Fall 2022

## ASSIGNMENT 1

---

Due Date: 4:30pm, Monday, October 03, 2022

Format: 6 problems, for a total of 100 marks

(Assignment is to be submitted in class)


Instructions:

- You are allowed to collaborate with your peers but copying your colleague's solution is strictly prohibited. This is not a group assignment. Each student must submit his/her own assignment.
  - Solve the assignment on blank A4 sheets and staple them before submitting.
  - Submit in-class or in the drop box labelled EE-240 outside the instructor's office.
  - Write your name and roll no. on the first page.
  - Feel free to contact the instructor or the teaching assistants if you have any concerns.
- 


Course Learning Outcomes Covered:

Derive and apply working principle of passive components R, L,C and independent and controlled energy sources for device and circuit modeling and analysis


---

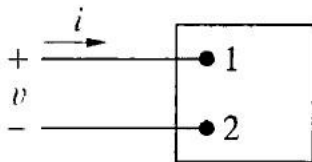**Problem 1 [12 marks]: Power and circuit variables**


(a)  $p = vi$

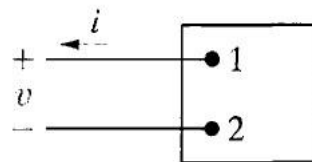

(b)  $p = -vi$

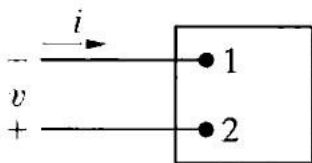


(c)  $p = -vi$

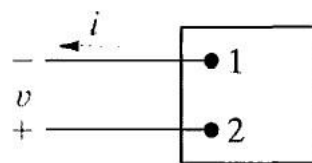


(d)  $p = vi$

Consider a 20 V voltage drop occurs across an element from terminal 2 to terminal 1 and that a current of 4 A enters terminal 2.


- [8 marks] Specify the values of V and I for the polarity references shown in figures (a)-(d) above.
- [2 marks] Describe whether the circuit inside the box is absorbing or delivering power.
- [2 marks] How much power is the circuit absorbing, if its not absorbing then explain why?

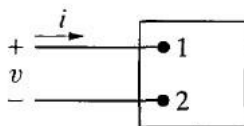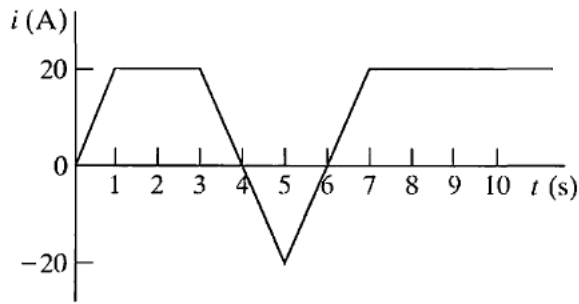**Problem 2 [12 marks]: Energy and Power**

The voltage and current across the terminals of the circuit element above are shown in the plots (a) and (b) below:



(a)

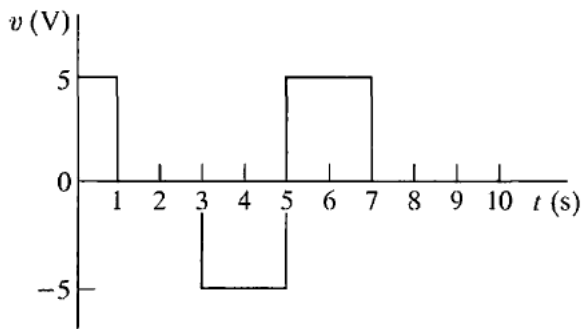

(b)

- a) [6 marks] Sketch the power versus time plot for  $0 \leq t \leq 10$ s.
- b) [2+2+2 marks] Calculate the energy delivered to the circuit element at  $t = 1$ , 6, and 10s respectively.


### Problem 3 [20 marks]: Capacitors

A parallel plate capacitor can handle 46J for 200V.

(a) [12 marks]




- (i) [3 marks] What is its capacitance?
- (ii) [2 mark] If the distance between the two capacitor plates is  $d = 1$ cm, what is the area of the plates?
- (iii) [4 marks] The distance between the two plates is now decreased to quarter of  $d$ , keeping the plates at the same potential, what is the change in the capacitance? And how about when the area is halved keeping the distance and potential constant?
- (iv) [3 marks] What is the amount of the current that needs to be discharged in both cases mentioned in (iii)?

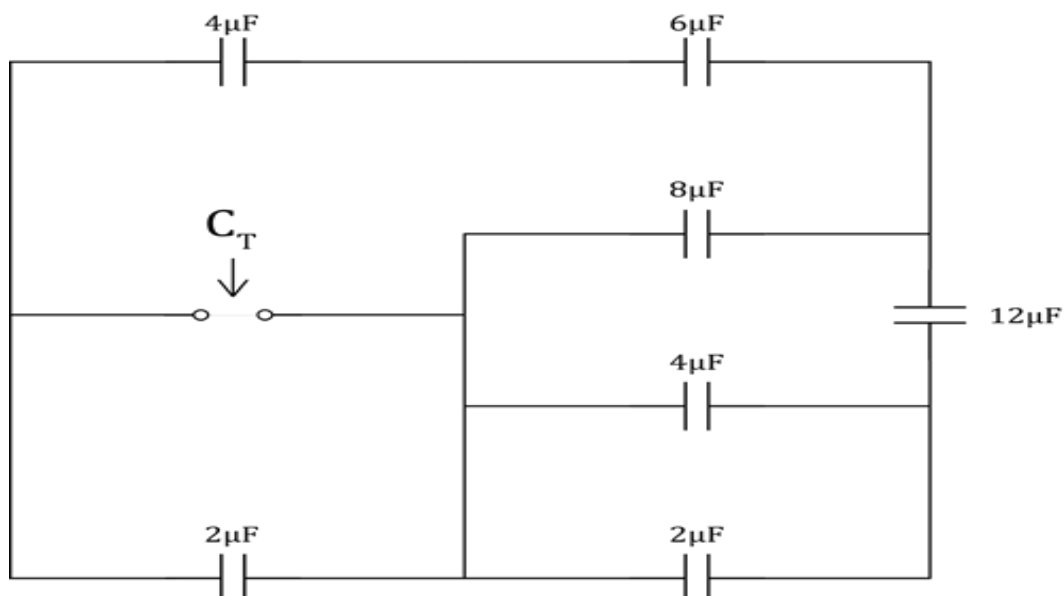(b) [9 marks] Find the capacitance  $C_T$  for the network below.



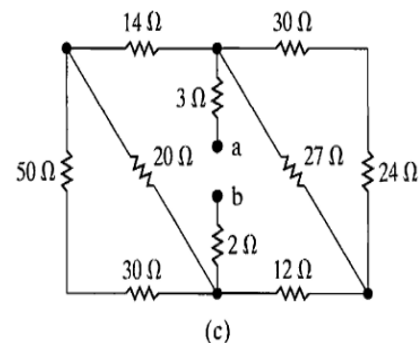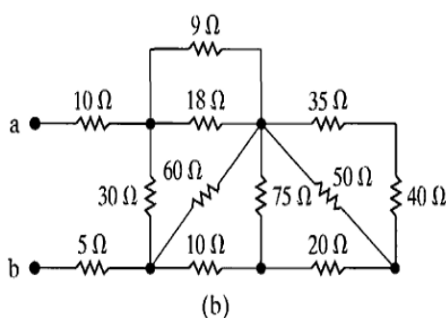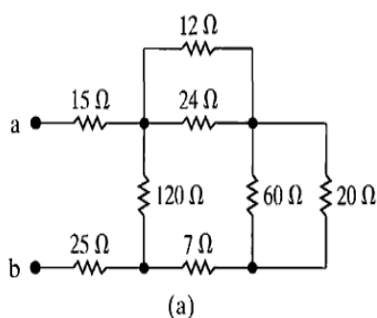**Problem 4 [15 marks]: Equivalent Resistance**

Find the equivalent resistance at  $R_{ab}$ , for each of the circuits in figures (a), (b), and (c) below.




**Problem 5 [20 marks]: Inductors**

- a) [5 marks] The current through a 0.1-H inductor is  $i(t) = 10te^{-5t}$  A. Find the voltage across the inductor and the energy stored in it.
- b) [5 marks] Find the current through a 5-H inductor if the voltage across it is:

$$v(t) = \begin{cases} 30t^2, & t > 0 \\ 0, & t < 0 \end{cases}$$

Also find the energy stored within  $0 < t < 5$  s.

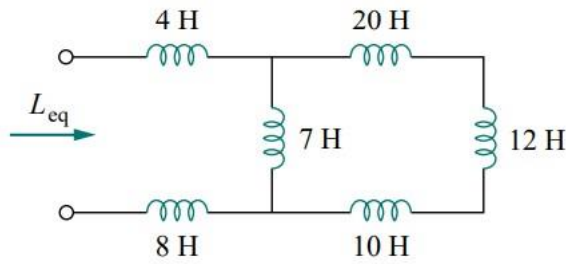- c) [5marks] Find the equivalent inductance of the circuit shown in figure below:




- d) [2 marks] The current in an 80-mH inductor increases from 0 to 60 mA. How much energy is stored in the inductor?
- e) [3 marks] The current through a 12-mH inductor is  $4 \sin 100t$  A. Find the voltage, and also the energy stored in the inductor for  $0 < t < \pi/200$  s.

**Problem 6 [20 marks]: Visualizing circuit parameters**

The charge that enters the BOX is shown in figure below. Calculate and sketch the

- a) Current flowing into the BOX.
- b) and the power absorbed by the BOX.

between 0 and 10 milliseconds.

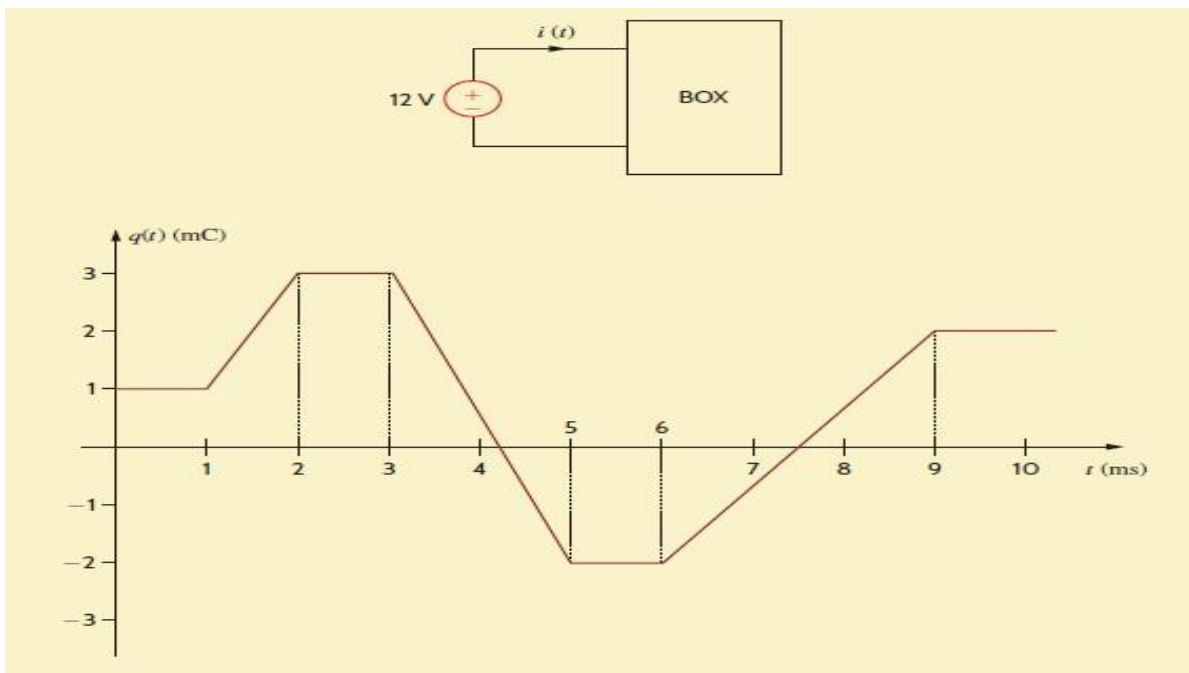

\*\*\*