

Department of Electrical Engineering
School of Science and Engineering

EE240 Circuits I - Fall 2022

ASSIGNMENT 3

Due Date: 4:30pm, Monday, November 28, 2022

Format: 6 problems, for a total of 120 marks

(Assignment is to be submitted in class)

Instructions:


- You are allowed to collaborate with your peers but copying your colleague's solution is strictly prohibited. This is not a group assignment. Each student must submit his/her own assignment.
 - Solve the assignment on blank A4 sheets and staple them before submitting.
 - Submit in-class or in the drop box labelled EE-240 outside the instructor's office.
 - Write your name and roll no. on the first page.
-
- Feel free to contact the instructor or the teaching assistants if you have any concerns.
-

Course Learning Outcomes Covered:

Formulate network equations based on the understanding of Kirchhoff's voltage and current laws.

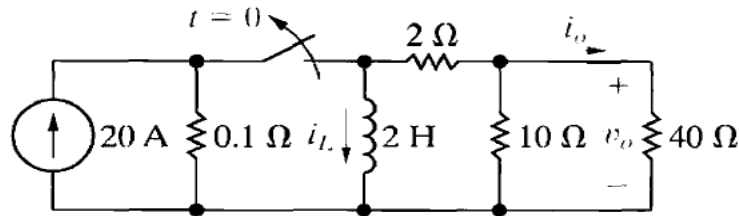Problem 1 [18 marks]: First Order Circuits (RL)


The switch in the circuit shown in the figure has been closed for a long time before its opened at time $t = 0$.



Find:

- a) [4 marks] Current through the inductor i_L for $t \geq 0$.
- b) [4 marks] Current i_o for $t \geq 0^+$.
- c) [4 marks] Voltage v_o for $t \geq 0^+$.
- d) [6 marks] The percentage of total energy stored in the 2H inductor that is dissipated in the 10 Ω resistor.

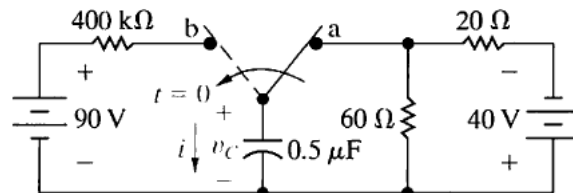Problem 2 [30 marks]: First Order RC Circuit Response





The switch in the circuit shown in Figure above has been in position a for a long time.

At $t = 0$ the switch is moved to position b.

- a) [5 marks] What is the initial value of V_c ?
- b) [3 marks] What is the final value of V_c ?
- c) [3 marks] What is the time constant of the circuit when the switch is in position b?
- d) [3 marks] What is the expression for $V_c(t)$ when $t \geq 0$?
- e) [6 marks] What is the expression for $i(t)$ when $t \geq 0^+$?
- f) [5 marks] How long after the switch is in position b does the capacitor voltage equal zero?
- g) [5 marks] Plot $V_c(t)$ and $i(t)$ versus t .


Problem 3 [17 marks]: Initial Conditions

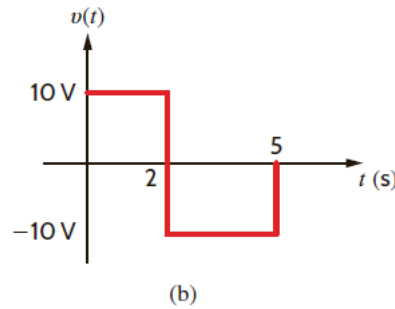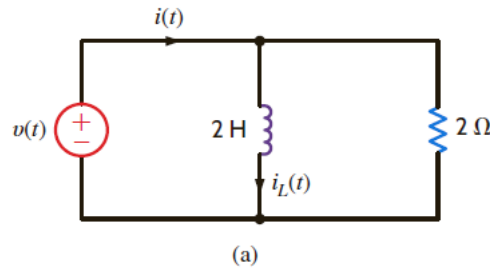


The voltage $V(t)$ shown in Fig. a is given by the graph shown in Fig. b. If $I_L(0) = 0$, answer the following questions:

- (a) [4 marks] How much energy is stored in the inductor at $t = 3$ s?
- (b) [4 marks] How much power is supplied by the source at $t = 4$ s?
- (c) [5 marks] What is $i(t = 6$ s)?
- (d) [4 marks] How much power is absorbed by the inductor at $t = 3$ s?

Problem 4 [15 marks]: Initial conditions

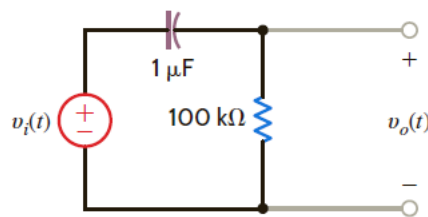

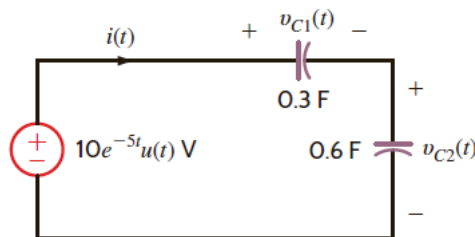
- (a) [7 marks] Find the output voltage $v_o(t)$ in the network in Fig. above if the input voltage is $v_i(t) = 5(u(t) - u(t - 0.05))$ V.



- (b) [8 marks] In the network in Fig. above, find $i(t)$ for $t > 0$. If $v_{C1}(0^-) = -10$ V, calculate $v_{C2}(0^-)$.

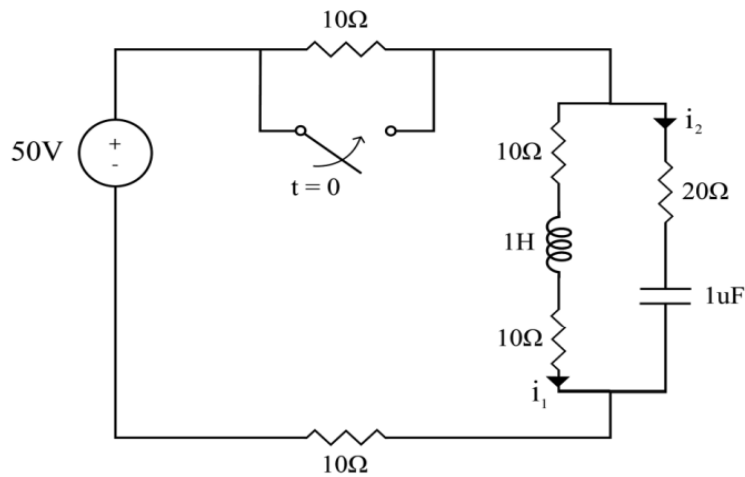Problem 5 [20 marks]: Initial Conditions

In the fig. shown below, the switch is initially open and steady state is achieved. At time $t=0$, the switch is closed.



- (a) [5 marks] Produce the first order differential equations that govern the circuit.
- (b) [3 marks] Determine $V_c(0^-)$, the voltage across the capacitor before the switch is closed. Indicate its polarity.
- (c) [10 marks] Calculate $i_1(0^+)$, $i_2(0^+)$, $di_1(0^+)/dt$, and $di_2(0^+)/dt$.
- (d) [2 mark] Determine $di_1(\infty)/dt$.

Problem 6 [20 marks]: First Order Circuits

For the circuit given below, find out $v(t)$ for all times $t > 0$ and also sketch its waveform.

