

Department of Electrical Engineering
School of Science and Engineering

EE240 Circuits I - Fall 2022

ASSIGNMENT 4

Due Date: 4:30pm, Monday, December 12, 2022 (Submit in the Dropbox located outside 9-251)

Format: 5 problems, for a total of 100 marks


Instructions:

- You are allowed to collaborate with your peers but copying your colleague's solution is strictly prohibited. This is not a group assignment. Each student must submit his/her own assignment.
 - Solve the assignment on blank A4 sheets and staple them before submitting.
 - Submit in-class or in the drop box labelled EE-240 outside the instructor's office.
 - Write your name and roll no. on the first page.
 - Feel free to contact the instructor or the teaching assistants if you have any concerns.
-

Course Learning Outcomes Covered:


- Analyze first and second order switched circuits for their initial and final condition, transient response etc.
 - Solve switched linear networks up to second order using initial conditions
-

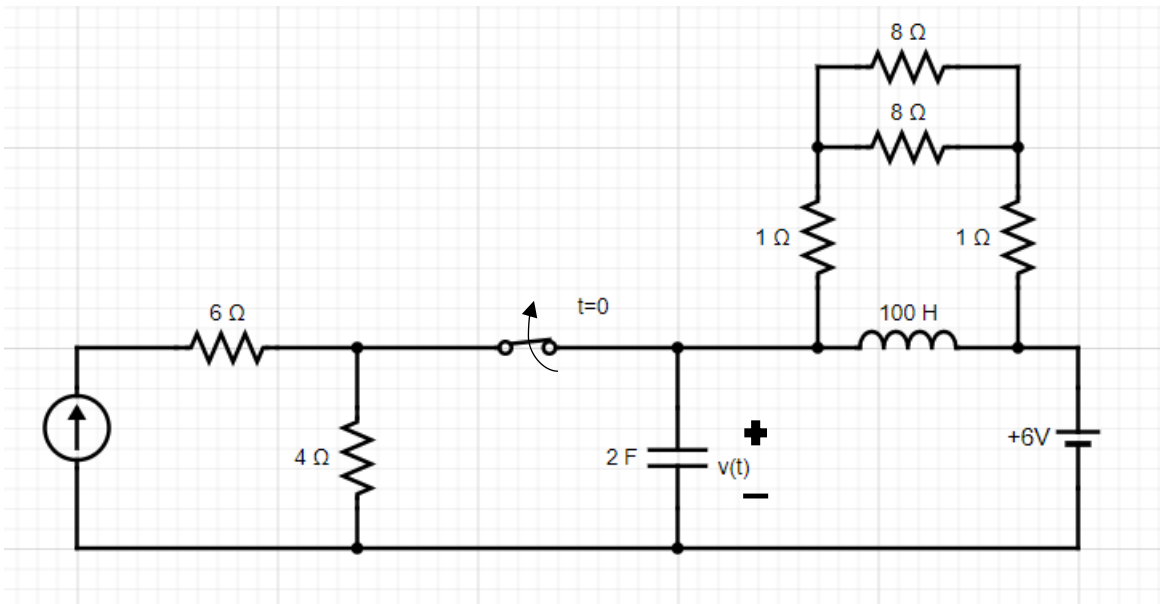Q1) The circuit contains a 2A current source. The switch is opened at $t=0$.




- i) Draw how the circuit looks at $t=0^-$ and determine the initial conditions of the capacitor and inductor. [3 marks]
- ii) Determine $v(t)$ for the circuit at $t > 0$. [7 marks]

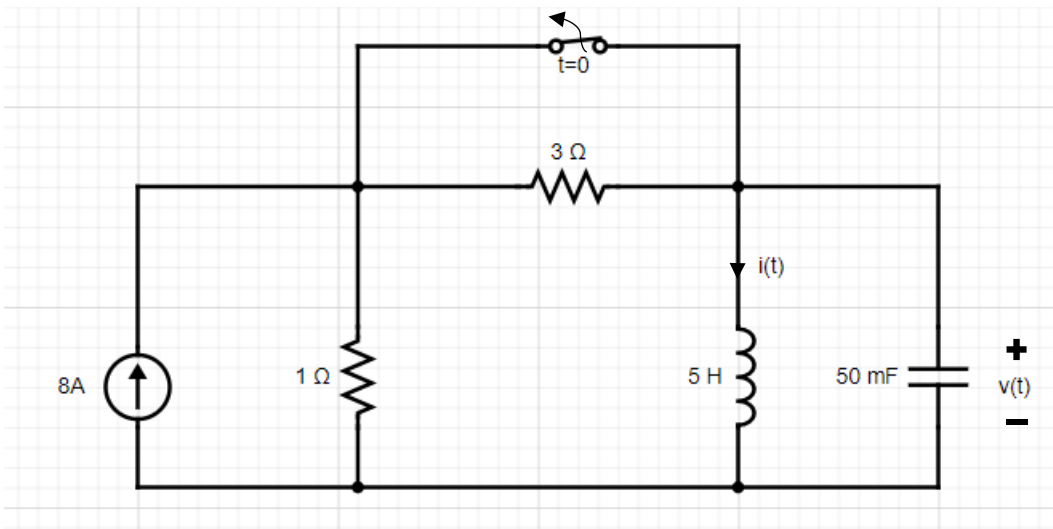Q2) Determine $i(t)$ in the circuit shown below for $t > 0$. [10 marks]




Q3) For the following circuit, compute its:

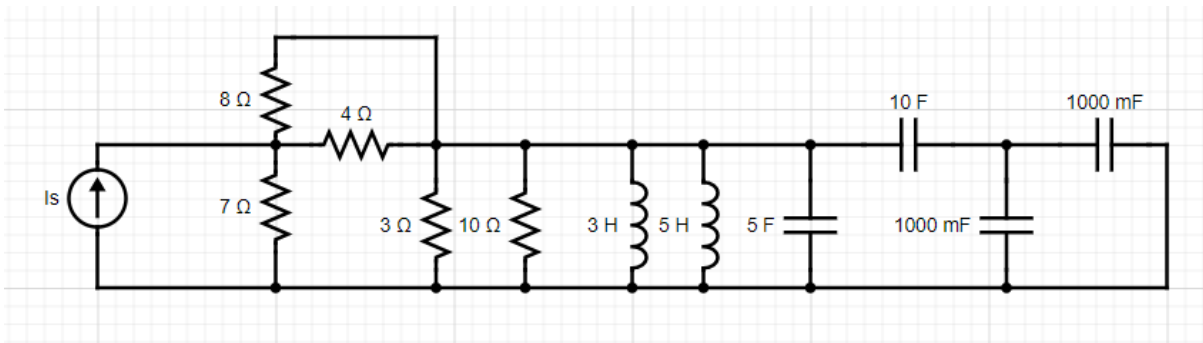- i) Resonant Frequency [2 marks]
- ii) Bandwidth [2 marks]
- iii) Quality factor [1 mark]



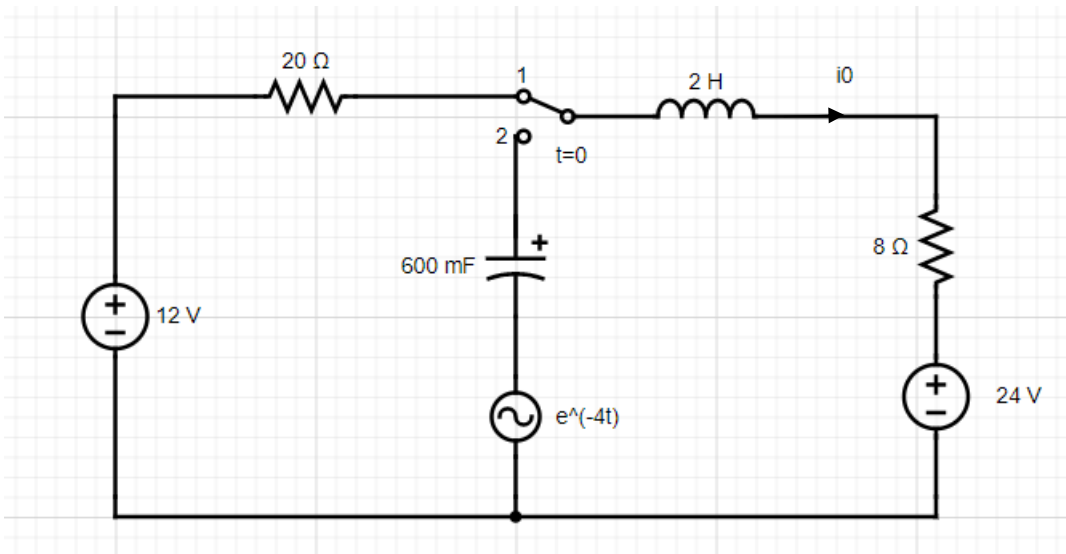Q4) In the following circuit, the switch is moved from position 1 to position 2 at $t = 0$. Determine $i_0(t)$ for $t \geq 0$. [15 marks]



Q5) The current flowing through a series RLC circuit driven by a voltage source is given by for $t > 0$:

$$Ze^{-4t} - 30e^{-6t} - 5e^{-2t} + 20e^{-5t}$$

where Z is an unknown constant. The voltage source is given by:

$$V(t) = (5e^{-2t} + 3e^{-5t})u(t)$$

The inductance is $L = 0.5H$.

- i) Find the corresponding value of R and C and draw the circuit. [4 marks]
- ii) Determine the value of Z . [4 marks]
- iii) Derive an expression for voltage across inductor $v_L(t)$ and find $v_L(t)$ at inductor voltage at $t = 1s$. [2 marks]