

LAHORE UNIVERSITY OF MANAGEMENT SCIENCES  
Department of Electrical Engineering

EE240 Circuits I  
Quiz 01 Solutions

**Question 1** (4 marks)

Determine the total charge entering a terminal of an electrical component between  $t = 1$  s and  $t = 2$  s if the current passing the terminal is  $i(t) = 3t^2 - t$  A.


**Solution:** The total charge is given by

$$q = \int_1^2 (3\tau^2 - \tau) d\tau = 5.5 \text{ C}$$

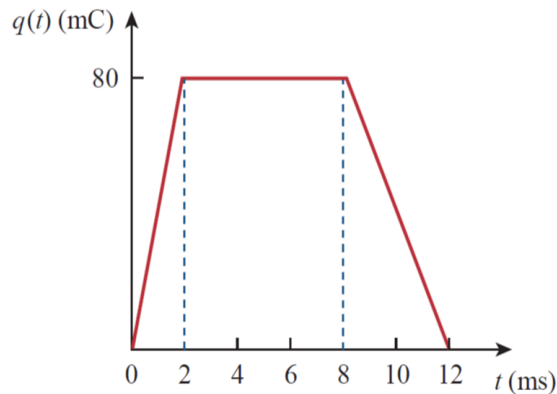**Question 2** (3 marks)


Find the current at  $t = 6$  ms and at  $t = 10$  ms if the charge entering a certain element is shown below.

**Solution:** We know that  $i(t) = \frac{dq}{dt}$  and therefore  $i(6 \text{ ms}) = 0$  and  $i(10 \text{ ms}) = 0$ .



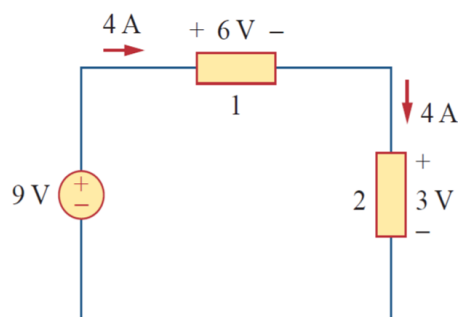**Question 3** (3 marks)

For the circuit given below, calculate the power dissipated or supplied by each element.



**Solution:** Power dissipated by element 1 is 24 W, power dissipated by element 2 is 12 W and the power dissipated by voltage source is -36 W.