

**LAHORE UNIVERSITY OF MANAGEMENT SCIENCES**  
**Department of Electrical Engineering**

**EE240 Circuits I**  
**Quiz 08**

**Name:** \_\_\_\_\_


**Campus ID:** \_\_\_\_\_

**Total Marks:** 10

**Time Duration:** 20 minutes

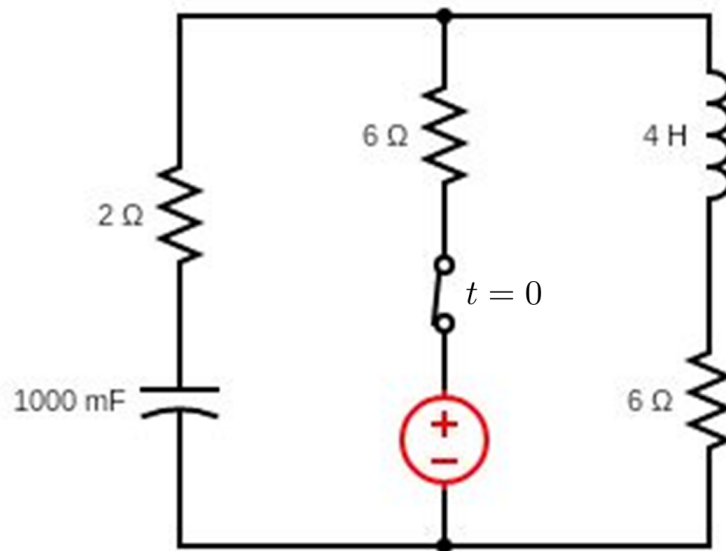**Question 1** (10 marks)

Consider the following circuit. The voltage source is 24 V DC. The switch is opened at  $t = 0$ .



- (a) [2 marks] Draw a snapshot of the circuit at  $t = 0^-$  and determine the voltage across capacitor and current through inductor at  $t = 0^-$ .

**Solution:** At  $t = 0^-$ , the capacitor acts as an open circuit since it will be fully charged and the inductor acts as a short circuit. The circuit at  $t = 0^-$  comprised of 24 V voltage source in series with two  $6\ \Omega$  resistors.

$$i_L(0^-) = 24/12 = 2\text{ A and } v_c(0^-) = 12\text{ V.}$$

- (b) [3 marks] Formulate a differential equation in terms of  $i_L(t)$  for  $t \geq 0$ . ( $i_L$  is the current through inductor from top to bottom).

**Solution:** Once the switch is operated, we have a series RLC circuit with equation in terms of  $i_L(t)$  given by

$$L \frac{di_L}{dt} + Ri_L + \frac{1}{C} \int i_L dt = 0$$

$$\frac{di_L}{dt} + \frac{8}{4}i_L + \frac{1}{4 \times 1} \int i_L dt = 0$$

$$\frac{di_L}{dt} + 2i_L + \frac{1}{4} \int i_L dt = 0 \tag{1}$$

(c) [5 marks] Determine  $i_L(t)$  for all times.

**Solution: Initial Conditions First:**

$i_L(0^+) = i_L(0^-) = 2 A$ . To find,  $\frac{di_L}{dt}$  at  $t = 0^+$ , we use

$$L \frac{di_L}{dt} + Ri_L + \frac{1}{C} \int i_L dt = 0$$

Note here  $\frac{1}{C} \int i_L dt = -v_C(t)$  and therefore  $\frac{1}{C} \int i_L dt = -12 V$  at  $t = 0^+$ . Consequently, we have

$$4 \frac{di_L}{dt}(0^+) + 8i_L(0^+) - 12 = 0,$$

which yields

$$\frac{di_L}{dt}(0^+) = -1 A/s.$$

**Solution of Differential Equation:**

Characteristic equation for (1) is given by

$$s^2 + 2s + \frac{1}{4} = 0$$

The roots are given by  $s_1 = -1 + \frac{\sqrt{3}}{2}$  and  $s_2 = -1 - \frac{\sqrt{3}}{2}$ . Consequently, we have

$$i(t) = K_1 e^{s_1 t} + K_2 e^{s_2 t}, \quad t \geq 0$$

Using initial conditions, we obtain  $K_1 = 1 + \frac{1}{\sqrt{3}}$  and  $K_2 = 1 - \frac{1}{\sqrt{3}}$ .