
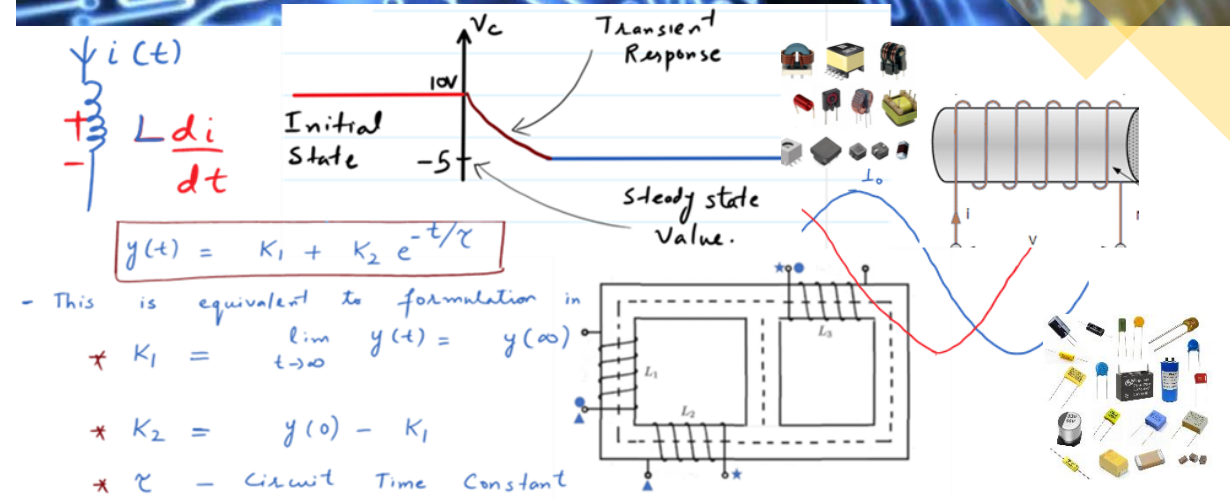


EE 240 Circuits I

Dr. Zubair Khalid

Department of Electrical Engineering
School of Science and Engineering

Lahore University of Management Sciences

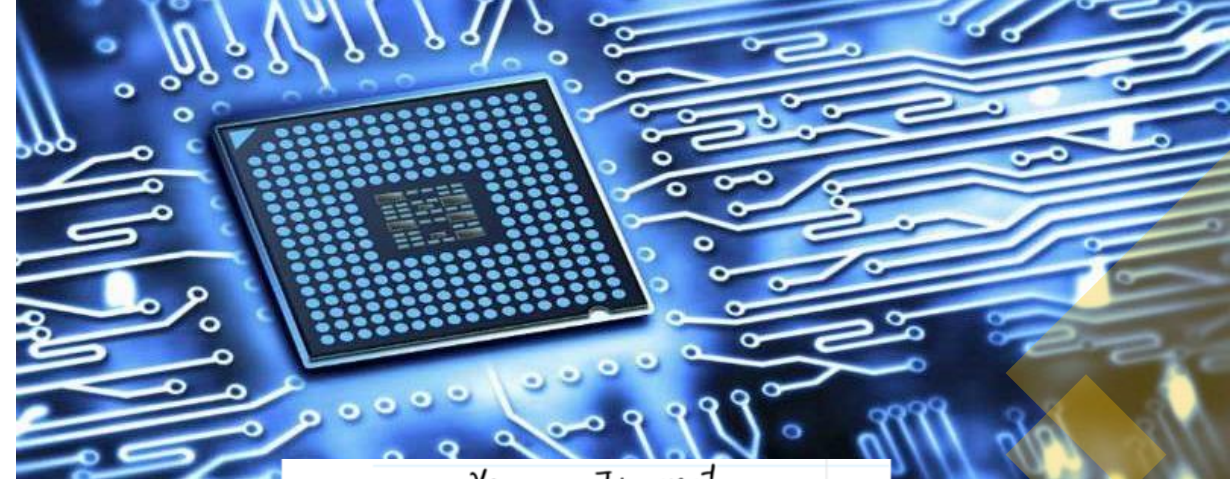


Recap

Elements and Sources in Series/Parallel


Series Connection:

Idea: same current, voltage is divided

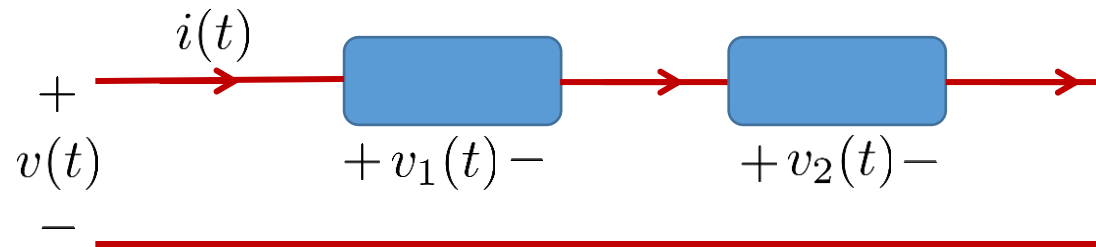


Parallel Connection:

Idea: same voltage, current is divided

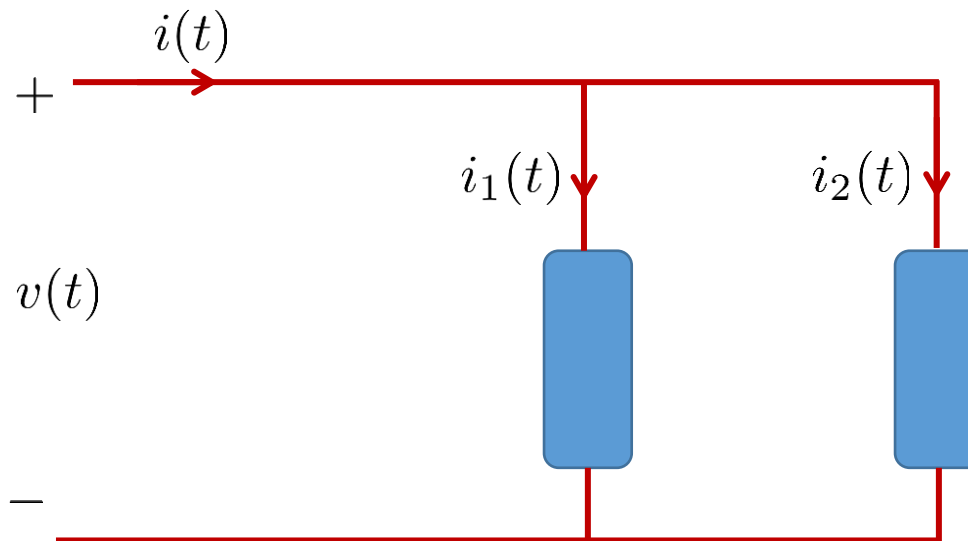

Voltage Sources in Series

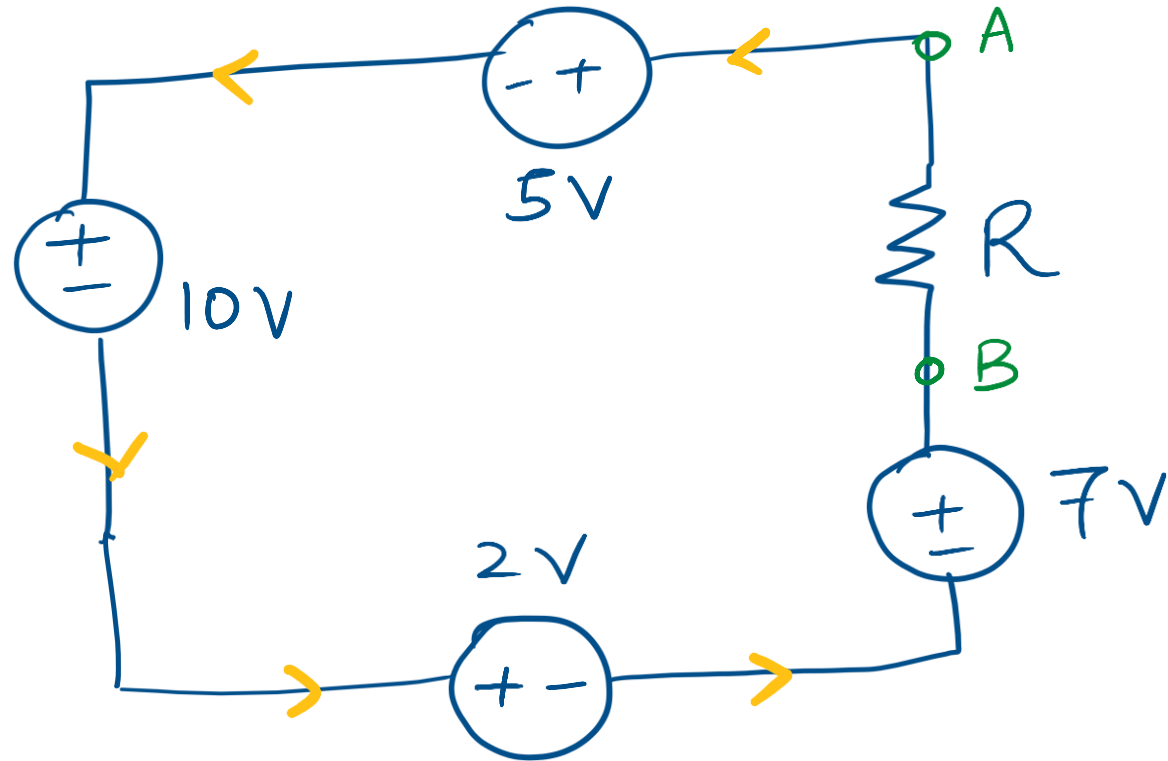Voltage sources in series can be represented with an equivalent single voltage source.





* Let's traverse from A to B.
* Drop of $5 + 10 + 2 = 17V \Rightarrow$ Net Drop $= 10V$
* Gain of $7V =$ Drop of $-7V$

Voltage Sources in Parallel

Q: Determine the internal resistance of the ideal voltage source?

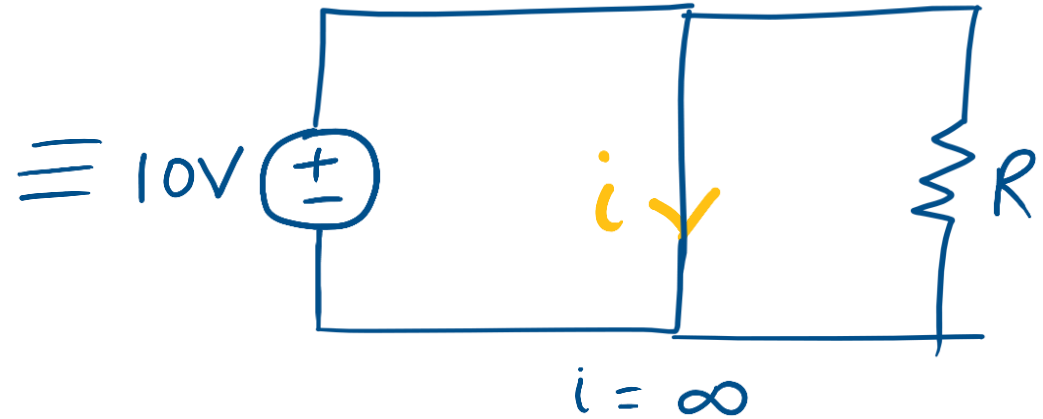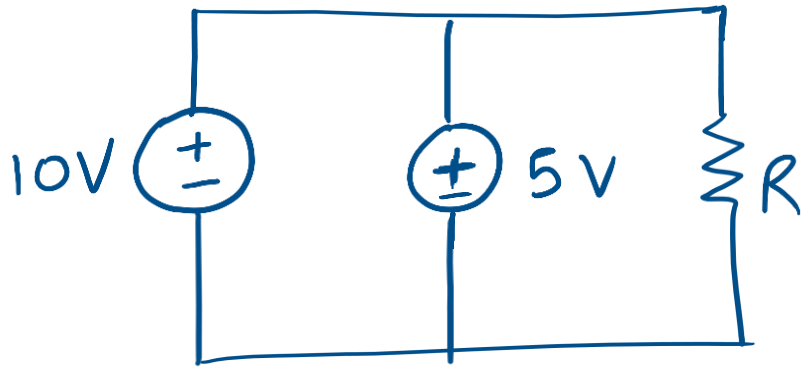A: Zero resistance (How? Analyze i - v characteristics)




* Infinite current flow due to zero resistance

Voltage sources are **NOT** connected in parallel **except** for the case when both sources have the same voltage level. For circuit analysis, voltage sources of same voltage level, connected in parallel, can be replaced with a single voltage source.

Current Sources in Parallel

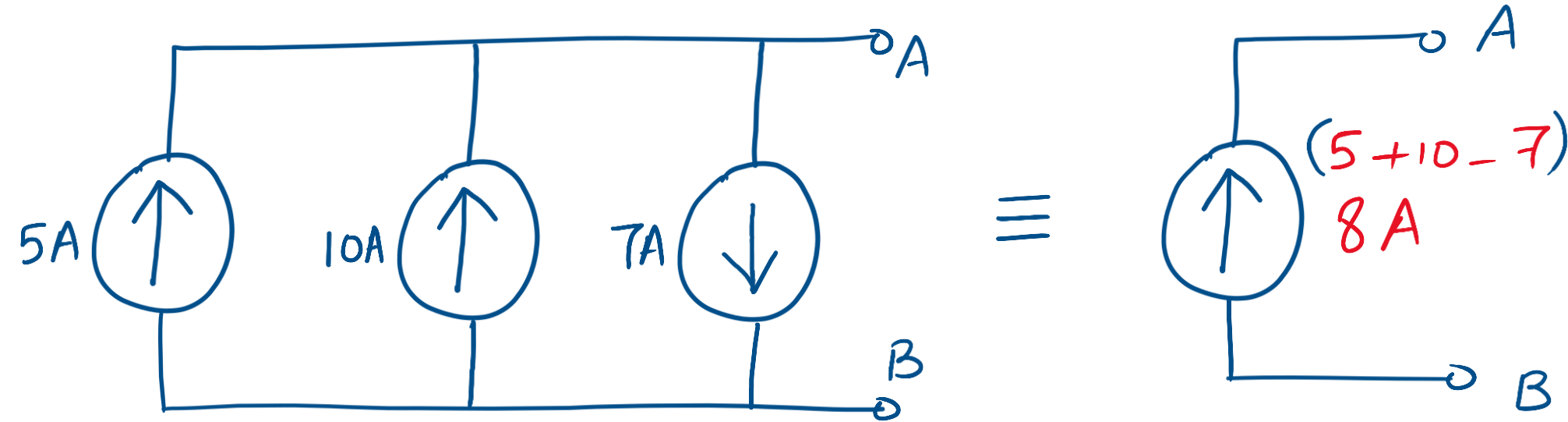Current sources in parallel can be represented with an equivalent single current source.



- * 5A and 10A is being fed to terminal A
- * 7A is being drawn from terminal A.


Current Sources in Series

Q: Determine the internal resistance of the ideal current source?

A: *Infinite* resistance (How? Analyze $i-v$ characteristics)

In other words,

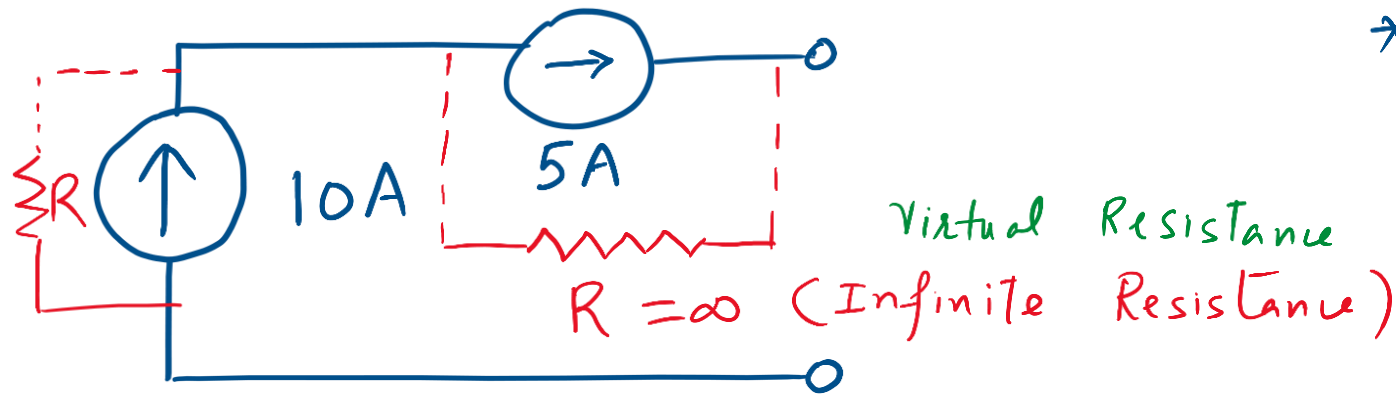- Ideal current source with zero current is equivalent to **open circuit**.
- Voltage across the current source depends on the circuit it is connected to.



* If KCL is to be satisfied, 5A current flow through infinite resistance due to which infinite voltage develops across a source.

Current sources are **NOT** connected in series **except** for the case when both sources have the same current rating (value + direction).
For circuit analysis, current sources of same value, connected in series, can be replaced with a single current source.


Current Sources in Series

Q: Determine the internal resistance of the ideal current source?

A: *Infinite* resistance (How? Analyze $i-v$ characteristics)

In other words,

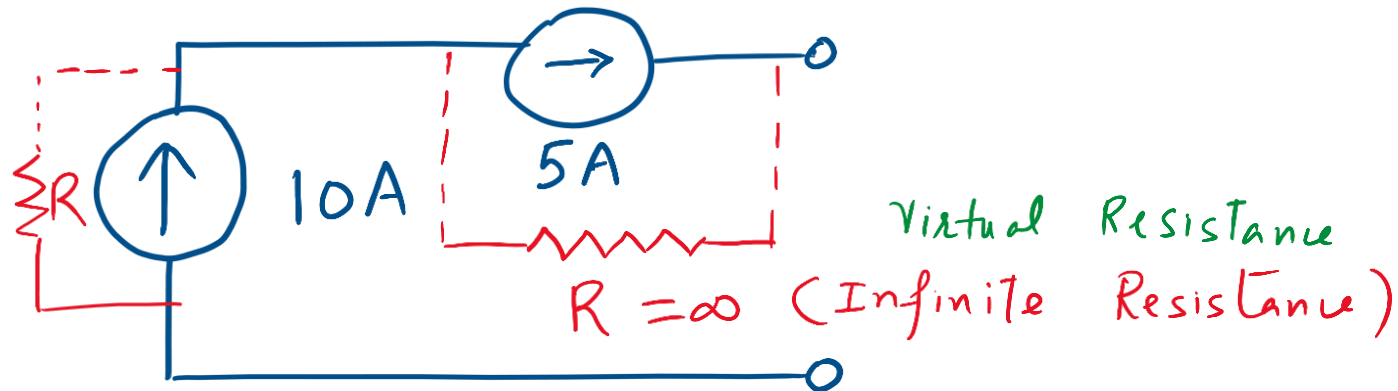
- Ideal current source with zero current is equivalent to **open circuit**.
- Voltage across the current source depends on the circuit it is connected to



Current sources are **NOT** connected in series **except** for the case when both sources have the same current rating (value + direction).


For circuit analysis, current sources of same value, connected in series, can be replaced with a single current source.

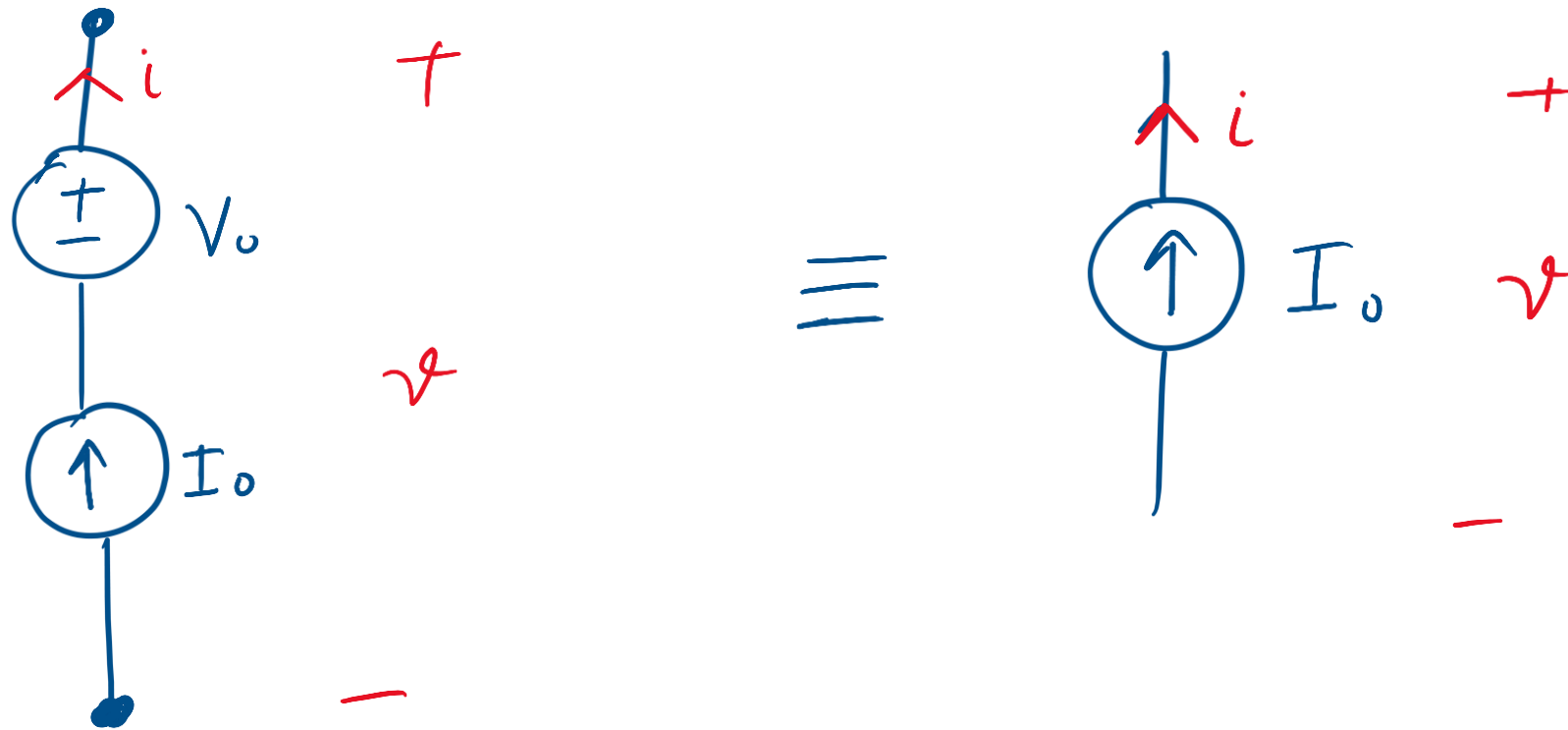Current Source and Voltage Source in Series




* Note here that $i = I_0$ for any value of v
* But these are the characteristics of a current source.

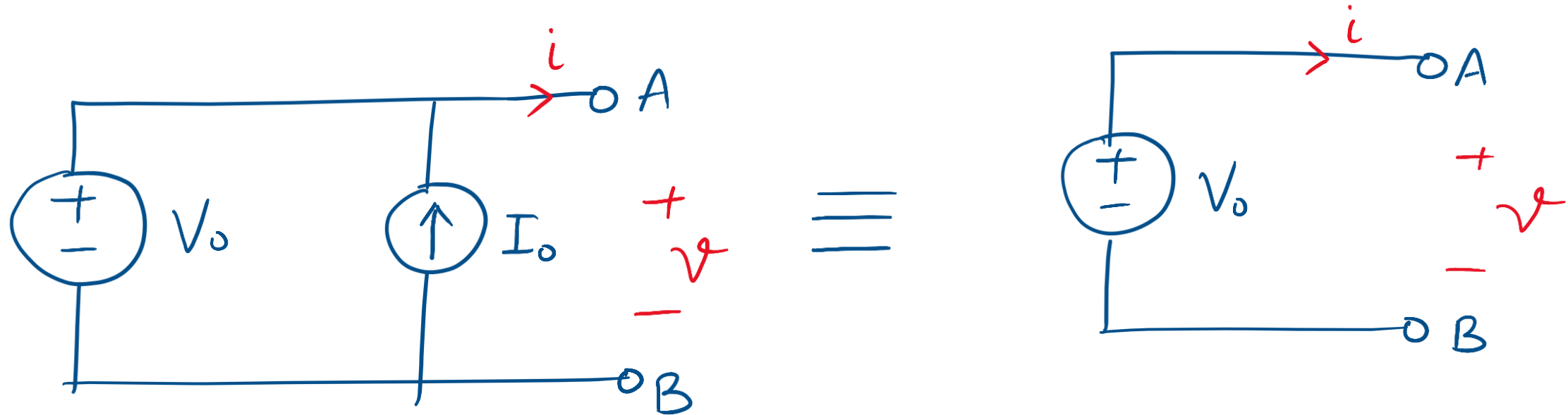Current Source and Voltage Source in Parallel




* $v = V_0$ for any value of i


Practical Models – Voltage Source

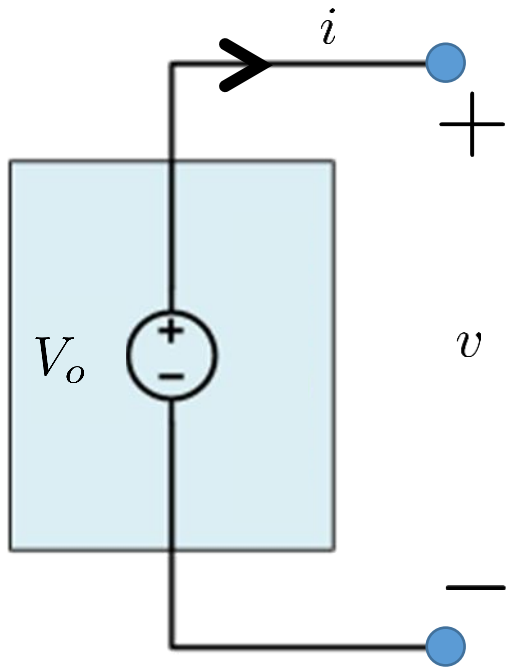

Ideal Voltage Source

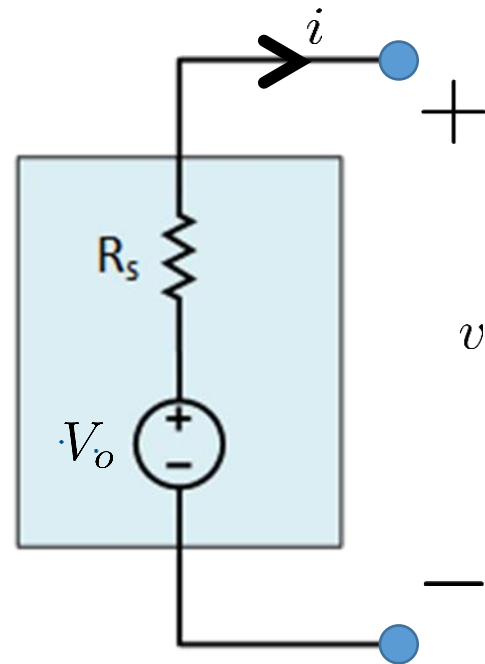

**Practical Voltage Source
(Model)**

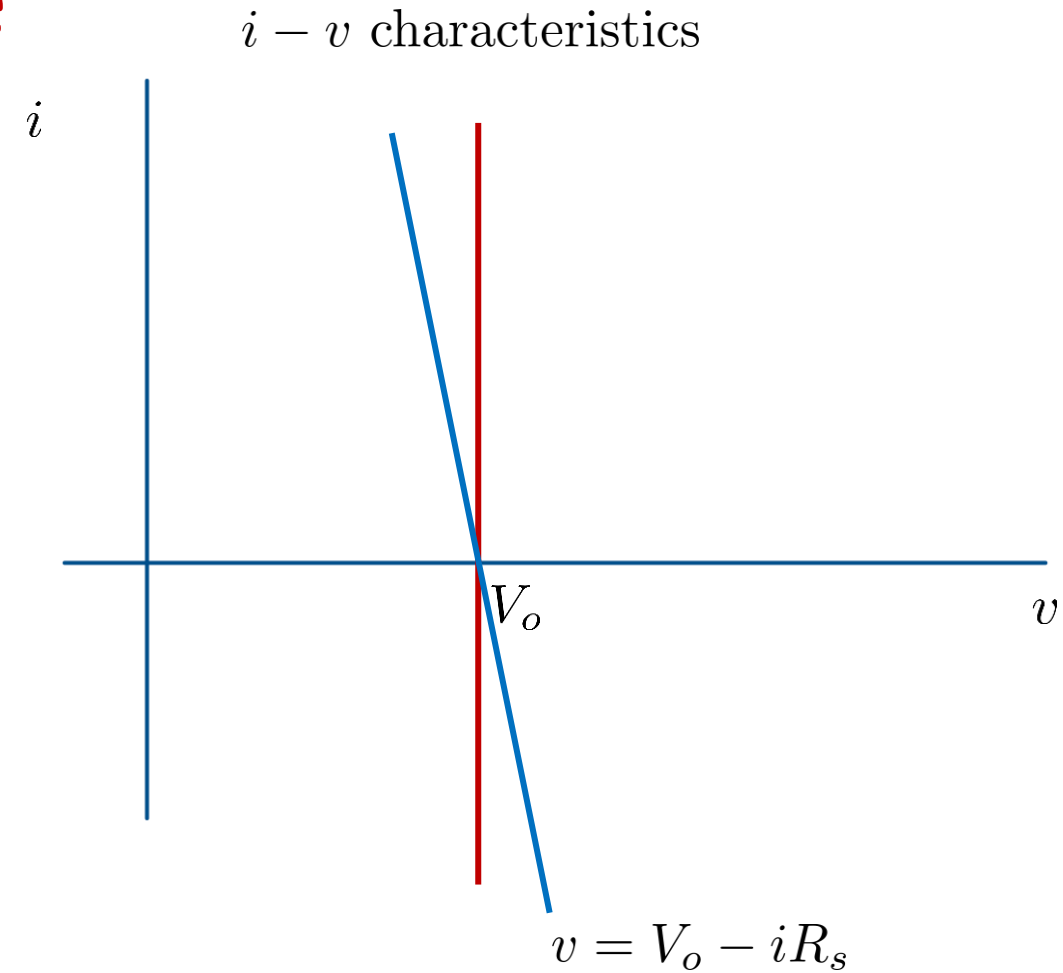


Practical voltage source: ideal voltage source with resistance R_s in series.


Consequence: Voltage drops with the increase in current across the terminals.

Practical Models – Current Source


$i - v$ characteristics

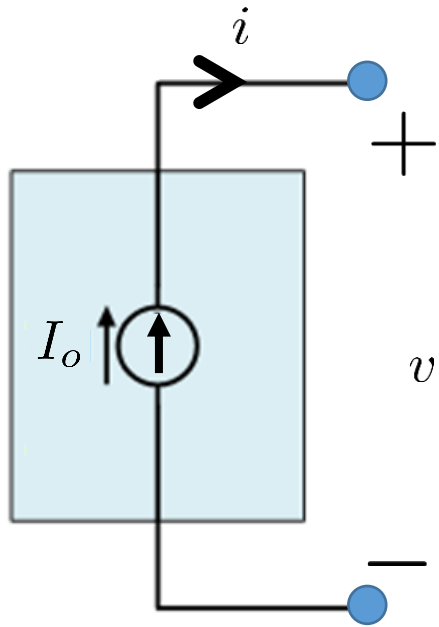

Ideal Current Source

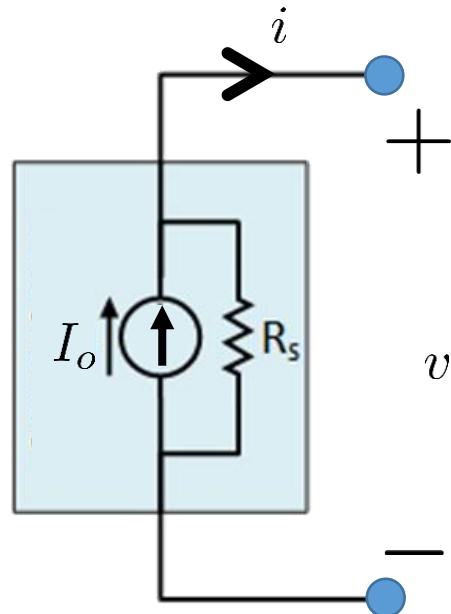

**Practical Current Source
(Model)**

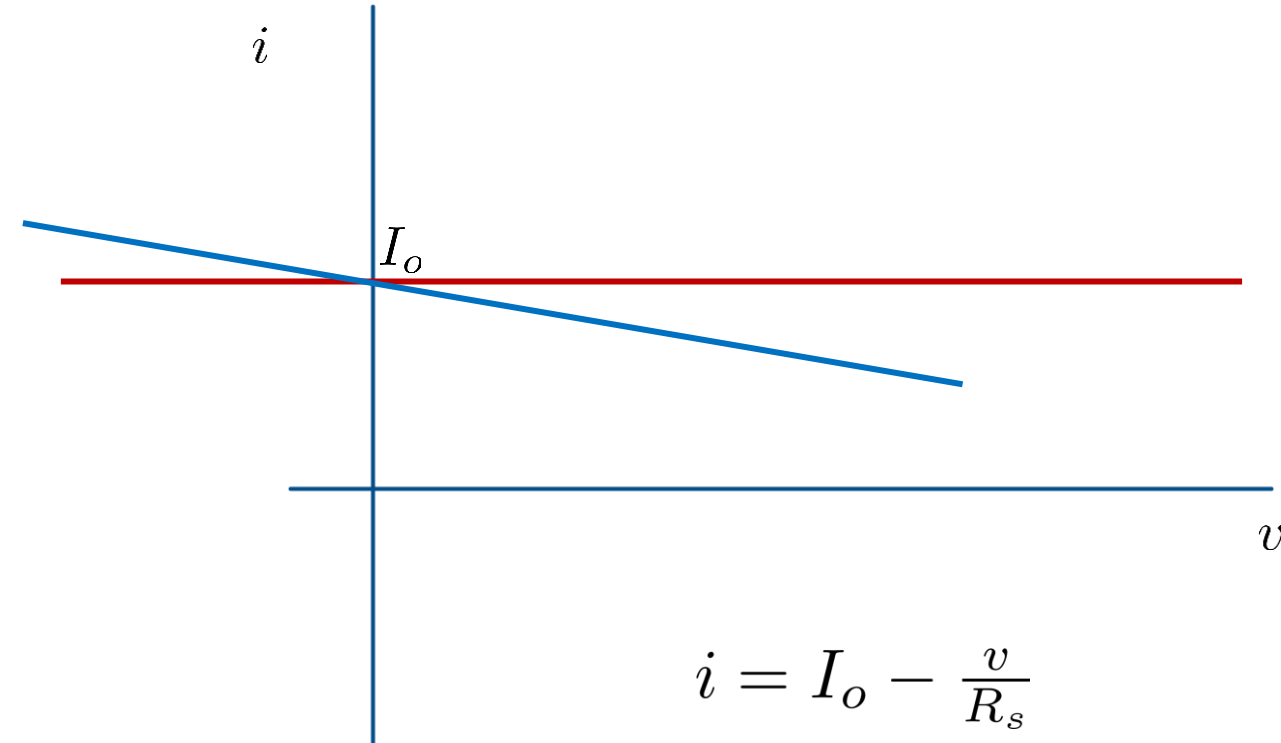


$$i = I_o - \frac{v}{R_s}$$

Practical current source: ideal current source with large resistance R_s in parallel.

Consequence: current drops with the increase in the voltage across the terminals.

Voltage and Current Divider Rules


Voltage Divider:

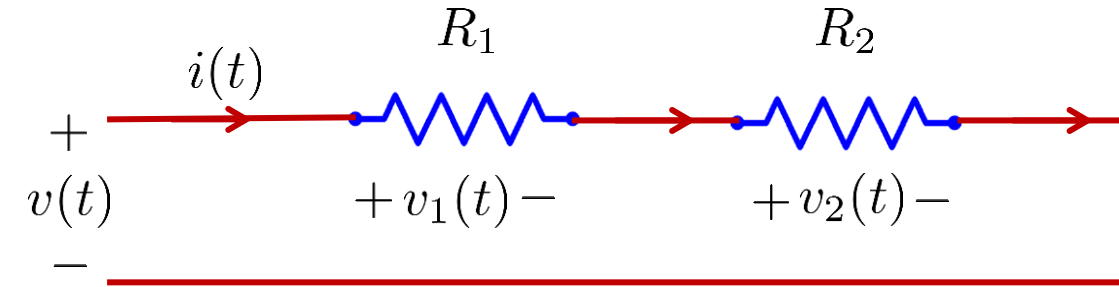

$$v_1(t) = \frac{R_1}{R_1 + R_2} v(t)$$

$$v_2(t) = \frac{R_2}{R_1 + R_2} v(t)$$

Current Divider:

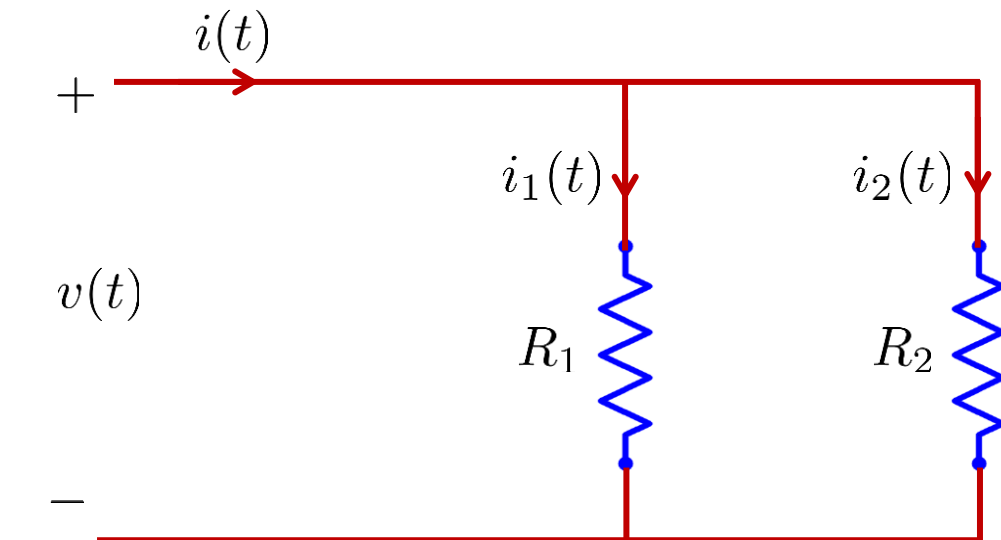


$$i_1(t) = \frac{R_2}{R_1 + R_2} i(t)$$

$$i_2(t) = \frac{R_1}{R_1 + R_2} i(t)$$

Equivalent Resistance

Examples:

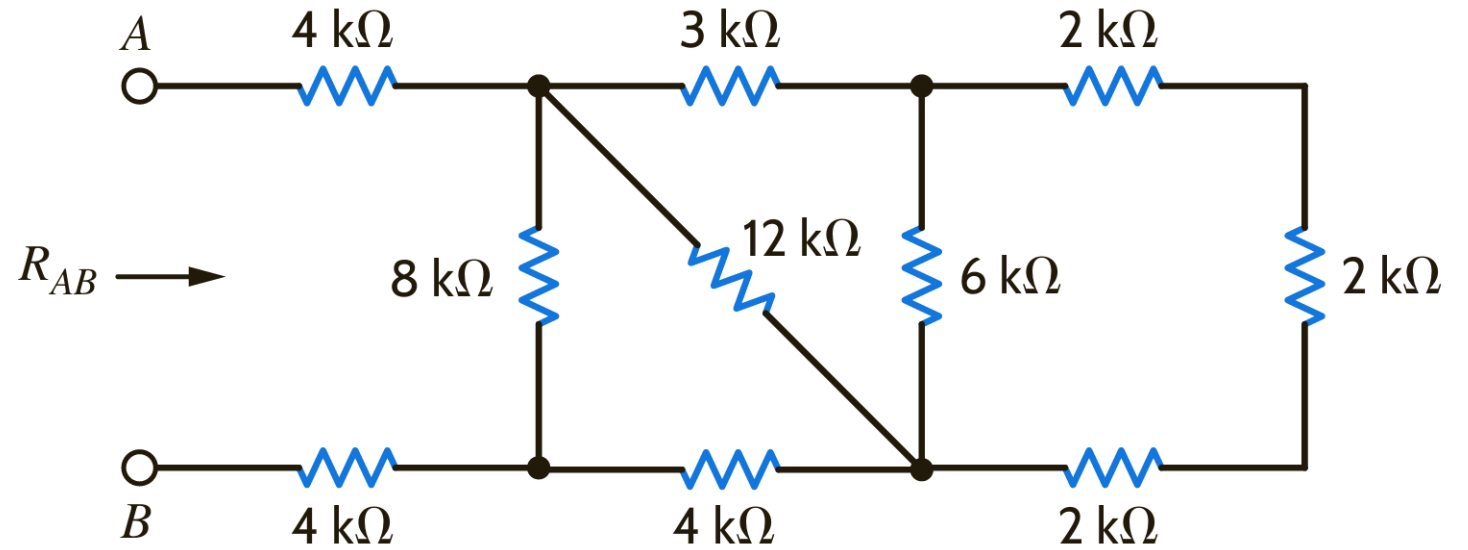

$$R_{\text{eq}} = 4\text{k} + 4\text{k} + 8\text{k} \parallel \left(4\text{k} + 12\text{k} \parallel \left(3\text{k} + 6\text{k} \parallel (2\text{k} + 2\text{k} + 2\text{k}) \right) \right) = 12\text{ k}\Omega$$

Equivalent Resistance

Circuit-Analysis Example:

