



EE 240 Circuits I

Dr. Zubair Khalid

Department of Electrical Engineering
School of Science and Engineering

Lahore University of Management Sciences

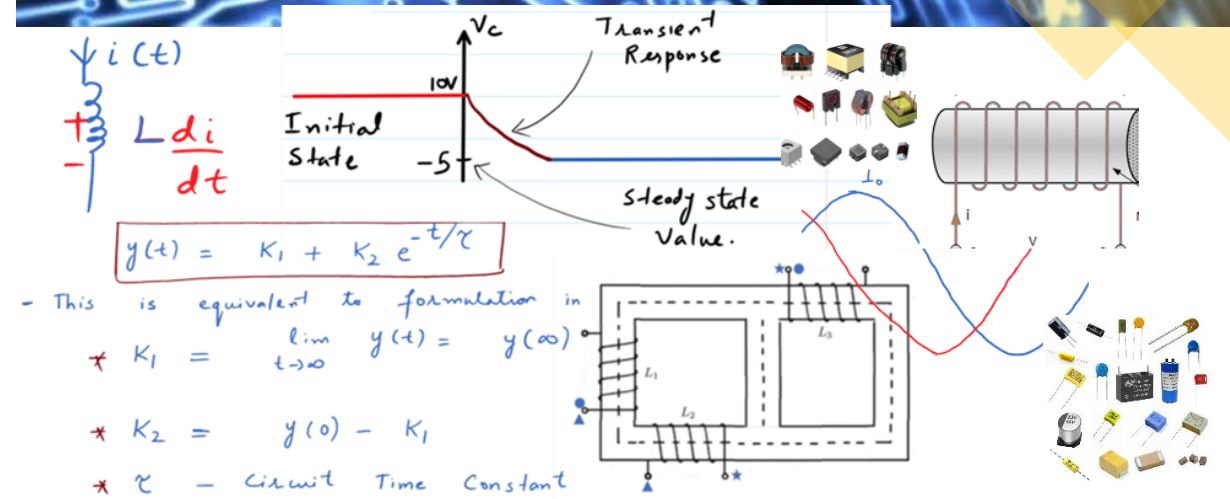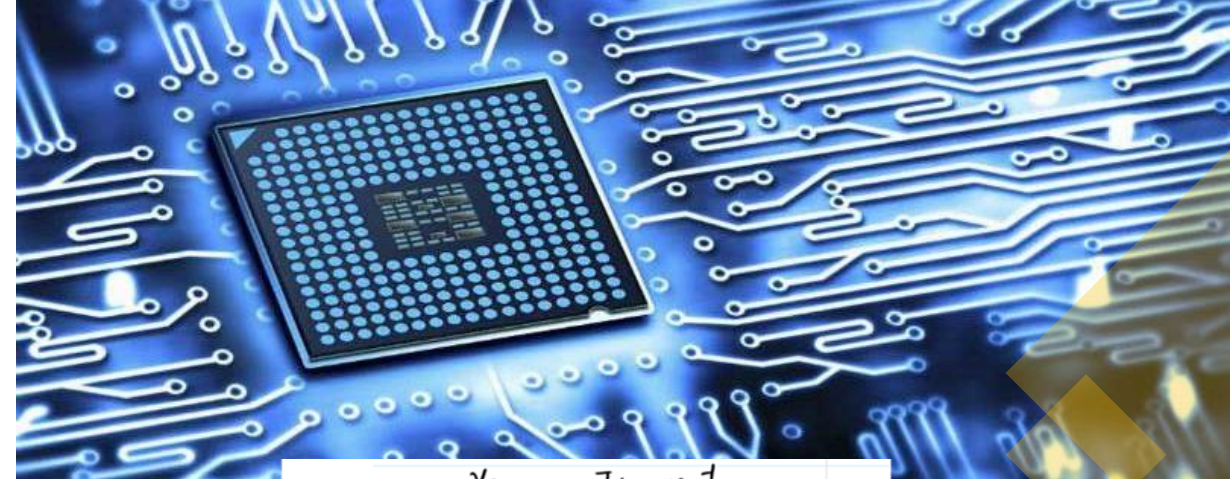- Loop Analysis
- Super Loop
- Additional Analysis Techniques





Loop Analysis using Kirchhoff's Voltage Law

Circuits Involving Independent Voltage Sources:

$$* -12 + 6K(I_1 + I_2) + 6K(I_1) = 0$$
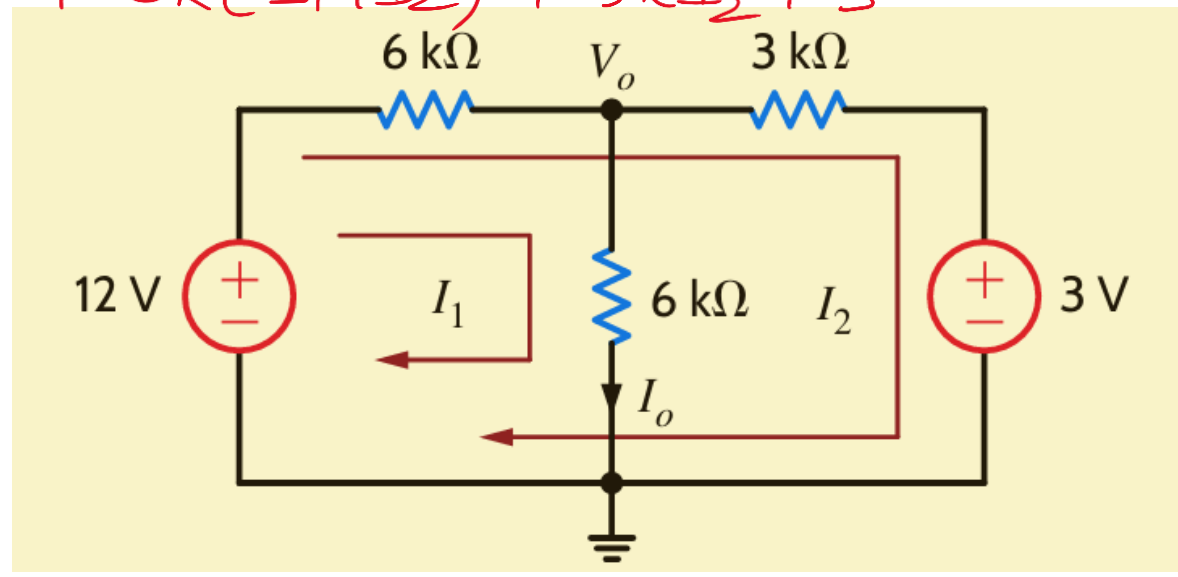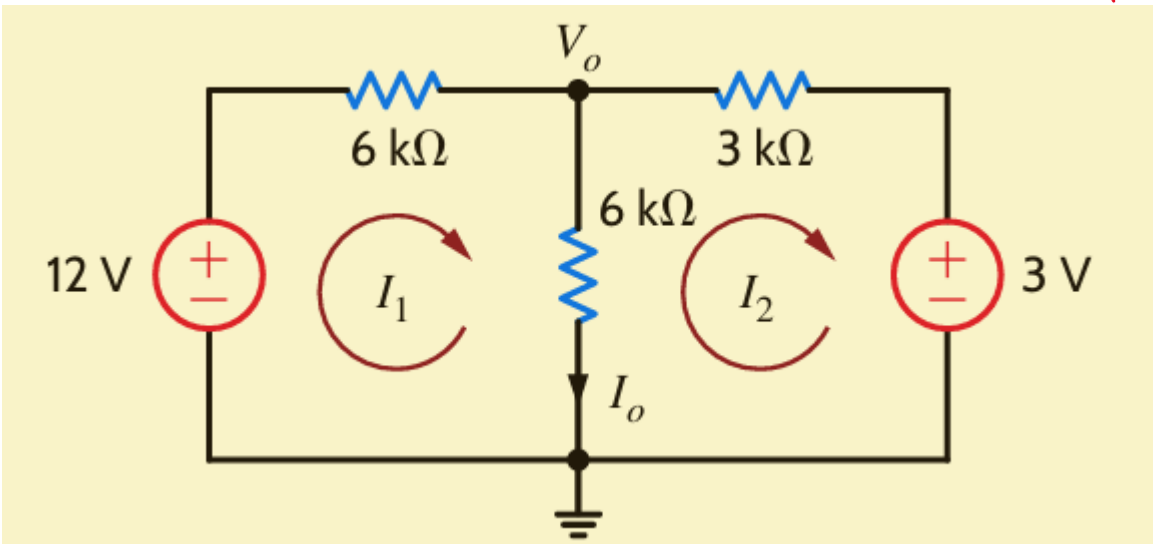
$$* -12 + 6K(I_1 + I_2) + 3KI_2 + 3 = 0$$



Independent loop: if loop traverses at-least one element that is not part of any other loop

Loop Analysis using Kirchhoff's Voltage Law

Circuits Involving Independent Current Sources:

$$* I_1 = 4 \text{ mA}$$


$$* I_2 = -2 \text{ mA}$$

$$* -4 + 1\text{k}(\text{I}_3 - \text{I}_1) + 4\text{k} \text{I}_3 = 0$$

$$\underline{\underline{\text{I}_3 = 1.6 \text{ mA}}}$$

$$V_o = (1.6)(4) = 6.4 \text{ V}$$
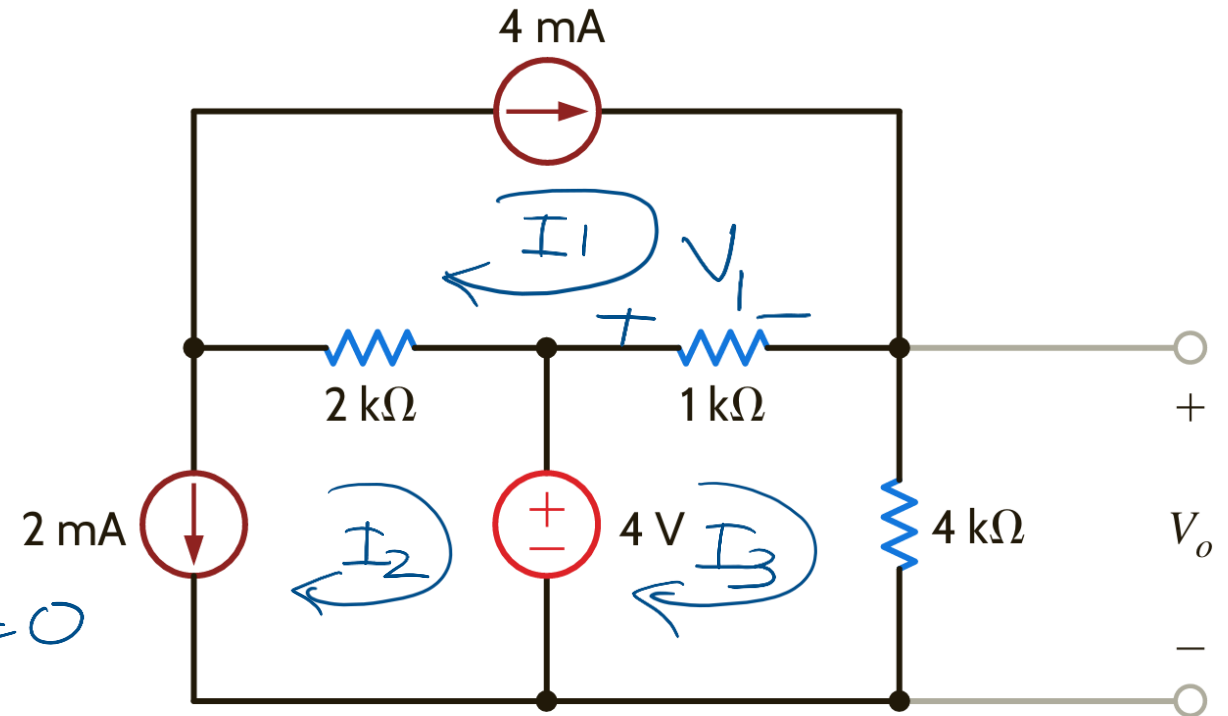
$$V_1 = 1\text{k}(\text{I}_3 - \text{I}_1) = -2.4 \text{ V}$$



$$\underline{\underline{V_o + V_1 = 4 \text{ V}}}$$

Loop Analysis using Kirchhoff's Voltage Law

Circuits Involving Independent Current Sources and Super-Loop:

Choice of loop currents


$$* I_2 = 2 \text{ mA}$$

$$* 3 \text{ k}\Omega I_1 + 4 \text{ k}\Omega (I_1 + I_2) - 12$$

$$+ 6 \text{ k}\Omega (I_1 + I_3) - 10$$

$$+ 2 \text{ k}\Omega I_1 = 0$$
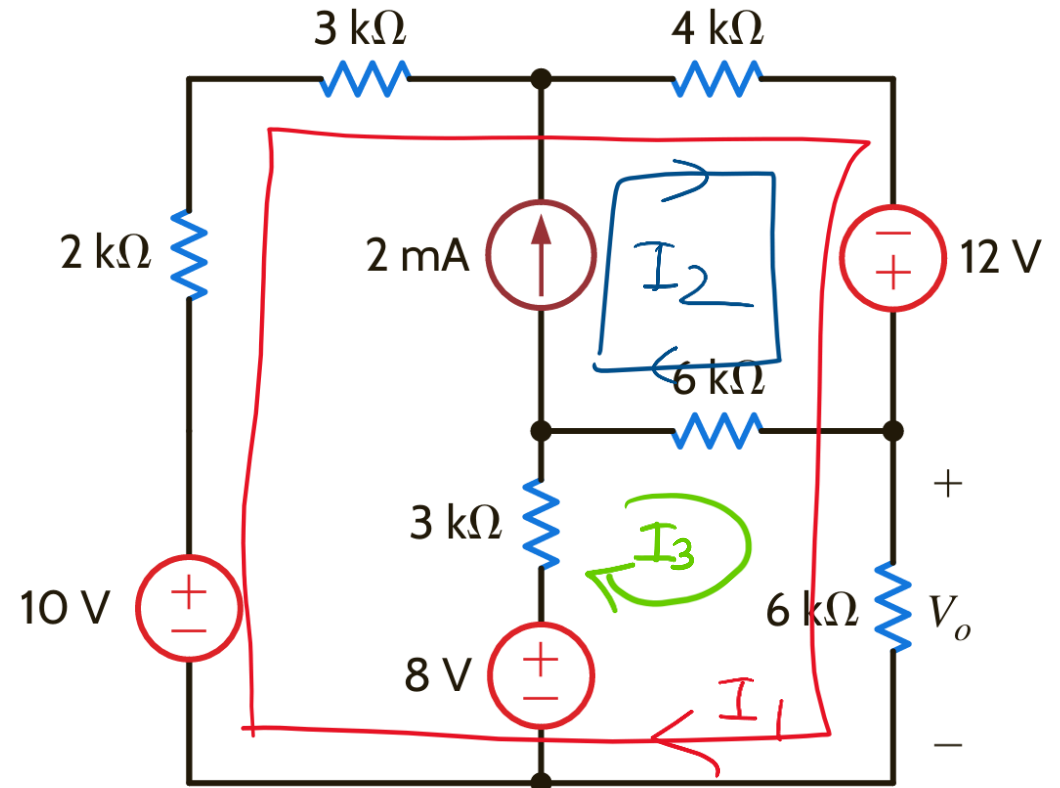
$$* 6 \text{ k}\Omega (I_3 - I_2) + 6 \text{ k}\Omega (I_3 + I_1) - 8 + 3 \text{ k}\Omega I_3 = 0$$



Loop Analysis using Kirchhoff's Voltage Law

Circuits Involving Independent Current Sources and Super-Loop:

Now let's learn and apply the concept of Super-Loop:

$$5K I_1 + V_1 + 3K(I_1 - I_3) + 8 - 10 = 0$$

$$4K I_2 + 6K(I_2 - I_3) - V_1 - 12 = 0$$

01

$$5K I_1 + 4K I_2 - 12 + 6K(I_2 - I_3)$$


$$+ 3K(I_1 - I_3) + 8 - 10 = 0$$

02

$$* 6K(I_3 - I_2) + 6K I_3 - 8 + 3K(I_3 - I_1) = 0$$

03

$$I_2 - I_1 = 2m$$

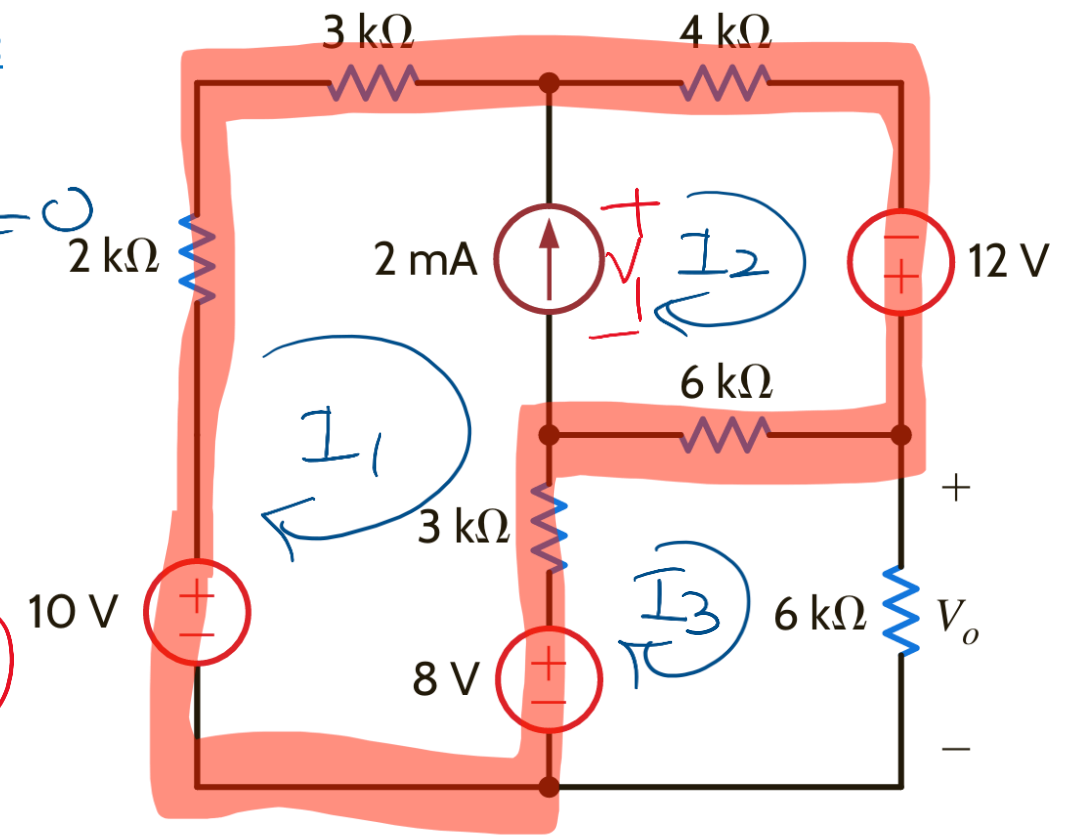

KCL, KVL – Number of Equations

Connection with graphical representation

We analyse the electric circuit by forming network equations governed by KCL and KVL.

We should learn to use these laws *intelligently* to formulate *minimum* number of *independent* equations describing the network *completely*.

KCL – Nodal Analysis

KVL – Loop Analysis

To determine the number of equations obtained by using KCL or KVL, we use the graphical representation of the circuit.

For a circuit with n nodes and b branches (or edges)

- KCL: number of equations = $n-1$
- KVL: number of equations = $b-(n-1)$


For a circuit with p parts

- KCL: number of equations = $n-1+(p-1)$
- KVL: number of equations = $b-(n-1)+(p-1)$

Recall $b-(n-1)$ represents the number of chords to be removed from the graph of the circuit to obtain its tree.

Nodal or Loop Analysis

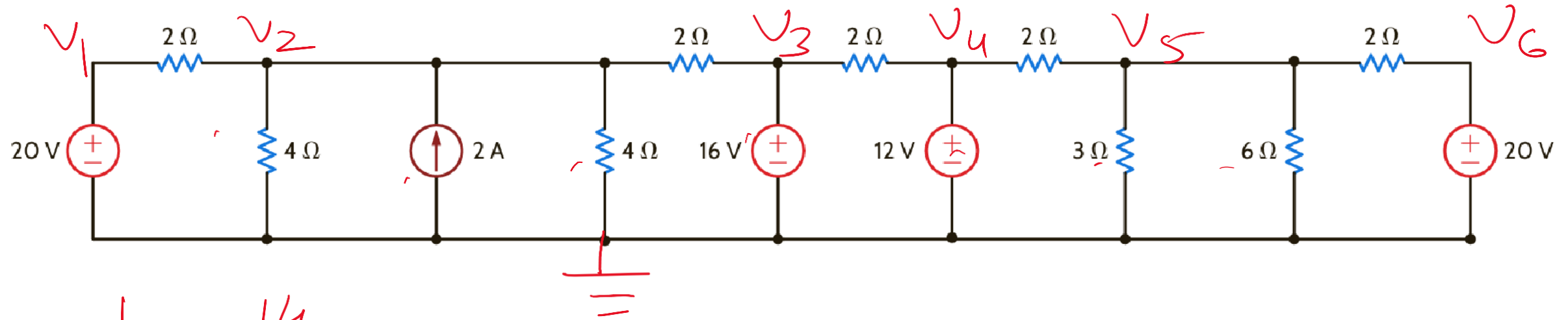Circuits Involving Independent Current Sources and Super-Loop:



* $b = 14$

* $n = 7$

Nodal; 6

Loop; 8

* V_1, V_3, V_4, V_6 are known

* Only 2 equations are needed
to find V_2 and V_5

Equivalent Networks

Concept:

Two networks are equivalent at a pair of terminals if the current and voltage have a same relationship at these terminals.

We had been dealing with this concept in the course. For example,

- Resistors/Capacitors/Inductors in Series or Parallel
- Current sources in parallel
- Voltage sources in series

Now we are going to learn the following techniques to obtain an equivalent network to facilitate the analysis of the circuits.


- Removing Extra Element
- Source Transformation
- Moving Sources

Equivalent Networks

Removing Extra Element


Idea: As far circuit analysis is concerned, we can remove a circuit element if it is appearing in parallel to the voltage source or in series to the current source.

Element in series to the current source:

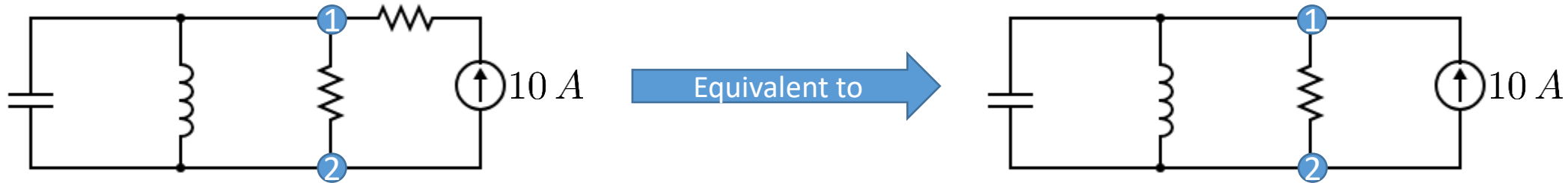

10A is being fed to node 1 and 10A is being drawn from the node 2.

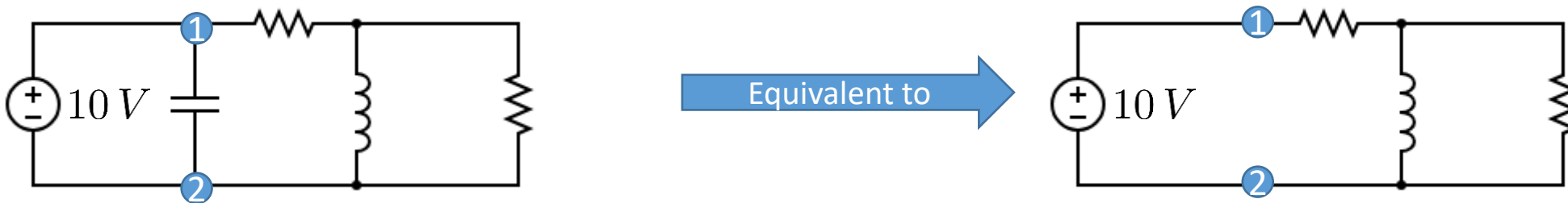
Element in parallel to the voltage source:



10V is the voltage across the nodes (terminals) 1 and 2.

Equivalent Networks

Source Transformation:

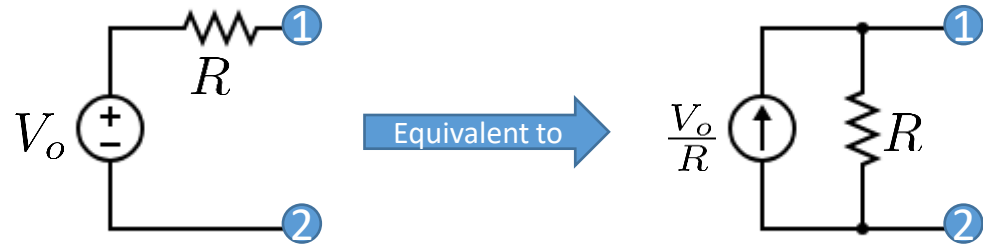


Show Equivalence:

Using KVL

$$iR + v(t) - V_o = 0$$


Using KCL
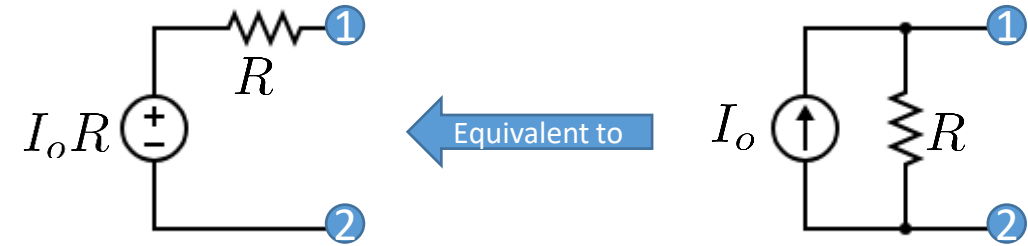
$$i + \frac{v(t)}{R} - \frac{V_o}{R} = 0$$



Idea: Voltage source and element in series can be transformed as current source with element in parallel.


Similarly:

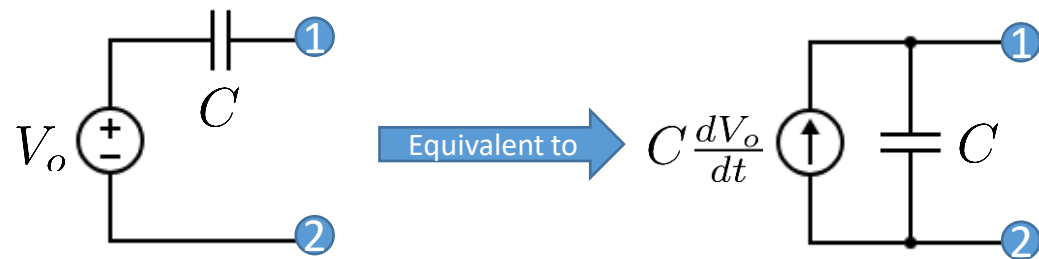



Source Transformation

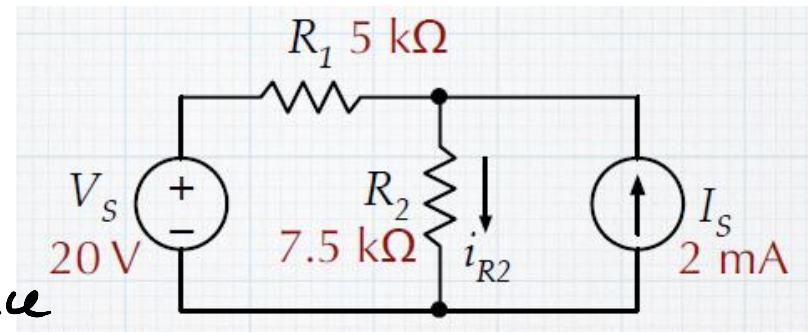Example

Determine I_{R_2} using source transformation.



Source transformation of voltage source

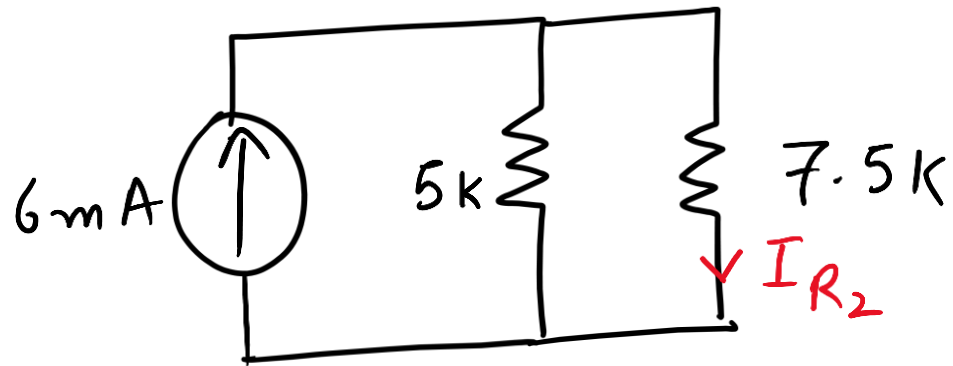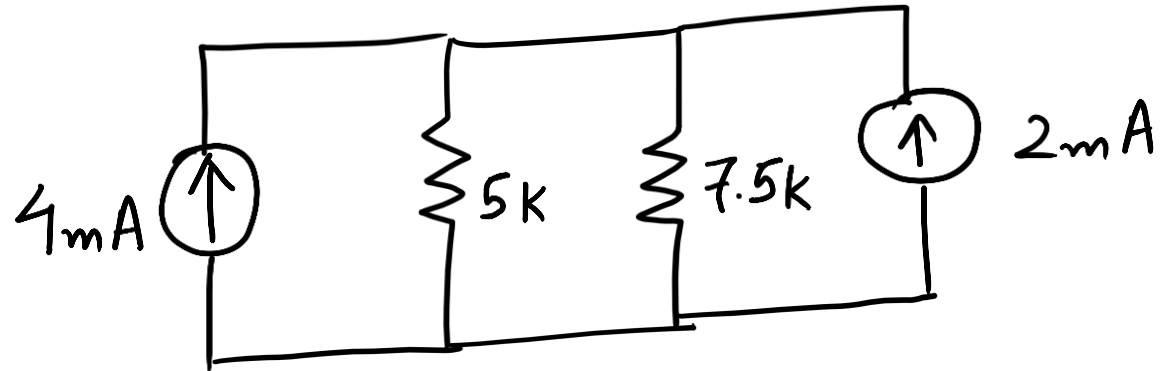


Applying current division rule;

$$I_{R_2} = \frac{5\text{ k}}{7.5\text{ k} + 5\text{ k}} \cdot 6\text{ m} \\ = \underline{2.4\text{ mA}}$$



Equivalent Networks

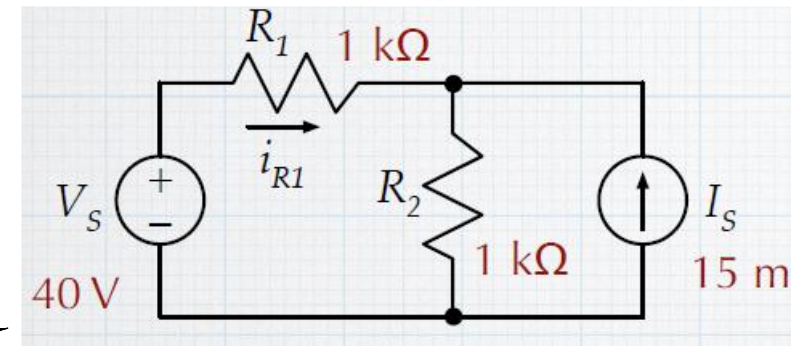Example

Determine I_{R_1} using source transformation.



Source Transformation of current source

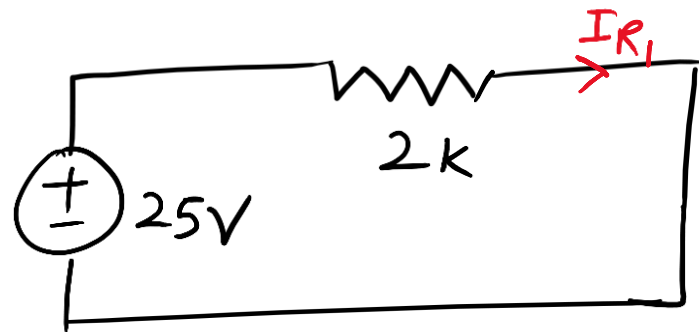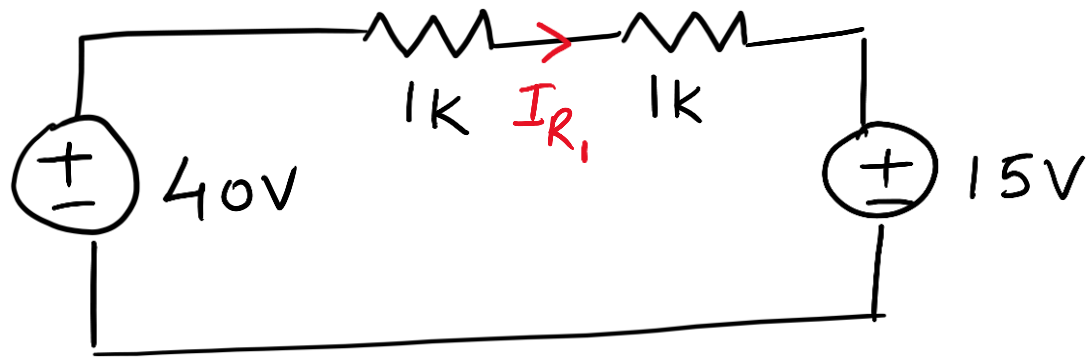

$$I_{R_1} = \frac{25}{2k} = \underline{12.5 \text{ mA}}$$


Caution: Do not apply source transformation using an element for which we are finding current or voltage.

Equivalent Networks

Moving Sources

Voltage Source: Move (Push) through a node

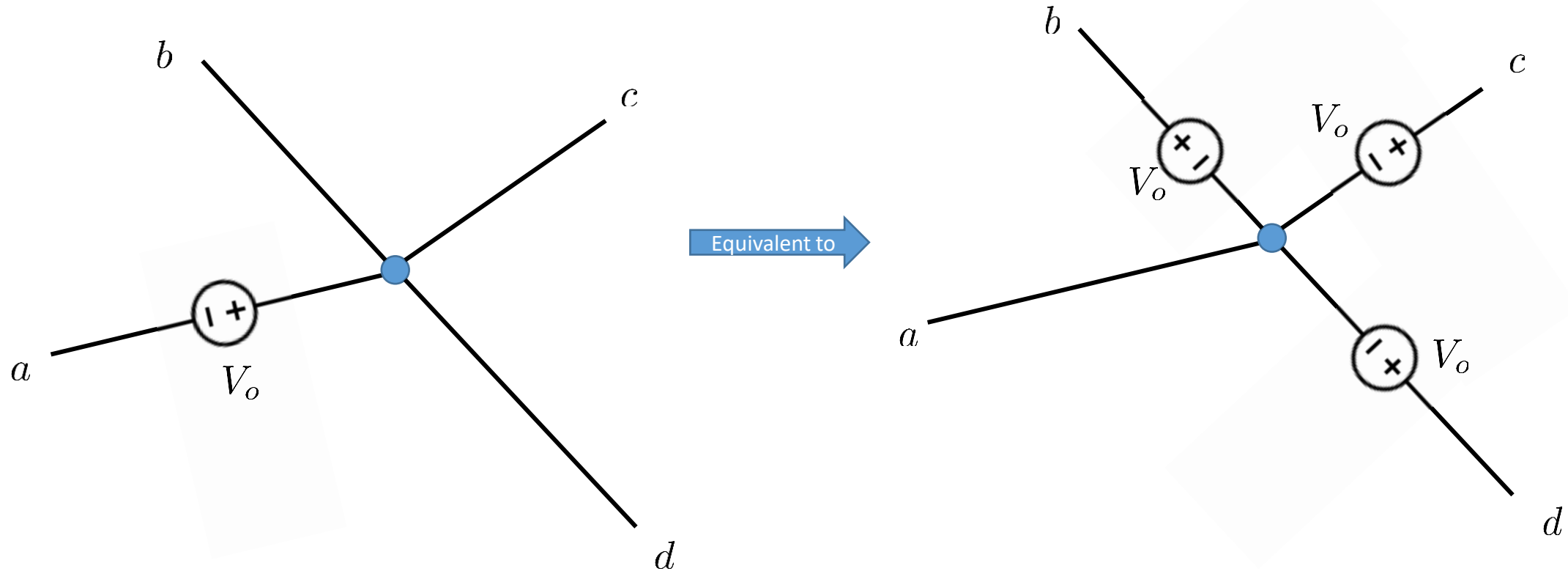Consider a node of the circuit with 4 branches connected to the node.




Idea: When voltage source is pushed from one branch through the node, it appears in every other branch connected to the node.

$$V_{ba} = V_{ca} = V_{da} = V_o$$

Equivalent Networks

Moving Sources

Current Source: Move around a node

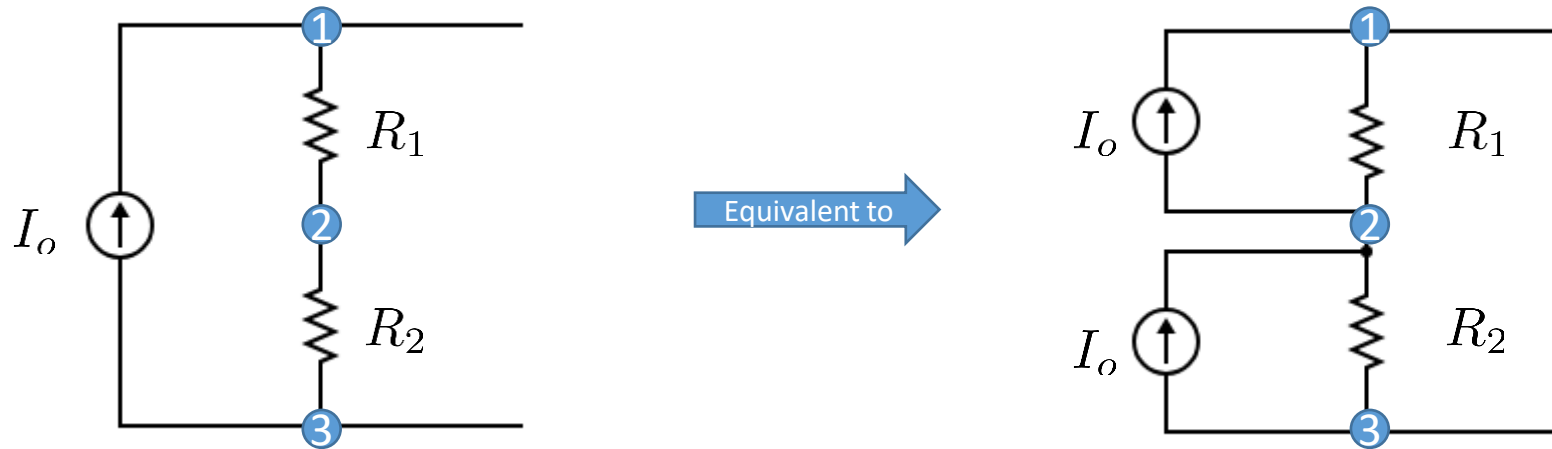


Current being fed (or drawn) to Node 1 (from Node 3) stays the same.

Idea: Drawing the amount of current and feeding the same amount of current from the node does not change the circuit.

Equivalent Networks

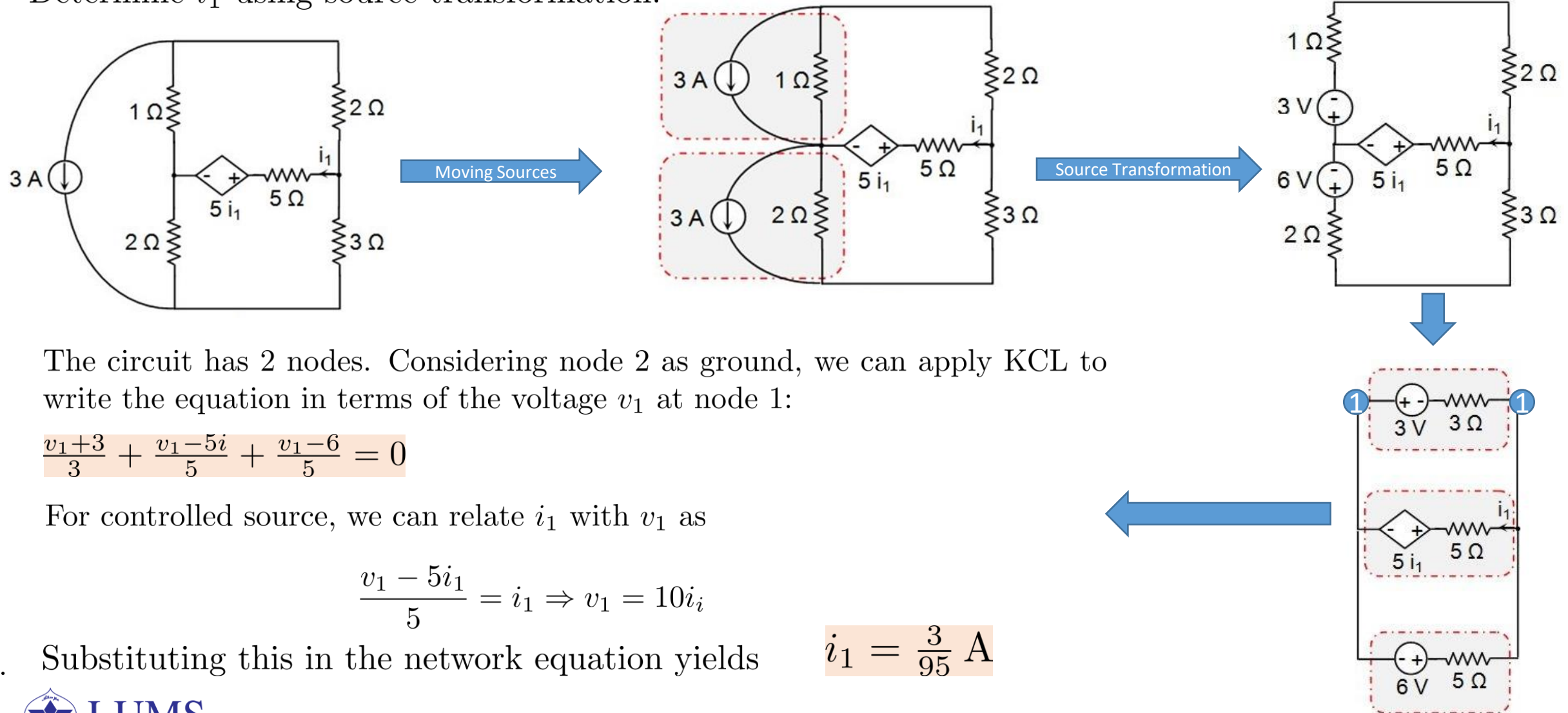Example (illustrate moving sources + source transformation)

Determine i_1 using source transformation.



The circuit has 2 nodes. Considering node 2 as ground, we can apply KCL to write the equation in terms of the voltage v_1 at node 1:

$$\frac{v_1 + 3}{3} + \frac{v_1 - 5i_1}{5} + \frac{v_1 - 6}{5} = 0$$

For controlled source, we can relate i_1 with v_1 as

$$\frac{v_1 - 5i_1}{5} = i_1 \Rightarrow v_1 = 10i_1$$

Substituting this in the network equation yields

$$i_1 = \frac{3}{95} \text{ A}$$

Superposition Theorem (Principle)


Idea:

In a linear system (circuit), the branch current (or node voltage) due to multiple independent current or voltage sources is equal to the algebraic sum of branch current (or node voltage) due to each/single independent current or voltage source.


Linear circuit: resistors, capacitors, inductors, independent/dependent sources, transformers.

Superposition simply follows from the definition of linearity.

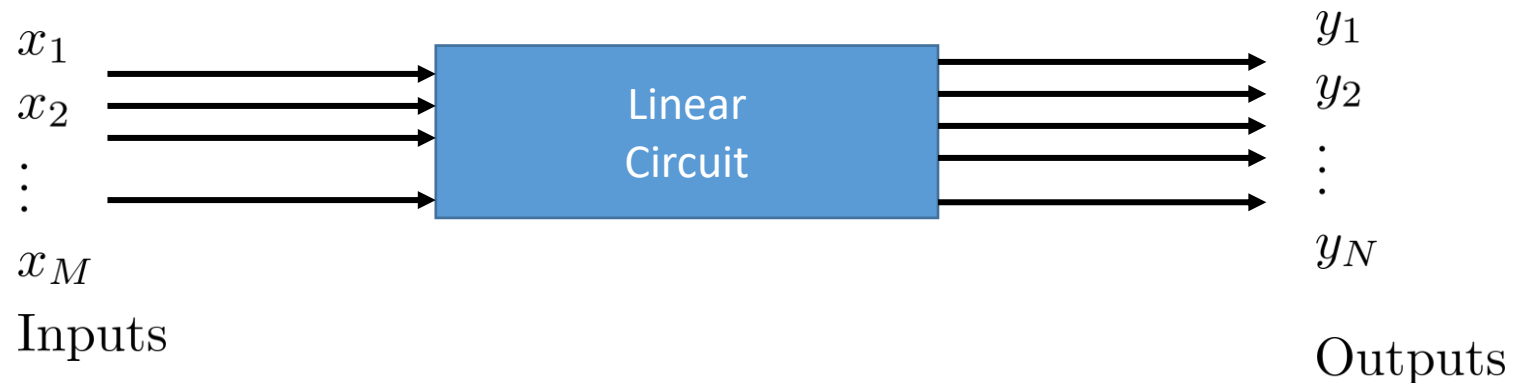A circuit can be considered as a system with inputs as independent sources and outputs representing current through any branch or voltage across any element.



Superposition Theorem (Principle)

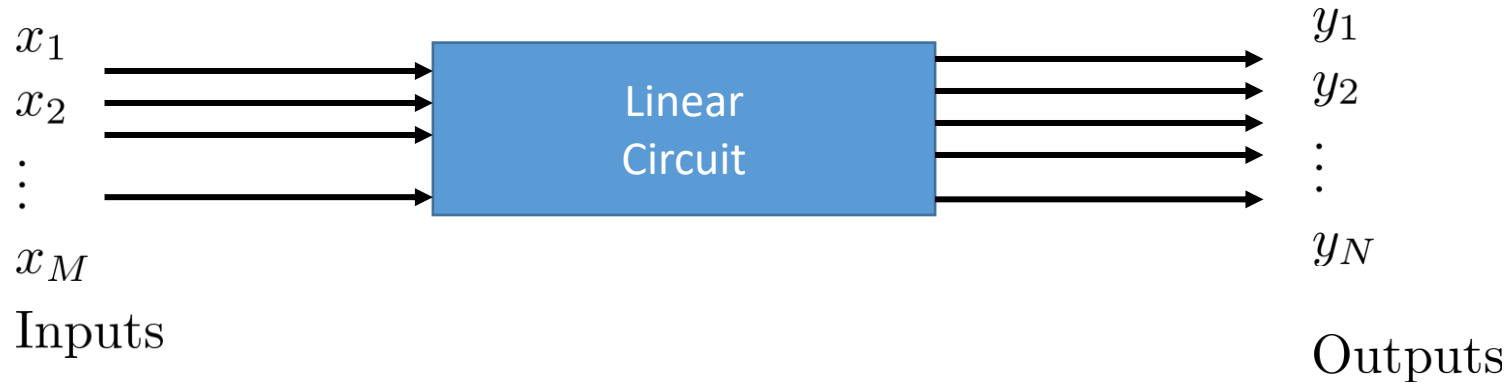

Each output $y_k(t)$ is a linear combination of inputs and/or derivatives of inputs.

Switch off all the inputs except one input, say x_ℓ , and observe the k -th output $y_{k,\ell}$, that is the output y_k when only input x_ℓ is active.

By superposition theorem,

$$y_k = \sum_{\ell=1}^M y_{k,\ell}$$

You only need to know the concept of superposition and obviously how to apply it.



Caution: *Dependent sources stay in the circuit as they are.*

Superposition Theorem (Principle)

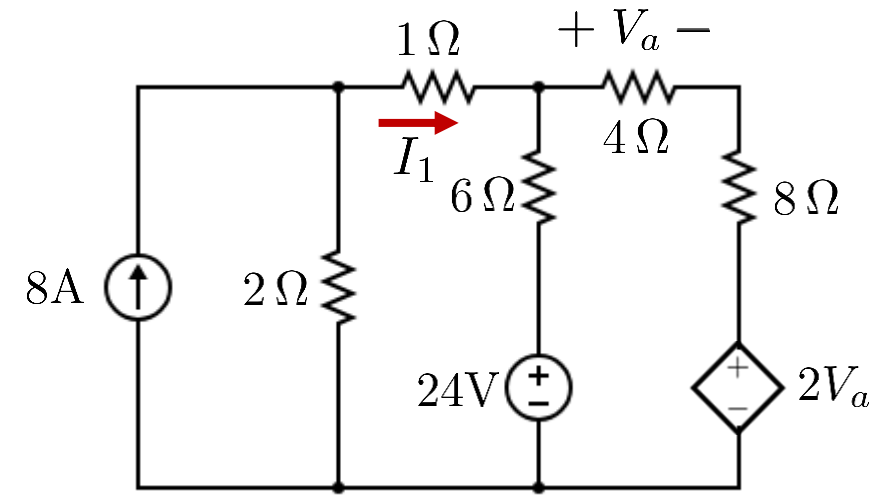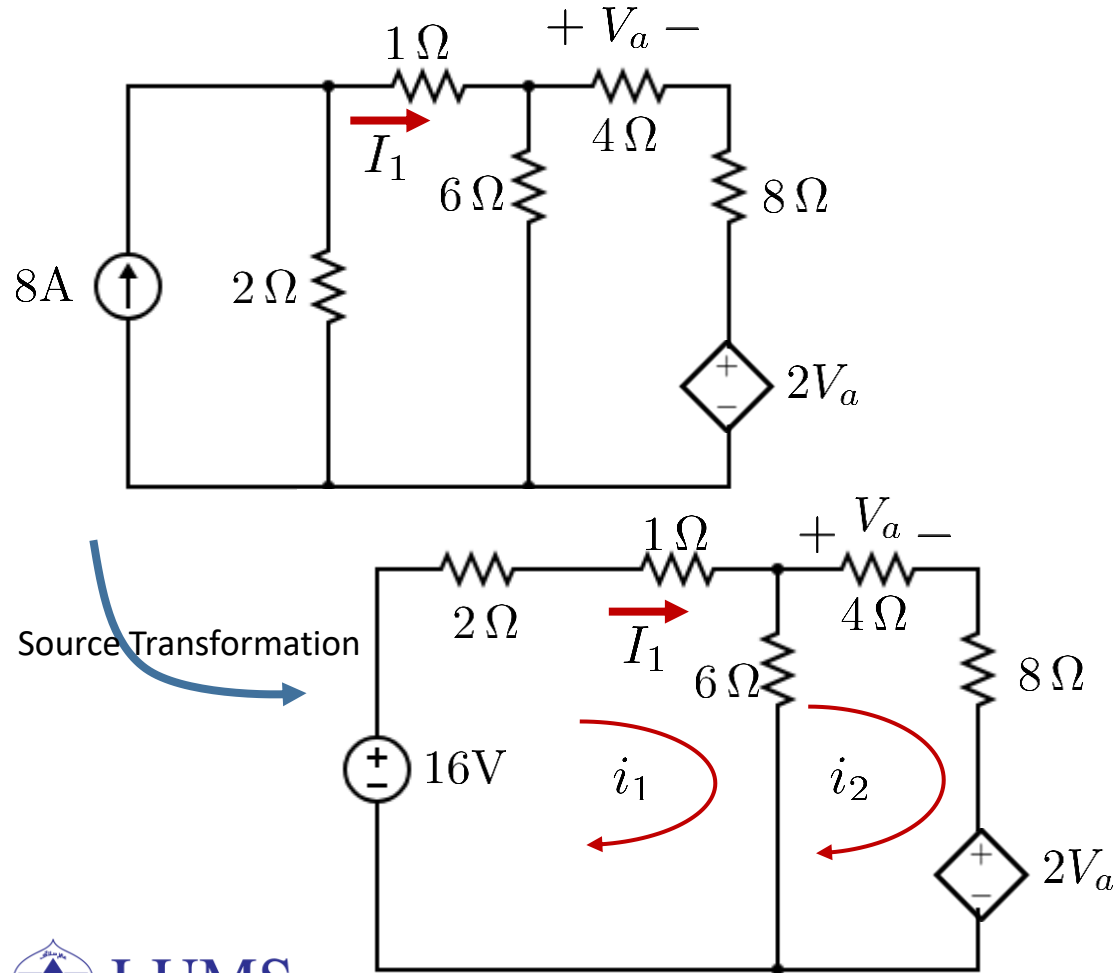Example Determine I_1 using superposition principle.

Keep only 8A source.

Switch off 24V source (replace it with short-circuit).



Loop 1 Equation:


$$9i_1 - 6i_2 = 16$$

Loop 2 Equation:

$$-6i_1 + 18i_2 = -2V_a$$

Controlled source equation:

$$V_a = 4i_2$$

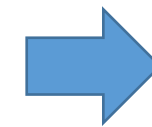

$$6i_1 = 26i_2$$

$$i_1 = \frac{208}{99} \text{ A}$$

$$i_2 = \frac{16}{33} \text{ A}$$

$$I_{1,8A} = i_1 = \frac{208}{99} \text{ A}$$



Superposition Theorem (Principle)

Example

Determine I_1 using superposition principle.

Keep only 24V source.

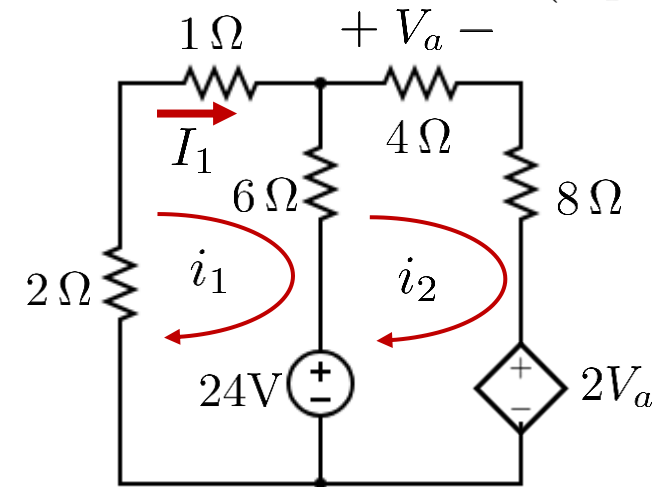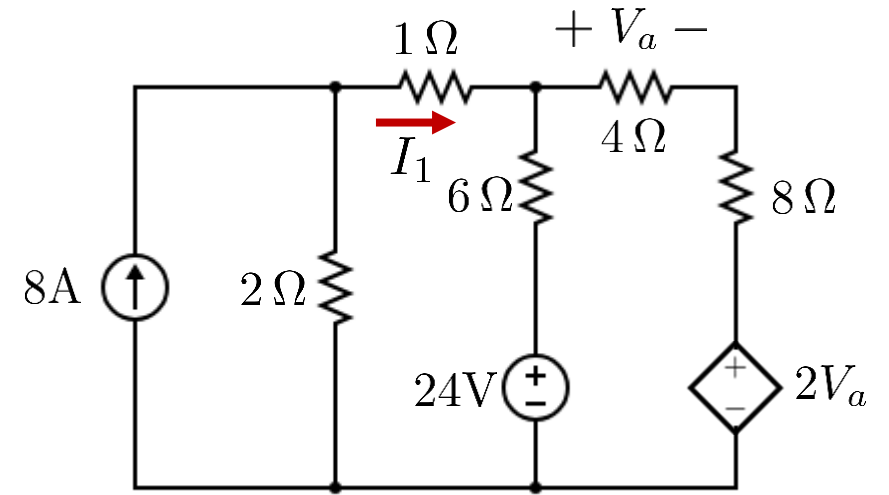Switch off 8A source (replace it with open-circuit).



Loop 1 Equation:

$$9i_1 - 6i_2 = -24$$

Loop 2 Equation:

$$-6i_1 + 18i_2 = -2V_a + 24$$


Controlled source equation:

$$V_a = 4i_2$$

$$i_1 = -\frac{80}{33} \text{ A}$$

$$i_2 = \frac{12}{33} \text{ A}$$
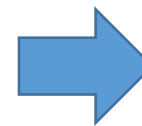
$$I_{1,24V} = i_1 = -\frac{80}{33} \text{ A}$$



$$-6i_1 + 26i_2 = 24$$

$$I_1 = I_{1,24V} + I_{1,8A} = -\frac{80}{33} + \frac{208}{99} = -\frac{32}{99} \text{ A}$$