

LAHORE UNIVERSITY OF MANAGEMENT SCIENCES
 Department of Electrical Engineering

EE 240 Circuits I
 Quiz 2

Name: _____


Campus ID: _____

Total Marks: 10

Time Duration: 15 minutes

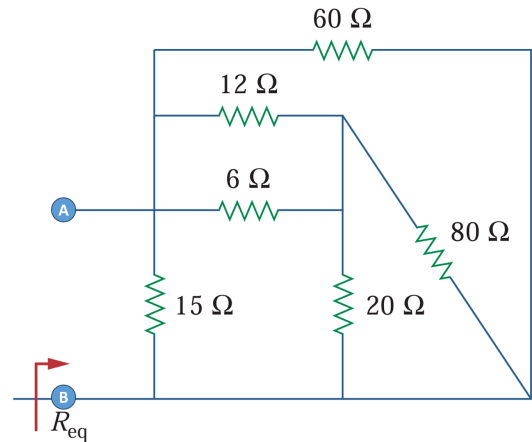Question 1 (5 marks)


For the following network of resistors, find the equivalent resistance across terminals A and B.



Solution: $R_{eq} = 15 || 60 || (80 || 20 + 12 || 6) = 12 || (16 + 4) = \frac{15}{2}$

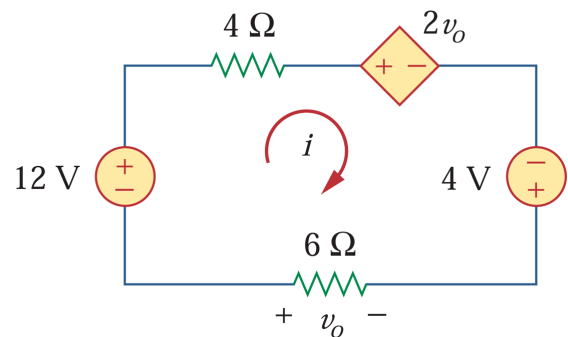Question 2 (5 marks)

For the circuit given below, find v_o and i .



Solution:

Apply Kirchhoff's Voltage Law (KVL) around the loop in the direction of i

$$-12 V + (4 \Omega) \cdot i + 2v_o - 4 V + (6 \Omega) \cdot i = 0$$

Using Ohm's law $v_o = -6i$, substitute into the KVL equation yields:

$$i = -8 A$$

Calculate v_o

$$v_o = 48 V$$